

**ROBOTICS MICROCONTROLLERS COMPUTER CONTROL SPACE**

Everything For Electronics

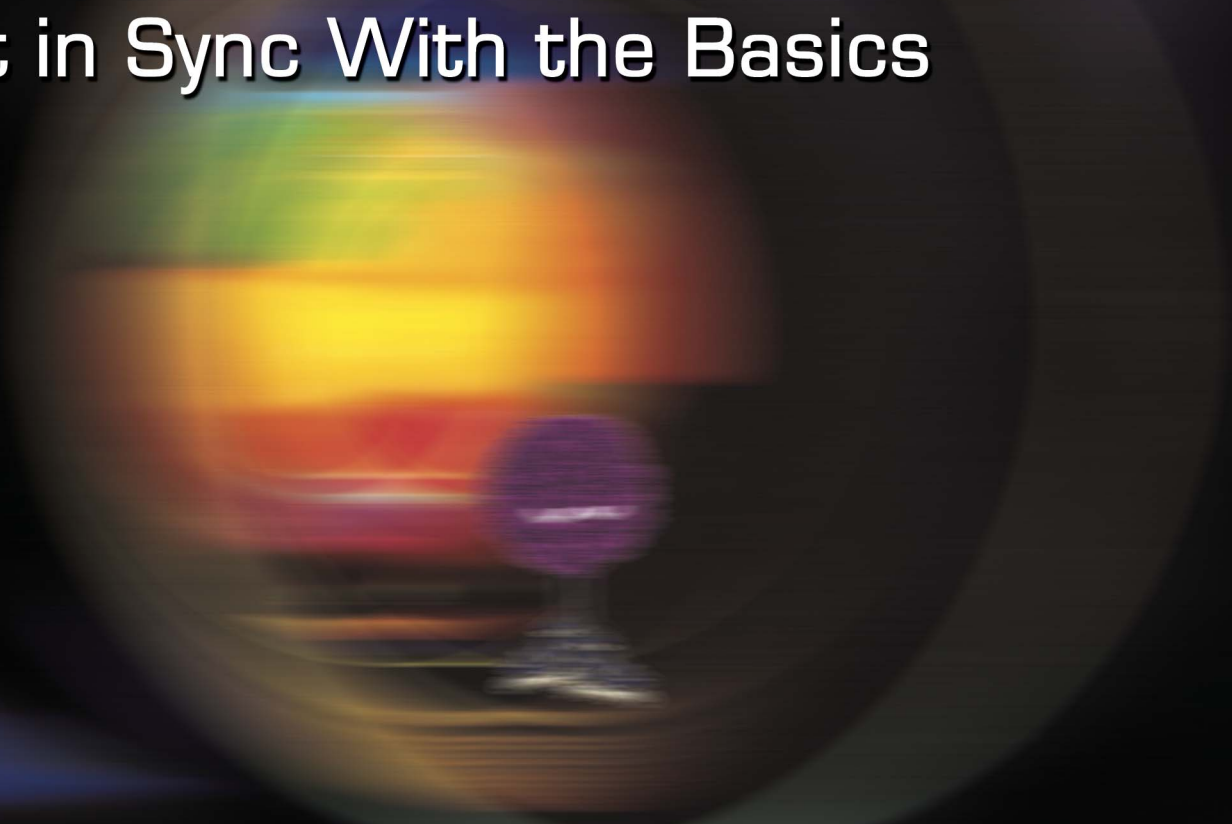
# ***Nuts & Volts***

**January 2005**

[www.nutsvolts.com](http://www.nutsvolts.com)

## **ANATOMY OF A VIDEO SIGNAL**


**Get in Sync With the Basics**

- 
- ✓ **LEDs, the Easy Way**
  - ✓ **Exploring PID**
  - ✓ **Those Enigmatic Interrupts**



**ANYTHING THEY CAN DO...**  
**WE DO...**

**BASICX24™**  
**\$49.95 (Qty 1)**

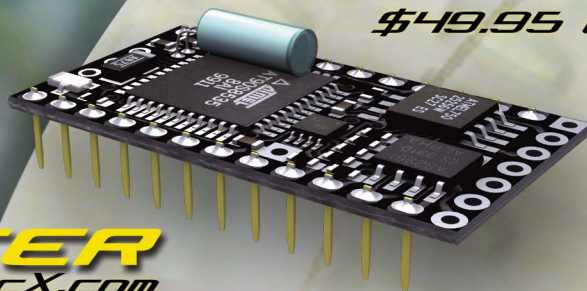

**...FASTER**  
**WWW.BASICX.COM**

Executing 65,000 lines of Basic code per second the BasicX-24 is the KING of Basic programmable microcontrollers.

400 bytes RAM.  
32K User program area.  
19 I/O lines with 8 10Bit ADC's.  
Real multitasking and Serial UARTs.

**...SMALLER**  
**WWW.SITEPLAYER.COM**

Siteplayer is a true stand-alone mini web server.

Super easy to use.  
Standard RJ-45 network interface.  
Control or monitor anything over the web.



**SITEPLAYER™**  
**\$29.95 (Qty 1)**

**...BETTER**  
**WWW.BASICX.COM**

High quality serial 2x16 LCD with backlight

Easy to use.  
2400 & 9600 Baud support  
Software controllable backlight and contrast.

**2x16 SERIAL LCD™**  
**\$39.95 (Qty 1)**



Circle #59 on the Reader Service Card.

**NetMedia**

**NETMEDIA INC. 10940 NORTH STALLARD PLACE TUCSON ARIZONA 85737**  
**WWW.NETMEDIA.COM 520.544.4567**



## Cellphone Headsets!

- ◆ For hands-free cellular phone users
- ◆ Several popular types available (see model numbers below)
- ◆ **Special! - qty discount package, 40pc. carton...\$100.00!**
- ◆ Great gift for family & friends!
- ◆ Brand new, factory retail pack
- ◆ HSC 90-day warranty



◆ For Ericsson 738/788/628/688/630 phones  
**HSC#20246 \$3.95**

◆ For Nokia 6110/6130/5110/5130/7110 phones (shown)  
**HSC#20247 \$3.95**

◆ 2.5mm conn. type for Nokia 8810 - useable w/ Motorola, many other phones!  
**HSC#20248 \$3.95**

## Wireless Video System!

- ◆ Tiny 3/4 in. color camera w/transmitter!
- ◆ Receiver is tuneable for best signal
- ◆ 9VDC batt. conn. for portable camera
- ◆ AC power packs for both units!
- ◆ RCA plugs for A/V out,
- ◆ 'F' conn for whip.
- ◆ New, 90-day warranty



**HSC#80748 \$59.95!**

## CompactPCI® Enclosure Package!

- ◆ CG Mupac's '535 Series'
- ◆ 19" rackmountable 9U cabinet
- ◆ 3-350W hot-swappable front-pull power supplies
- ◆ 21-slot 6U x 160mm front & 6U x 80mm rear IEEE1101.10/1101.11 Compliant CompactPCI subracks
- ◆ Hot-pluggable fan tray w/2 141 CFM top-mntd blowers, bottom blowers also
- ◆ Two front-pull drawers for SCA-type SCSI hard disk drives
- ◆ **Bonus!** 'Force' 'X86' plug-in included at **no extra charge!!** Complete 'X86' computer, 233 MHz, w/VGA, PIO, SIO, USB, 10BaseT and floppy disk drive!!
- ◆ Unused - removed from installation



**HSC#20249 \$295.00**

## System Accessories

- ◆ Force CPCI-680 CPU, 450MHz, 128MB
- ◆ Fast/Wide SCSI, Linux compatible
- ◆ Universal Mode PCI-PCI Bridge

**HSC# 20426 \$195.00!**

◆ Extra plug in 350W switching power supply, incl. CPCI-3500-P-38

**Power Supply \$125.00!**

## Ethernet Xceiver!

- ◆ MT-RJ 850nm VCSEL 2x5 Transceiver,
- ◆ IEEE802.3z, 1000BASE-SX, 1.0625/1.25 Gbps
- ◆ Channel class: 100-M5-SN1, 100-M6-SN1
- ◆ Class I laser safety without OFC circuit
- ◆ Single +3.3VDC operation, < 0.6W PwrDis



**HSC#20273 \$29.95!**

## Color Touch Screen!

- ◆ ALPSLFH8P4032E
- ◆ 4-wire touchscreen intfc.
- ◆ 240x320 diag. LCD STN display w/CCFL backlight (no inverter incl.)
- ◆ 2.75" x 3.50" x 0.375" **Special!...2/\$59.95!**
- ◆ For info, see <http://hubbard.engr.scu.edu/embedded/lcd/lfh8p4032b/lfh8p4032b.html>



**HSC#19827 \$39.95**

## Ultrasonic Range Sensor

- ◆ Similar to SonaSwitch 'Mini-S'
- ◆ Mounts in 1.575" hole!!
- ◆ Fixed range: 5-7 feet.
- ◆ Rep. sense rate: 10Hz
- ◆ See <http://www.halted.com> for tech info
- ◆ HSC 90-day warranty



**HSC#19833 \$9.95**

## HSC Exclusive -- Pixie2!

- ◆ Tiny QRP Xcvr rig! 200-300 mW out
- ◆ Kit incl. all board-mounted parts
- ◆ Use 'walkman' phones
- ◆ **QRP crystal pack special! Finally!...40, 30, 20, 17, 15 & 10 meter calling freqs. in one bag!**



**HSC#crystalpak \$14.95**

**HSC#Pixie2 \$9.95**

## Mini Phone!

- ◆ Miniature, Ultra-Light w/belt clip
- ◆ Has redial, stores 10 numbers, flash/call waiting, hook on/off, mute...MORE!
- ◆ Headset has 2.5mm plug, will work with some cellphones!
- ◆ 3 ringer tones, speed dial!
- ◆ 15' cord, adapter included
- ◆ New, HSC 90-day warranty



**HSC#20244 \$9.95**

## Power Supplies!

- ◆ 'Potrans' Mod. No. PP-303X
- ◆ 300W, Std. ATX
- ◆ **HSC#20190 \$14.95**
- ◆ 'PowerComputing' Mod. No. TCX-20D
- ◆ 200W, Std. ATX



**HSC#19721 \$12.50**

## Hobbyist Alert -- Motors on the Web!

Here is a sample of the way our website is growing...have a look at some of the motors we offer! From time to time, we will show you some of our vast inventory here in this ad, but if you want to see more, go to [www.halted.com](http://www.halted.com) for the full story...we are uploading all the time!

| Motor Type                           | HSC#  | Price   |
|--------------------------------------|-------|---------|
| 1.5V                                 | 18855 | \$2.95  |
| 1.5V .5 AMP                          | 19296 | \$2.50  |
| 115 VAC LEAD SCREW REQ. 10 WATT      | 13184 | \$7.50  |
| 115V 25W 1500 RPM W/GEAR REDUCTION   | 17366 | \$37.50 |
| 115VAC 1/12 HP 3450/2850 RPM         | 14645 | \$14.95 |
| 12-24VDC 17000RPM                    | 19358 | \$4.50  |
| 120V                                 | 11815 | \$3.95  |
| 120V 60HZ 60RPM .82/10 MFD           | 18971 | \$4.95  |
| 120VAC 2.75 AMP 1/15 HP 900/1050 R   | 14709 | \$9.95  |
| 120VAC 213MA 15.482RPM               | 19679 | \$3.95  |
| 12VDC 50 OHM 15DEG 4PHASE STEPPER    | 20264 | \$2.95  |
| 12VDC 50 OHM STEPPER                 | 20265 | \$2.95  |
| 12VDC 50 OHM STEPPER                 | 20262 | \$2.95  |
| 12VDC 50 OHM, 3.75DEG, 4PHS, STEPPER | 92682 | \$2.95  |
| 18.5 VDC HOBBY                       | 17523 | \$1.95  |
| 24VDC                                | 18394 | \$1.95  |
| 24VDC 110 OHM 7.5DEG 4PHASE STEPPER  | 20263 | \$2.95  |
| 3-6VDC                               | 19683 | \$1.95  |
| 3V 1 AMP                             | 19295 | \$2.95  |
| 5.8VDC 1.26A .125X.35 SHAFT          | 18899 | \$2.50  |
| 6VDC NOM. 10000RPM .135 SHAFT        | 18758 | \$2.50  |
| 9-24VDC 15,000 RPM                   | 19669 | \$1.95  |
| ASSY DC HOBBY                        | 17211 | \$4.95  |
| DC                                   | 19697 | \$2.95  |
| DC FF130RH                           | 18136 | \$1.95  |
| DC HOBBY                             | 20092 | \$.99   |
| DC WORM DRIVE WITH DRIVER            | 19796 | \$4.95  |
| GEARED 115 VAC 300 RPM               | 13186 | \$7.50  |
| HOBBY                                | 19034 | \$1.50  |
| STEPPER                              | 18491 | \$4.95  |
| STEPPER                              | 19583 | \$2.95  |
| STEPPER 1.2A 3.3 OHM                 | 19784 | \$12.50 |
| STEPPER 1.8DEG. 2.2V 3.0A            | 19849 | \$17.50 |
| STEPPER 10.6V 5 DIG STEP 35 OZ TO    | 17453 | \$9.95  |
| STEPPER 12 VDC LEAD SCREW REQ.       | 13183 | \$9.50  |
| STEPPER 12V .15A 1.8 DEG             | 18490 | \$4.95  |
| STEPPER 12V 8W                       | 465   | \$15.00 |
| STEPPER 12VDC                        | 17875 | \$9.95  |
| STEPPER 12VDC 75 OHM                 | 19668 | \$4.95  |
| STEPPER 2 PHASE 1.8 DEG PER STEP     | 20000 | \$14.95 |
| STEPPER 2.1V 3.4A 2PHASE MTG.BRKT    | 19999 | \$19.50 |
| STEPPER 24V 16.7W GEARED IMP.PROTEC  | 15787 | \$4.95  |
| STEPPER 24VDC, 12 OHM                | 19701 | \$4.95  |
| STEPPER 24VDC, 9 OHM                 | 19700 | \$5.95  |
| STEPPER 3.5V 1.5A 1.8 DEG STEP       | 18863 | \$6.50  |



## Special Bargains!!

|  |  |  |                                     |
|--|--|--|-------------------------------------|
| Dot Matrix Display<br>#19429 \$8.00      | Laptop Floppy Drive<br>HSC#20180 \$14.95           | 12VDC Adapt., 3.4A<br>HSC#19312 \$9.95   | Cordless USB Adap<br>#19738 \$6.00! |
| Cabinet, 7-Bay<br>#80544 \$20.00         | 33.6k Socket Modem<br>HSC#20217 \$4.95!            | Internet TV Appliance<br>#20027 \$29.95! | 80W Power Supply<br>#18415 \$5.00   |
| VideoWAVE Editor<br>#19656 \$9.95!       | Cordless LAN Card<br>#19737 \$6.00!                | Cabinet, Rack 1U<br>#19437 \$9.00!       | 150W Power Supply<br>#19266 \$8.00  |
| Digital Multimeter<br>#AEEC1504 \$14.95! | 'Mylex' RAID Card<br>New Price!<br>#19427 \$15.00! | Par. Port 3.5" HD Case<br>#19976 \$19.95 | 200W Power Supply<br>#19267 \$10.00 |

You can get more info about any of these items on our website!

**HSC Electronic Supply**

3 Retail/Wholesale Locations:  
Main Office - Mail Orders...  
3500 Ryder St. Santa Clara, CA 95051  
Santa Clara 1-408-732-1573  
Sacramento 1-916-338-2545  
Rohnert Park 1-707-585-7344

Look for us on...



Since 1963!...  
**Silicon Valley's Electronic Marketplace**

Order Toll-Free: 1-800-4-HALTED(442-5833)  
or...ONLINE, AT: [www.halted.com](http://www.halted.com)

Terms: Some quantities limited; all items are subject to prior sale. **Minimum order: \$10.00 plus shipping.** Orders under \$30.00 subject to \$3.00 handling fee, in addition to shipping. All orders shipped by UPS Surface unless otherwise specified. \$6.00 UPS charge added for COD. Visit our website for detailed information on domestic and international shipping methods.



# TABLE OF CONTENTS

Vol. 26 No. 1


## PROJECTS and FEATURES

- 36 SIMPLE SHADED POLE AC MOTOR**  
Power your projects with a twist.  
*by Richard Panosh*
- 42 THE EVER-SHRINKING  $\mu$ C, PART 2**  
More exploration of the PIC10F.  
*by Peter Best*
- 50 CALCULATING CURRENT**  
LED circuits, the easy way!  
*by Mark Dobrosielski*
- 59 VIDEO BASICS**  
Understanding what you see.  
*by Keith Jack*
- 65 PID CONTROLLER, PART I**  
Proportional Integral Derivative control explained.  
*by Aaron Dahlen*
- 71 INTERNET AND THE PCB**  
An insider's view on the collision of these two forces.  
*by Robert Schnyder*

## COLUMNS

- 8 MICRO MEMORIES**  
Yamaha's early music computer.
- 14 Q&A**  
Doorbell circuits; gel-cell answers; Geiger meter; and more.
- 22 NEAR SPACE**  
Hack cell phone batteries for hobbyist uses.
- 28 LET'S GET TECHNICAL**  
Pseudo-random frequency hopping.
- 76 STAMP**  
Enigmatic interrupts.
- 84 TECHKNOWLEDGEY 2005**  
Virus-sensing oscillator; what's under your hood; and more.
- 88 IN THE TRENCHES**  
Considerations for analog to digital conversion.

JANUARY 2005

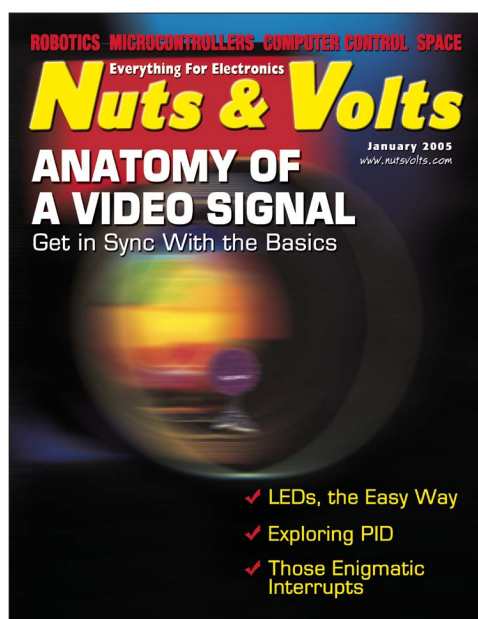

p. 59

p. 50

p. 65

p. 76

## DEPARTMENTS

- 97** Advertiser's Index  
**56** Classified Display Ads  
**26** Electro-Net  
**53** Electronics Showcase  
**32** New Product News  
**74** News Bytes  
**54** NV Bookstore  
**6** Publisher's Info  
**6** Reader Feedback  
**94** Tech Forum

Nuts & Volts (ISSN 1528-9885/CDN Pub Agree#40702530) is published monthly for \$24.95 per year by T & L Publications, Inc., 430 Princland Court, Corona, CA 92879. PERIODICALS POSTAGE PAID AT CORONA, CA AND AT ADDITIONAL MAILING OFFICES. POSTMASTER: Send address changes to Nuts & Volts, 430 Princland Court, Corona, CA 92879-1300 or Station A, P.O. Box 54, Windsor ON N9A 6J5; cpcreturns@nutsvolts.com



# CIRCUIT BOARD solutions for your robotic needs

**FREE**  
Download the  
new version at  
[www.pcb123.com](http://www.pcb123.com)





VERSION  
**2.0**

PCB123 Provides the  
Complete Circuit Board Solution,  
Design Through Order

PCB123 is a **FREE** layout and schematic design software  
tool that quotes your board while you design!

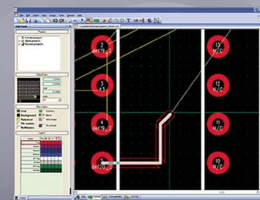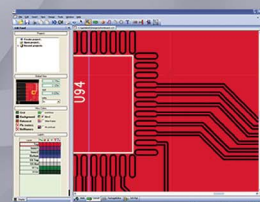**New / Enhanced Features:**

- Import Net lists from multiple CAD vendors
- 145,000+ parts library
- 2, 4, and 6 layer support
- Fast, accurate DRC
- Copper pour with net connectivity
- Fine pitch autorouter with fanout




13626 S Freeman Rd. Mulino, OR 97042 USA  
Phone: (800) 228-8198 x236 / Fax: (503) 829-6657

DOWNLOAD THE NEW VERSION  
@ [www.pcb123.com](http://www.pcb123.com)

**YOUR  
TARGET**

**FOR PROTOTYPE CIRCUIT  
BOARDS**

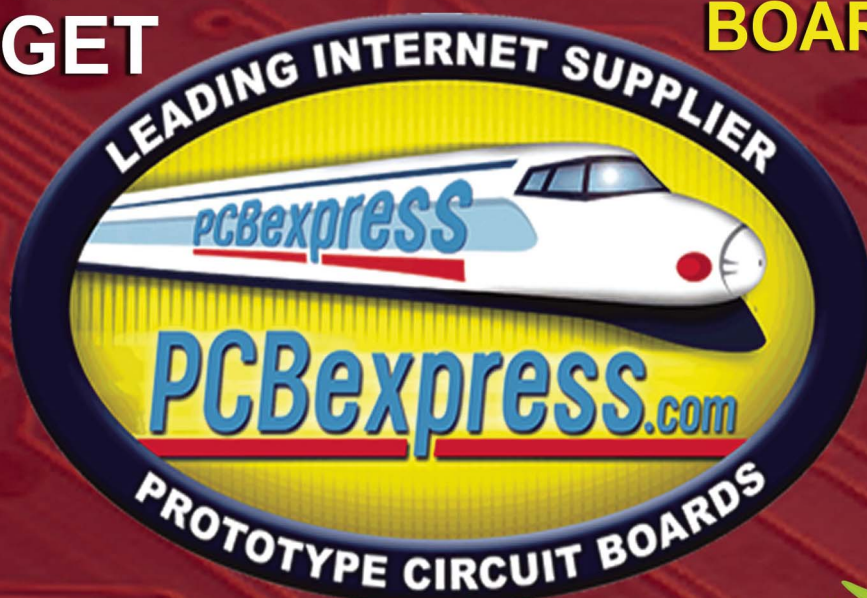

Successfully selling online since 1997.  
Experience you can trust! Try us out today at:  
**[www.PCBexpress.com/nv](http://www.PCBexpress.com/nv)**

Enter  
the link for  
a special  
N&V  
discount!

Need  
**FREE**  
design  
software?

Have  
design  
files?



# Reader Feedback

*Dear Nuts & Volts:*

Just a quick request that your magazine publish more articles describing projects for the PIC Microcontroller that DO NOT involve robotics and that DO NOT require STAMP programming. A program in PIC Basic that would involve, say, model railroad block control circuitry or block detection or a Christmas light display would be nice.

**Jim Cavanaugh**  
via Internet

*Dear Nuts & Volts:*

Your December 2004 column "Open Communication" about ham radio is great. I was interested in just that receiver kit when the issue arrived. It cleared up many of the questions I could not find on the website. I can't wait until the February issue is here for the transmitter kit!

**Gene Arnold**  
via Internet

*Dear Nuts & Volts:*

Please feature more analog "how-to-circuits" such as op-amps and transistor circuits. I know electronics is constantly changing, but there are still plenty of technicians around who have worked with these types of circuits. There is a real void now that *Radio Electronics* and *Electronics Now* are gone.

**Frank Pohs**  
via Internet

*Dear Nuts & Volts:*

This is my last year in college (engineering) and your last four magazines were and still are

extremely helpful for my senior project class in school. However, I still need some help on building my project (a portable microcontroller-based electrocardiograph recorder).

I'm looking for a way to be able to store the collected data into a USB Flash drive (or USB memory sticks) that can be plugged into the device.

**Wilber Hernandez**  
via Internet

*Dear Nuts & Volts:*

While catching up on my magazine reading, I came to the nice "Just for Starters" article on counters by Mark Balch in your October 2004 issue. Mark mentioned the problem of spurious clocking due to switch contact bounce.

A few years ago, while working on a project with several push-buttons, I looked for a low parts-count solution and discovered a chip that some of your readers may not know about and may find as useful as I did.

It is the MC14490 hex contact bounce eliminator. It is a CMOS device in a 16-pin DIP. Each of the six circuits takes an input signal from a bouncing contact and generates a clean digital signal four clock periods after the input has stabilized. The clock frequency (bounce delay) of the built-in clock is set by a single external capacitor. You can get this device from Digi-Key for \$5.12 each, or \$4.10 each if you want 25 of them ([www.digikey.com](http://www.digikey.com)).

**Bob E. Baker**  
via Internet

by J. Shuman

Published Monthly By  
**T & L Publications, Inc.**  
430 Princeland Ct., Corona, CA 92879-1300  
**(951) 371-8497**  
FAX **(951) 371-3052**  
**www.nutsvolts.com**  
Subscription Order ONLY Line  
**1-800-783-4624**

## FOUNDER/ASSOCIATE PUBLISHER

Jack Lemieux

## PUBLISHER

Larry Lemieux  
[publisher@nutsvolts.com](mailto:publisher@nutsvolts.com)

## ASSOCIATE PUBLISHER/ VP OF SALES/MARKETING

Robin Lemieux  
[robin@nutsvolts.com](mailto:robin@nutsvolts.com)

## MANAGING/TECHNICAL EDITOR

Dan Danknick  
[dan@nutsvolts.com](mailto:dan@nutsvolts.com)

## ASSOCIATE EDITOR/ PRODUCTION MANAGER

Alexandra Lindstrom  
[alexa@nutsvolts.com](mailto:alexa@nutsvolts.com)

## CONTRIBUTING EDITORS

|                 |                   |
|-----------------|-------------------|
| Gerard Fonte    | TJ Byers          |
| Peter Best      | Jon Williams      |
| Richard Panosh  | Mark Dobrosielski |
| Keith Jack      | Aaron Dahlen      |
| Robert Schnyder | Ed Driscoll       |
| Paul Verhage    | James Antonakos   |
| Jeff Eckert     |                   |

## CIRCULATION DIRECTOR

Mary Descaro  
[subscribe@nutsvolts.com](mailto:subscribe@nutsvolts.com)

## SHOW COORDINATOR

Audrey Lemieux

## WEB CONTENT/NV STORE

Michael Kaudze  
[michael@nutsvolts.com](mailto:michael@nutsvolts.com)

## PRODUCTION/GRAPHICS

Shannon Lemieux

## STAFF

Kristan Rutz  
Dawn Saladino

## INTERN

Mandy Garcia

Copyright 2005 by **T & L Publications, Inc.**  
All Rights Reserved

All advertising is subject to publisher's approval. We are not responsible for mistakes, misprints, or typographical errors. *Nuts & Volts Magazine* assumes no responsibility for the availability or condition of advertised items or for the honesty of the advertiser. The publisher makes no claims for the legality of any item advertised in *Nuts & Volts*. This is the sole responsibility of the advertiser. Advertisers and their agencies agree to indemnify and protect the publisher from any and all claims, action, or expense arising from advertising placed in *Nuts & Volts*. Please send all subscription orders, correspondence, UPS, overnight mail, and artwork to: **430 Princeland Court, Corona, CA 92879**.

JANUARY 2005





**FREE  
424 page  
Catalog**


## JUST ONE OF OUR MANY GREAT PRE-BUILT & TESTED CONSUMER PRODUCTS!

### Map Reading Made Easy!

XC-0375 \$11.95

The digital map distance calculator is truly a great device. All you have to do is program the scale of your map, then roll the wheel tip along the intended route. It will then display the **ACTUAL REAL WORLD DISTANCE** in miles

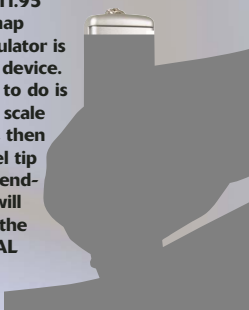(or kilometres) on the LCD. It is light and compact at around 5-inches long.



## We Stock...

Electronic Components

Electronic Project Kits

Test & Measurement Equipment

Power Products & Accessories

Audio & Video Equipment & Accessories

Computer & Telecoms Accessories

Security & Surveillance Equipment



# Easy, Safe, Fast...

Get Your **FREE US\$ Priced Catalog** - all 424 pages!

Just fill out the catalog request form at [www.jaycarelectronics.com/catalog](http://www.jaycarelectronics.com/catalog)

Check our website!

- All of our 6,000+ products with search facilities.
- 128-bit secure on-line ordering - safe & secure.
- Over 3,500 product datasheets & application notes.
- And we're from Australia, so you can trust us!



Moreinfo?

[www.jaycarelectronics.com](http://www.jaycarelectronics.com)

### Get the Video Quality You Paid For With Our Doctor Video Kit

KC-5390 \$64.95

Did you know that you are not getting the best picture from that expensive movie collection you paid good money for? Copy protection is put in place on videos and DVDs for a good reason, but this robs you of the true high quality reproduction that it is capable of. Get the quality you paid for and strip out these annoying signals! It supports composite and S-video signals and can be configured for NTSC or PAL format. Kit includes case, circuit board, all electronic components, and clear English instructions. Note: Some SMD soldering required.

Caution: During signal conditioning, this unit removes copyright protection. Piracy is a crime, & Jaycar Electronics takes no responsibility for its potential for unlawful use.



### Remote Control Extender Kit MkII

KC-5209 \$13.25

If you have a source device such as a DVD player running to a TV in another room, or perhaps a HiFi system with speakers in the other end of your house, you probably get tired of walking to the other room just to change tracks or fast forward etc. This project effectively transfers the IR signal from your remote control and re-transmits it in the other room! Kit includes case, circuit board, all electronic components, and clear English instructions.



### Theremin Synthesiser Kit

KC-5295

\$34.95

The Theremin is a weird musical instrument that was invented early last century but is still used today. The Beach Boys' classic hit "Good Vibrations" featured a Theremin. Kit includes a machined, silk-screened, and pre-drilled case, circuit board, all electronic components, and clear English instructions.


This product is now available pre-built and fully tested - Cat. AM-4025 \$64.95

### Performance Electronics
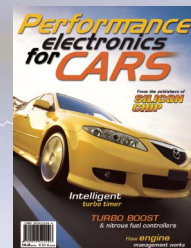
#### for Cars Book

BS-5080 \$13.60


Australia's leading electronics magazine, Silicon Chip Magazine, has developed a range of projects for performance cars. There are 16 projects in total, ranging from devices for remapping fuel curves, to nitrous controllers, and more! The book includes all instructions, components lists, colour pictures, and circuit layouts. There are also chapters on engine management, advanced systems, DIY modifications, and more. Over 150 pages! All of the projects described are available in kit form, exclusively from Jaycar. Check out our website for all the details.


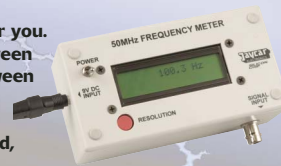
### 50MHz Frequency Meter Kit with LCD Display

KC-5369 \$49.95

If you want a great value frequency meter, then this project is for you. It features Autoranging operation for ease of use, switching between its three ranges. High resolution of 0.1Hz up to 150Hz, 1Hz between 150Hz and 16MHz, and 10Hz above 16MHz. It can be powered by a 9V battery or wall adaptor (not included) and the case measures just 5 1/8" x 2 5/8" x 1". Kit includes case, circuit board, electronic components, and clear English instructions.



Log on to  
[www.jaycarelectronics.com/catalog](http://www.jaycarelectronics.com/catalog)  
for your **FREE** catalog!  
**1-800-784-0263**

(Monday - Friday 09.00 to 17.30 GMT + 10 hours only). For those that want to write:  
100 Silverwater Rd Silverwater NSW 2128 Sydney Australia

# Micro Memories

## The Yamaha CX5M: The Music Computer — '80s Style

**T**hese days, recording music on a PC is a surprisingly straightforward affair. Once you master a program like Cakewalk's Sonar or Steinberg's Cubase, it's a matter of if you can dream it up, you can record it. With programs like Sony's Acid, you don't even need to be much of a musician: just layer various loops to taste and you can start making music.

Back in the 1980s, it was a different story. Back then, we had to walk barefoot in the snow for miles — uphill both ways — to get to our local music store and use stone knives and bearskins to record our music. And we liked it just fine, damnit!

Well, no we didn't because, actually, we had to use the first generation of mass produced computer music technology and it was pretty brutal.

### Meet the CX5M

A case in point was the Yamaha CX5M, sold as a complete, modular music system. It essentially put the guts of a Yamaha DX21 synthesizer

inside of a CPU with a QWERTY keyboard and MIDI interface. To control it, the keyboard/CPU had a multi-pin connection designed to accept a 66-key music keyboard (the kind with black and white keys, not ones that say QWERTY on them — that was Yamaha model number YK10, incidentally). It wasn't touch sensitive and it lacked a pitch-bending wheel, but it had a decent feel to it.

The computer used a Z80 chip as its microprocessor and MSX as its operating system ([www.faq.msxnet.org](http://www.faq.msxnet.org)), which was popular in the early '80s in Europe, Asia, and South Korea, but made few inroads into the US.

The DX21 synthesizer inside of the CX5M was the baby brother to Yamaha's enormously popular (and more expensive) DX7 (there'll be a test later on all of Yamaha's model designations), which popularized a new form of synthesis: digital frequency modulation — FM, for short. Its pure, bell-like tones were seemingly used on every hit record made in the 1980s and used examples of DX7s can be found in

music stores to this day.


The CX5M didn't have a dedicated monitor; instead, an adaptor cable with an RF output was designed to be used with a standard TV, much like the original Atari 2600 and other early video games. I ended up using an old 14" turret dial TV for my CX5M. But that's okay, the graphics in the CX5M were no great shakes — we're not talking Apple Macintosh here.

The CX5M's CPU accepted data two ways: it had an Atari-like cartridge interface and Yamaha produced a variety of cartridges for the machine (more on those in a moment). Like older, 1970s era computers, you could plug a cassette recorder into it. Originally, this was used simply to save programs and files created by the user, but a year or two into the (short) lifespan of the CX5M, Yamaha released a couple of tapes to reprogram the CX5M's synthesizer with new sounds. One tape was mostly musical instruments; the other was mostly sound effects.

### How Did It Sound?

Curiously for a unit marketed by Yamaha (at least in the US) towards musicians and heavily advertised for a year or two in music trade magazines, the unit didn't boot directly to the synthesizer. Instead, when first turned on, it defaulted to a DOS prompt and the user had to type "Call Music" to get into the synthesizer. Great engineering, fellas!

The CX5M.

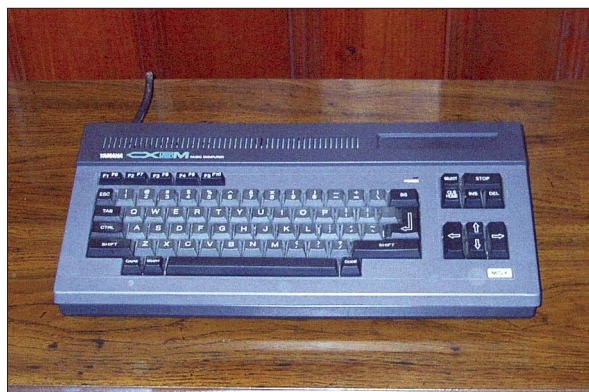

MIDI and keyboard outputs.





Once it was activated, though, how did the synthesizer sound? Pretty good, actually — it was capable of very high quality sounds. (They were very clear and bright, though. I found that I needed to warm many of them up by running them through chorus effects, phasers, and flangers to get sounds that “sat” in recordings better.)

Like its big brother — the DX7 — the CX5M was especially good at mimicking tones that already had a bell-like quality to them: there were great electric piano, tubular bell, xylophone, and glockenspiel sounds.

### Programming Nightmare

The problem was that it was a bear to program these sounds — both programming new sounds and programming compositions based on those sounds. One of the first cartridges that Yamaha introduced for the CX5M was the YRM-101 FM Music Composer software, which allowed for writing scores on a staff-like interface on the screen.

As I recall, it didn't allow for much — if any — recording of real time playing, so everything had to be entered via the keyboard — a daunting task.

MIDI was a relatively new concept when the CX5M debuted, having only been developed by Roland, Oberheim, Sequential Circuits, and other musical electronics manufacturers beginning in 1981. However, it was well established enough by 1985 that the CX5M came equipped with MIDI in and out jacks. I recall mating the unit to my Roland TR-707 drum machine and using the CX5M to sync up drums with compositions I wrote using the Music Composer cartridge and recording both the CX5M and the drum machine simultaneously to my four-track cassette recorder (not exactly Vangelis or Peter Gabriel territory, but you have to start somewhere and, remember, this was pretty much the state of home music recording in 1986).

Another early cartridge for the CX5M was catalog number YRM-103, their DX7 voicing program. It was designed to simplify the programming of Yamaha's then-flagship DX7 synthesizer — a daunting task for even the most experienced electronic musician.

Eventually — and I'll bet I wasn't alone — I simply ended up using

the computer's synthesizer almost exclusively and playing it in real time on recordings. Like I said, you couldn't program it — but it sure sounded pretty good when you played it.

Also, just as with the DX7, reprogramming the synthesizer in the CX5M for new sounds was extremely difficult and I suspect that — just as with the DX7 — most musicians

# \$51<sup>For 3</sup> PCBs

## FREE Layout Software!

## FREE Schematic Software!



- 01 DOWNLOAD our free CAD software
- 02 DESIGN your two or four layer PC board
- 03 SEND us your design with just a click
- 04 RECEIVE top quality boards in just days

[expresspcb.com](http://expresspcb.com)



The YK10 keyboard.



The accompanying voice cassettes.

relied primarily on the CX5M's presets (a list of which is available — but in German — at [www.online.no/~eiriklie/CX5MFAQ.html](http://www.online.no/~eiriklie/CX5MFAQ.html)) and additional sounds, such as those in their voice data cassettes.

## Stepping Stone to the Future

Even up to the 1970s, the synthe-

sizers of the past were bulky machines with seemingly hundreds of cables dangling from telephone switchboard-like interfaces. The first all-synthesizer score in Hollywood — for the 1956 sci-fi classic *Forbidden Planet* by the husband and wife musician team of Louis and Bebe Barron — took three months to complete and utilized equipment that filled their


Manhattan, NY apartment.

Today, an average personal computer — even a laptop — can record music, duplicate all of the great synthesizers of the past, and allow its users to create new sounds, as well.

It took a long time, though, to get to this point and the Yamaha CX5M — even if it was difficult to program — put some great sounds in the hands of its users. **NV**
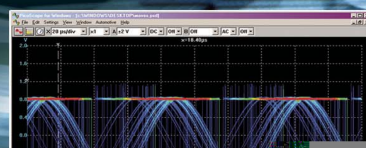
## PicoScope 3000 Series PC Oscilloscopes

The PicoScope 3000 series oscilloscopes are the latest offerings from the market leader in PC oscilloscopes combining high bandwidths with large buffer memories. Using the latest advances in electronics, the oscilloscopes connect to the USB port of any modern PC,





**“Lower costs, higher output—it’s easy to measure the value of eBay.**

My company counts on me to get great deals on test equipment. That’s why I count on eBay. Oscilloscopes, lenses, transformers, signal generators... all the gear I want is there for less. So far, I’ve bought \$40,000 worth of new and used equipment for just \$20,000. With a well-equipped lab, we’re troubleshooting more efficiently and getting products to market faster.”

Stan Searing – eBay User ID: [searing \(595\)](#) ★  
Application Engineering Manager, Pixim, Inc.,  
a 50-person manufacturer of imaging platforms  
in Mountain View, CA.

© 2008 eBay Inc. All rights reserved. eBay and the eBay logo are registered trademarks of eBay Inc. Designated trademarks and brands are the property of their respective owners. All logos subject to availability.

[www.ebaybusiness.com](http://www.ebaybusiness.com)

Circle #36 on the Reader Service Card.





**Ring In The New  
Year With A Ramsey  
AM/FM Broadcaster!**

## Digital FM Stereo Transmitters

- ✓ Rock stable PLL synthesized
- ✓ Front panel digital control and display of all parameters!
- ✓ Professional metal case
- ✓ Super audio quality!
- ✓ 25mW and 1W models!

For nearly a decade we've been the leader in hobbyist FM radio transmitters. Now for 2005 we introduce our brand new FM30 series of FM Stereo Transmitters! We told our engineers we wanted a new technology transmitter that would provide FM100 series quality without the advanced mixer features. They took it as a challenge and designed not one, but TWO transmitters!



The FM30 is designed using through-hole technology and components and is available only as a do-it-yourself kit, with a 25mW output very similar to our FM25 series. Then the engineers redesigned their brand-new design using surface mount technology (SMT) for a very special factory assembled and tested FM35WT version, with 1W output for our export market! Both are designed around an RF tight vinyl clad metal enclosure for noise free and interference free operation. All settings are done through the front panel digital control and LCD display! All settings are stored in the non-volatile memory for future use.

Both the FM30 and FM35WT operate on 13.8 to 16VDC and include a 15VDC plug in power supply. The stylish metal case measures 5.55"W x 6.45"D x 1.5"H and is available in either white or black. (Note: The end user is responsible for complying with all FCC rules & regulations within the US, or any regulations of their respective governing body).

|         |   |          |
|---------|---|----------|
| FM30    | Digital FM Stereo Transmitter Kit, 0-25mW White     | \$199.95 |
| FM30B   | Digital FM Stereo Transmitter Kit, 0-25mW, Black    | \$199.95 |
| FM35WT  | Digital FM Stereo Transmitter, Assembled, 1W, White | \$299.95 |
| FM35BWT | Digital FM Stereo Transmitter, Assembled, 1W, Black | \$299.95 |

## Professional Synthesized Stereo FM Transmitter

- ✓ Fully synthesized 88-108 MHz for no frequency drift
- ✓ Line level inputs and output
- ✓ All new design, using SMT technology

Need professional quality features but can't justify the cost of a commercial FM exciter? The FM25B is the answer!

A cut above the rest, the FM25B features a PIC microprocessor for easy frequency programming without the need for look-up tables or complicated formulas! The transmit frequency is easily set using DIP switches; no need for tuning coils or "tweaking" to work with today's 'digital' receivers. Frequency drift is a thing of the past with PLL control making your signal rock solid all the time - just like commercial stations. Kit comes complete with case set, whip antenna, 120 VAC power adapter, 1/8" Stereo to RCA patch cable, and easy assembly instructions, and the SMT parts are factory preassembled - you'll be on the air in just an evening!

|       |  |          |
|-------|--|----------|
| FM25B | Professional Synthesized FM Stereo Transmitter Kit | \$139.95 |
|-------|--|----------|

## Tunable FM Stereo Transmitter

- ✓ Tunable throughout the FM band, 88-108 MHz
- ✓ Settable pre-emphasis 50 or 75 µSec for worldwide operation
- ✓ Line level inputs with RCA connectors

The FM10A has plenty of power and our manual goes into great detail outlining all the aspects of antennas, transmitting range and the FCC rules and regulations. Runs on internal 9V battery, external power from 5 to 15 VDC, or an optional 120 VAC adapter is also available. Includes matching case!

|       |                                   |         |
|-------|-----------------------------------|---------|
| FM10C | Tunable FM Stereo Transmitter Kit | \$44.95 |
| FMAC  | 110VAC Power Supply for FM10C     | \$9.95  |

## Tru-Match FM Broadcast Antenna

We've been besieged with calls asking us where to get a good quality FM Broadcast antenna. Remember, matching your antenna to your transmitter is the single most important link in your transmitter setup - and a good antenna and match are the secret to getting maximum range.

When we say "match" we mean electrical impedance match... if the proper impedances are not maintained between transmitter and antenna, power is reflected away from the antenna and back into the transmitter! This can cause the final amplifier stage to be damaged, not to mention spurious signals and lousy range. Don't forget, there are three important factors in your broadcast range: antenna, antenna, and antenna! Buy this kit and get the most from your FM Broadcaster!

|       |                                    |         |
|-------|------------------------------------|---------|
| TM100 | Tru-Match FM Broadcast Antenna Kit | \$69.95 |
|-------|------------------------------------|---------|

## Professional FM Stereo Radio Station

- ✓ Rock stable PLL synthesized
- ✓ Front panel digital control and display of all parameters!
- ✓ Professional metal case
- ✓ Super audio quality!
- ✓ 25mW and 1W models!



Our FM100B is the updated version of a truly professional frequency synthesized radio transmitter station in one durable, handsome cabinet. It is used all over the world by serious hobbyists as well as churches, drive-in theaters, and schools. No one else offers all of these features at this price! The included frequency display and audio level meters assist in easy operation. The "B" version now includes some additional functionality including a line level monitor output, improved stereo separation, spectral purity, audio clarity, and adjustable RF Output. An exclusive selectable microphone mixer and auto AGC circuit combines your local mic audio with your music input or mutes the music when mic audio is present. You don't even need an external mixer!

Sound quality is impressive; it rivals commercial stations. Low pass input filtering plus peak limiters put maximum "punch" in your audio, and prevent overmodulation distortion. No wonder everyone finds the FM100B to be the answer to their transmitting needs... you will too! The kit includes a sharp looking metal cabinet, whip antenna, and built-in 110/220 volt AC power supply. An external antenna connection allows hook-up to high performance antennas like our TM100 and FMA200. We also offer a high power export version of the FM100B that's fully assembled with one watt of RF power for miles of program coverage. Many islands and villages use it as their local radio station! The export version can only be shipped outside the USA, or within the US if accompanied by a signed statement that the unit will be exported. (Note: The end user is responsible for complying with all FCC rules & regulations within the US, or any regulations of their respective governing body).

|          |  |          |
|----------|--|----------|
| FM100B   | Super-Pro FM Stereo Radio Station Kit, 5uW-25mW  | \$269.95 |
| FM100BEX | High Power Version, 5uW-1Watt Output             | \$349.95 |
| FM100BWT | High Power Version, 5uW-1Watt, Factory Assembled | \$429.95 |

## Professional Synthesized AM Radio Transmitter

- ✓ Fully frequency synthesized, no frequency drift!
- ✓ Ideal for schools
- ✓ Microprocessor controlled
- ✓ Simple settings

Run your own radio station! The AM25 operates anywhere within the standard AM broadcast band, and is easily set to any clear channel in your area.

It is widely used by schools - standard output is 100 mW, with range up to 1/4 mile, but is jumper settable for higher output where regulations allow. Broadcast frequency is easily set with dip-switches and is stable without drifting.

The transmitter accepts line level input from CD players, tape decks, etc. Includes matching case & knob set and AC power supply!

|      |   |         |
|------|---|---------|
| AM25 | Professional Synthesized AM Radio Transmitter Kit | \$99.95 |
|------|---|---------|

## Tunable AM Radio Transmitter

- ✓ Tunes the entire 550-1600 KHz AM band
- ✓ 100 mW output, operates on 9-12 VDC
- ✓ Line level input with RCA connector

A great first kit, and a really neat AM transmitter! Tunable throughout the entire AM broadcast band. 100 mW output for great range! One of the most popular kits for schools and scouts! Includes matching case for a finished look! The AM1 has been the leading Scouting project for years and years. Try out your kit skills and at the same time...get on the air!

|       |                                  |         |
|-------|----------------------------------|---------|
| AM1C  | Tunable AM Radio Transmitter Kit | \$34.95 |
| AC125 | 110VAC Power Supply for AM1C     | \$9.95  |

- ✓ Fully weatherproof-rugged PVC construction
- ✓ Matches 50 or 75 ohm systems
- ✓ Tunable for a perfect match over the entire 88-108 MHz FM band
- ✓ 25 watt RF power maximum





# What's New For 2005

## The Newest Neatest Stuff!

### Audio/RF Signal Generator **NEW!**

- ✓ DDS and SMT technology!
- ✓ 0 Hz to 5 MHz at 0.1Hz resolution!
- ✓ 0 to 10V peak to peak output level
- ✓ Sine, Square, or Triangle waveform

Following our world famous SG550, we are proud to introduce the SG560, the next generation signal generator!



To begin with we increased the frequency range all the way up to 5MHz and all the way down to 0Hz (yes, we mean zero...or DC!) continuously in 0.1Hz steps across the entire range! Then we gave it a variable output level all the way up to 10V peak to peak in either Sine, Square, or Triangle waveforms! You can also provide a DC offset to the output to recreate TTL, 4000 series logic levels, low voltage logic levels, AC waveforms with a DC component, or just plain AC signals!

SMT and DDS technology is used throughout the SG560 for ultimate performance and reliability. If you're looking for a lab quality sig gen at a super hobbyist price, the brand new SG560 fits the bill...and a whole lot more!

**SG560WT Audio/RF Signal Generator, Factory Assembled \$329.95**

### Hand Held Digital Scope With DVM Readout **NEW!**

- ✓ Digital waveform and measurement display!
- ✓ 10MHz and 40MHz sample rates!
- ✓ Backlit LCD display
- ✓ RS232 output (40MHz model only)
- ✓ Charger, case, probes included

We've seen a lot of portable scopes and scope/meters, and we've also seen the price tags! They have always been way out of the reach and budget of the hobbyist. No more! Now for close to the price of a good DMM you can have a personal scope that also has DVM readout for dBm, dBV, DC, and True RMS! Frequency readout is also displayed on the screen through markers, plus the scopes have two memories for digital storage.



The 40MHz model also includes an RS232 output and serial interface to capture the screen display on your scope to your PC at the mere push of a button! These scopes run on 5 standard AA Alkaline batteries (not included) which provide up to 20 hours of use. You can also use rechargeable AA NiMH batteries instead and they'll be charged with the included power supply! Both units come with a custom foam lined high impact carrying case, set of high quality scope probes, AC power adapter and a comprehensive user's manual. If you're working with electronic circuits, automotive applications, audio and stereo applications or other applications, the personal scope is for you...at a price that can't be beat!

**HPS105E Personal Handheld 10MHz Digital Scope \$229.95**  
**HPS40 Personal Handheld 40MHz Digital Scope w/RS232 \$299.95**

### Dual Display DMM With RS232 Output **NEW!**

- ✓ RS232 output to your PC!
- ✓ Digital and analog bargraph display
- ✓ Backlit LCD display with data hold
- ✓ Manual and auto ranging
- ✓ Includes probes, RS232 cable, & software

We gave you an inexpensive pocket DMM for under 20 bucks. Then we gave you a super multi-purpose professional multimeter that measured virtually everything for 40 bucks. What's next, you ask? You won't believe it! Everything PLUS RS232 serial data output for connection to your PC! That's right, now you can measure, control, and store your DMM and its readings on a graphical display on your PC!



Features both auto and manual ranging with a large 3 1/4 digit display with a 38 segment analog bargraph. Selectable backlight and data display hold features are also included. Plug in the provided DB9 serial cable to your PC, load the included software, and you're off and running with a remote control digital multimeter from your PC! Includes standard test probes, temperature test probes, professional rubber holster, RS232 cable, installed 9V battery, Windows software CD, all in a neat travel case. (Hard to believe for \$85 isn't it!!)

**DVM345DI Dual Display DMM With RS232 Output \$84.95**

### Metal Detector Wand **NEW!**

- ✓ Professional Quality

Just like at the airports, this hand held metal detector wand detects the smallest metal objects hidden in both people and packages. Rocker switch turns the unit on and power is indicated with a green LED. When metal is detected, a red LED is illuminated along with an alert tone. Headphone jack is provided for private security checks. Runs on a standard 9V battery and includes a case & strap. Factory assembled & tested.



**CS10MD Security Wand \$54.95**

### Vehicle EL Wire Set **NEW!**

- ✓ Sound activated electroluminescence!

Now this is neat stuff! Nearly 10' of electroluminescent wire to install in your car. BUT...it gets better! A built-in sensor modulates the EL wire to the beat of music! Can be set for full mode, music mode, or off. Plugs into 12VDC car jack. Fully assembled.



**NWRR30 Red EL Kit \$27.95**  
**NWRC30 Green EL Kit \$27.95**  
**NWRB30 Blue EL Kit \$27.95**

### Electronic Watch Dog **NEW!**

- ✓ Sound activated barking dog on a PC board!

It's nice to have a barking dog to react to someone at our door. But not all of us can have a dog! No problem there, build your own! Two distinct barking sounds are sound activated with a built-in microphone that has adjustable sensitivity. I wish my dog had adjustable sensitivity! This dog eats 9-12VDC. Easy kit assembly.



**K2655 Watch Dog Kit \$32.95**

### Stereo Super Ear **NEW!**

- ✓ Amplifies sound 50 times!

The "Super Ear" is an ultra high gain amplifier that includes two super sensitive mics at a 45 degree angle to give you a true stereo output. Includes on/off switch and volume control. Standard audio jack is provided for audio output. Runs on 3 standard AAA batteries (not included). Easy to assemble and fun to use!



**MK136 Super Ear Kit \$9.95**

### Electronic Learning Labs



- ✓ Learn and build!
- ✓ 130, 300, & 500 In One!
- ✓ Super comprehensive training manuals!

Whether you want to learn the basics of electricity, the theory of electronics, or advanced digital technology, our lab kits are for you! Starting with our PL130, we give you 130 different electronic projects, together with a comprehensive 162 page learning manual. A great start for the kids...young and old!

Step up to our PL300, which gives you 300 separate electronic projects along with 165 page learning and theory manual. The PL300 walks you through the learning phase of digital electronics.

If you're looking for the ultimate lab kit, check out our PL500. Includes a whopping 500 separate projects, a 152 page starter course manual, a 78 page advanced course manual, and a 140 page programming course manual! The PL500 covers everything from the basics to digital programming! Learn about electronics and digital technology the fun way and build some neat projects!

**PL130 130 In One Learning Lab Kit \$42.95**  
**PL300 300 In One Advanced Learning Lab Kit \$69.95**  
**PL500 500 In One Super Learning Lab Kit \$169.95**

### MORE than just friendly on-line ordering!

Clearance Specials, Ramsey Museum, User Forums, Dealer Information, FAQ's, FCC Info, Kit Building Guides, Downloads, Live Weather, Live Webcams, and much more!

**www.ramseykits.com**  
**800-446-2295**



590 Fishers Station Drive  
 Victor, NY 14564  
 (800) 446-2295  
 (585) 924-4560

Where  
 Electronics  
 Is Always  
 FUN!

- ◆ Build It!
- ◆ Learn It!
- ◆ Achieve It!
- ◆ Enjoy It!

Circle #79 on the Reader Service Card.

Prices, availability, and specifications are subject to change. Visit [www.ramseykits.com](http://www.ramseykits.com) for the latest pricing, specials, terms and conditions. Copyright 2005 Ramsey Electronics, Inc...so there!



## Get The Catalog!

Get the brand new 2005 Ramsey Hobby Catalog! **64 value packed pages** of the newest goodies around! Order your copy on-line or give us a call!

# Electronics Q&A

In this column, I answer questions about all aspects of electronics, including computer hardware, software, circuits, electronic theory, troubleshooting, and anything else of interest to the hobbyist.

Feel free to participate with your questions, as well as comments and suggestions.

You can reach me at:  
**TJBYERS@aol.com**

## What's Up:

Got batteries? I've got answers for monitoring gel-cells. Have a transistor you can't replace? Got that covered, too.

And just for fun, I threw in a couple of one-night projects — Geiger meter, anyone?

## Operational Amplifier

**Q** I recently had to make a circuit to subtract two DC voltages. I first considered using a differential op-amp with one voltage feeding the positive input and the other connected to the negative input. After doing the math to balance out the four resistors for the gain I wanted, it struck me that a summing amp has an advantage: only one feedback resistor has to be changed to alter the gain!

I used an inverting op-amp for one input and fed it to a summing amplifier and ended up with the right number (Figure 1). What are the ramifications between the differential amp and my solution to produce the difference of two voltages?

**John  
via Internet**

**A** Operational amplifiers (op-amps) are so named because they were originally used to model the basic mathematical operations of add, subtract, multiply, integrate, etc. in electronic analog computers. Figure 2 shows how the op-amp is configured to “calculate” a few popular math functions.

In the Add circuit, each voltage is weighed equally and there is no limit (well, almost) to the number of inputs you can deal with. Notice that only

one resistor ( $R_f$ ) is needed to define the gain of the circuit and the output is inverted. The Subtract circuit measures the difference between  $V_1$  and  $V_2$  by using the inverting and non-inverting inputs of the op-amp. It's limited to just two voltages. With the values shown, both of these circuits provide a gain of 10x.

The Weighed and Average circuits are special cases of the Add circuit. The gain of the Weighed circuit is 17.5 for the values shown and the Average circuit has unity gain. In the Inverting configuration, both resistors have to be the same value.


What are the ramifications? Obviously, your inverting design allows you to mix both addition and subtraction with multiple inputs, something a single op-amp can't do. Also, a single resistor determines the gain of the stage. On the other hand, each op-amp in the chain adds its share of noise to the output, which could be a factor in very low voltage measurements.

## Ding Dong

**Q** I am trying desperately to build a doorbell intercom. I want it to sound like a ding dong or ding ding version — something pleasant to that extent. I have close to 100 LM555 timers in my possession and I am willing to use as many as it takes.

**Alex Belenkiy  
via Internet**

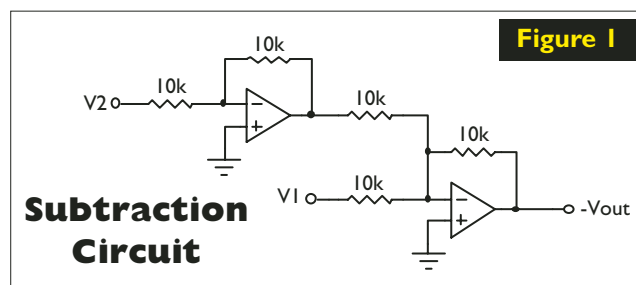**A** With the doorbell chime circuit in Figure 3, you'll have close to 98 left over for other projects. Yep, it only takes two 555 chips to make a reasonable facsimile





of a mechanical chime.

The first 555 is a one-shot monostable multivibrator. It controls the second 555 — an astable multivibrator oscillator that drives an 8 Ω speaker. The frequency of the oscillator is, of course, determined by C1, but that would just make a one-tone bell. To change the frequency, the voltage on the control input (pin 5) is modulated by the 2N2222A transistor. When the one-shot output is high, the transistor turns on and grounds the control pin through a 100K resistor. When the output goes low, pin 5 is tied high through the 100K resistor, thus giving the bell its distinctive ding-dong effect.

To further enhance the effect, the astable oscillator is also powered by the output of the monostable multivibrator. When the output is high, voltage is applied to the Vcc and Reset inputs (pins 8 and 4, respectively). When the output goes low, the voltage slowly declines. This causes the volume of the tone to decrease, as it does in a real metal chime. Capacitor C2 determines the time of the decay.

## Is My Bot's Battery Dead?

**Q** In my new bot, I have two battery power supplies — one 6 volt and one 12 volt. The 6 volt takes care of my servos and the 12 volt is for the drive motor. The batteries are down at the bottom of the bot with the control stuff on top. What I need is a low battery indicator for both banks. I thought to use a green LED for the servos and a red one for the drive batteries. Do you have any answers?


**Don**  
via Internet

**A** There are any number of under-voltage ICs that can fill the bill, but I decided on the ICL7665 for this application. It has a proven track record, comes in an eight-pin DIP package, and is readily available. The chip draws a mere 3 μA of power and can operate over a Vcc range of 1.8 to 16 volts, independent of the voltage to be monitored.

The ICL7665 sports two individually programmable voltage detectors; one of the voltage detectors is under-voltage and the other is overvoltage. Both have open drain outputs — which explains the transistor on the Out1 output (Figure 4). It inverts the overvoltage signal into an undervoltage signal by switching on the LED when the overvoltage falls below the

**Figure 2**

### Add

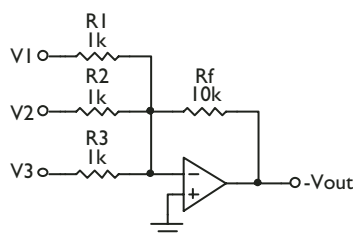


For  $R1 = R2 = R3 = R$  (amplified gain)

$$-V_{out} = \frac{R_f}{R} (V1 + V2 + V3)$$

For  $R1 = R2 = R3 = R_f$  (unity gain)


$$-V_{out} = V1 + V2 + V3$$

### Weighed

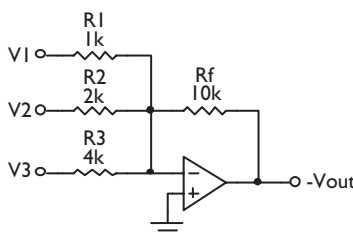


$$-V_{out} = \frac{R_f}{R1} V1 + \frac{R_f}{R2} V2 + \frac{R_f}{R3} V3$$

### Inverter

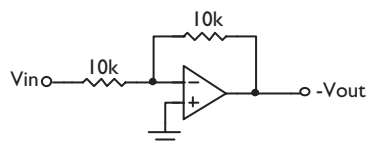

### Subtract

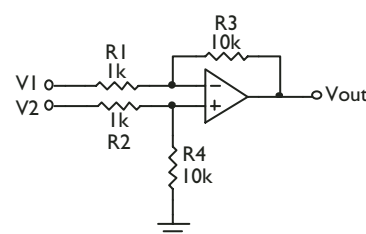


For  $R1 = R2$  and  $R3 = R4$  (amplified gain)

$$V_{out} = \frac{R3}{R1} (V2 - V1)$$

For  $R1 = R3$  and  $R2 = R4$  (unity gain)

$$V_{out} = V2 - V1$$


### Average

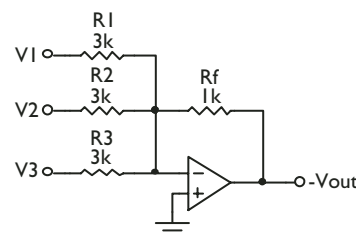


For  $R1 = R2 = R3 = 3R_f$

$$-V_{out} = \frac{V1 + V2 + V3}{3}$$

### Buffer

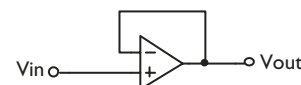

**Figure 3**

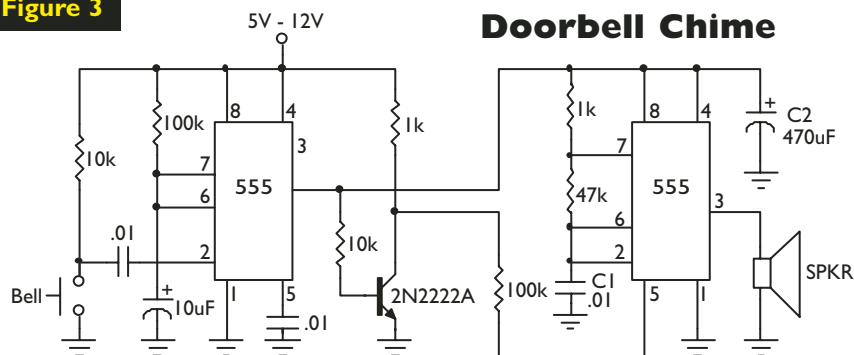

programmed limit. This happens because the 2N2222A transistor's base is shorted to ground and can't conduct when the battery is "overvoltage." When the battery voltage declines below the threshold limit, Out1 goes high (open) and the transistor turns on (clever, huh?).

Both channels have a hysteresis pin that prevents the LEDs from cycling, but I decided not to use them in this design. I feel that a flickering LED will get your attention a lot faster than one that just drones on, especially in the heat of battle.

You'll notice that there are two values for the sense resistors. That's because you didn't tell me whether the batteries were NiCd or gel-cell, so I calculated for both. The LED turns on when there's approximately 20% of the charge left in the battery.

## How Dead Is It?

**Q.** I have recently acquired several 6 V, 9.5 A/H gel-cell batteries. My questions are how do I tell when a gel-cell is dead and how do I build a simple charger for those that are not? Most of the batteries measure between 2 and 4 volts, with some at 0 volts.

**Naic via Internet**

**A.** Unlike NiCd and lithium batteries — which maintain a constant output voltage until "dead" — the state of charge of a gel-cell is very much defined by its voltage. Figure 5 shows the voltage range for a single gel-cell. To find the voltage range for your battery, multiply the voltage by the number of cells in the battery. For a 6 volt, three-cell battery, the range is 5.79 (0%) to 6.39 (100%).

If the voltage of your battery is below the lower limit, don't panic. This happens when the battery is left unattended for long periods. If the battery hasn't been abandoned for too long, you can most likely bring it back to life. What happens when a battery totally discharges is that the plates sulfate.

Some say that the ideal way to bring a dead battery back to life is by pulsing it with a high current to "blow" the sulfate off the plates. I suggest a C/1 charge (10 amps, in your case) with a 10% duty cycle.

In this circuit (Figure 6) I'm using the output of the 555 to pulse a TIP145 Darlington pass transistor. The pulse frequency is about 500 Hz, but that's easily adjusted via the 0.22  $\mu$ F capacitor.

The transformer is 12 volts, center-tapped with an output of 10 amps, like the 7846TR from Marlin P. Jones & Associates (800-652-6733; [www.mpja.com](http://www.mpja.com)). The voltage is only partially filtered, hence the 1N4148 diode and 100  $\mu$ F filter cap so that the Vcc of 555 isn't on the same roller coaster and has a steady power source.

When the charge in the gel-cell reaches 6.2 volts, the pulser turns off and the LED turns on. I know this is short of a full charge, but now it's time to switch the battery over to a conventional charger for final charging.


## Dip Oscillator Meter

**Q.** I would like to build a Dip meter in order to learn more about them. Do you have any advice or know of any books that introduce the theory of a dip meter?

**James Ko via Internet**

**A.** Originally known as a grid DIP meter, the dip oscillator is a simple instrument used to measure the resonant frequency of a tuned circuit. Typical applications include antenna matching, filter trap tuning, determining unknown inductance or

**Figure 4**

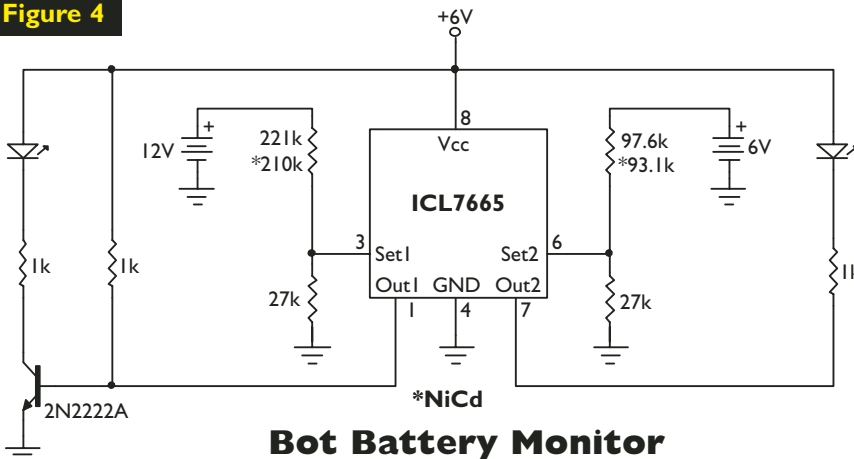

**Bot Battery Monitor**



capacitance, measuring the length of a coaxial cable, and the list goes on. No physical connection is required. You just have to bring the sense coil in close proximity to the circuit under test.

Basically, the dipper is an LC oscillator that's tuned by a variable capacitor. The sense coil, which is traditionally plugged into a socket at the top of the meter, determines the frequency sweep of the oscillator. When the coil is placed close to a tuned circuit, you adjust the frequency using the variable capacitor. When the frequency of the dip oscillator matches the frequency of the circuit under test, the energy is transferred from the oscillator to the passive circuit. In effect, there is a dip in the output power of the oscillator.

There are many dipper designs implementing every sort of oscillating device from vacuum tubes to transistors to tunnel diodes. The simplest is a one transistor circuit built around an MPF102 FET (Figure 7). It's tuned for a range of 2 to 60 MHz, but small changes in the values of the tuning capacitor and coil can extend that range up or down.

Construction is straightforward, but the connecting wires should be kept short and to the point to avoid spurious radiation.


Calibration is traditionally done by marking the dial using tank circuits of a known frequency. This technique will put you in the ballpark. For those of us who have graduated to the digital age, Figure 8 has a digital counter output.

Coil information is shown in Table 1. PVC water pipe — found at any Home Depot — makes an excellent coil form. The tap is counted from the bottom of the coil and the winding length is critical. Spread the windings apart, if necessary.

Lastly, the wire is enamel coated magnet wire, not plastic insulated.

Figure 5

### Gel-Cell Charge vs Voltage

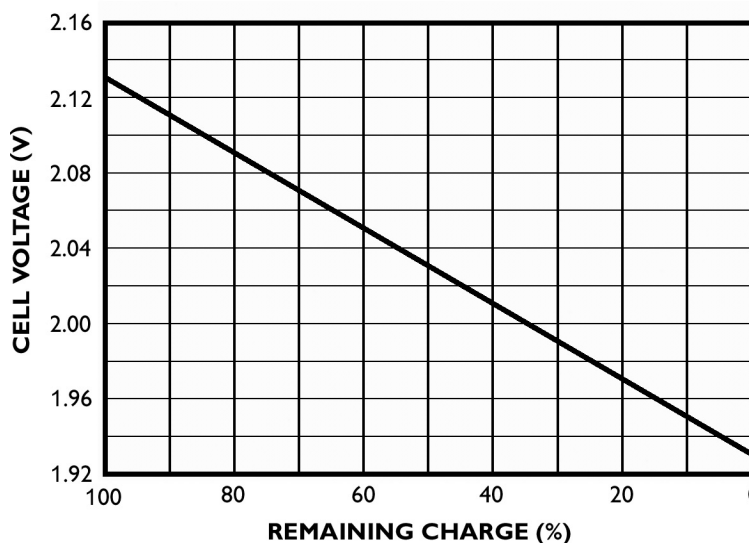

### Obsolete Transistors

**Q.** Can you please find updated numbers for the following obsolete transistors: HEP724, HEP739, SK3011, SK3003 ... 2N1524, MPS3708, TIS-59? I feel that the TIS-59 can be replaced by a 2N3819 or a MPF-102, but that's only a guess.

**Kendrick  
via Internet**

**A.** A few years back, there were no less than four major semiconductor makers who offered a line of replacement transistors, including Motorola (HEP), GE (GE-), Sylvania

(ECG), and RCA (SK). These parts were originally intended for the replacement, hobbyist, and experimental markets and — in time — found applications in industrial repair and maintenance departments.

Today, only NTE ([www.ntec.com](http://www.ntec.com)) survives. I was able to find all but one of your transistors on their cross reference website ([http://nte01.ntec.com/nte/NTERefSemiProd.nsf/\\$\\$Search?OpenForm](http://nte01.ntec.com/nte/NTERefSemiProd.nsf/$$Search?OpenForm)) — and that's only because the TIS-59 is listed as a TIS59 (originally from TI). Yes, the hyphen matters in the search engine. Once you have

### Gel-Cell Conditioner


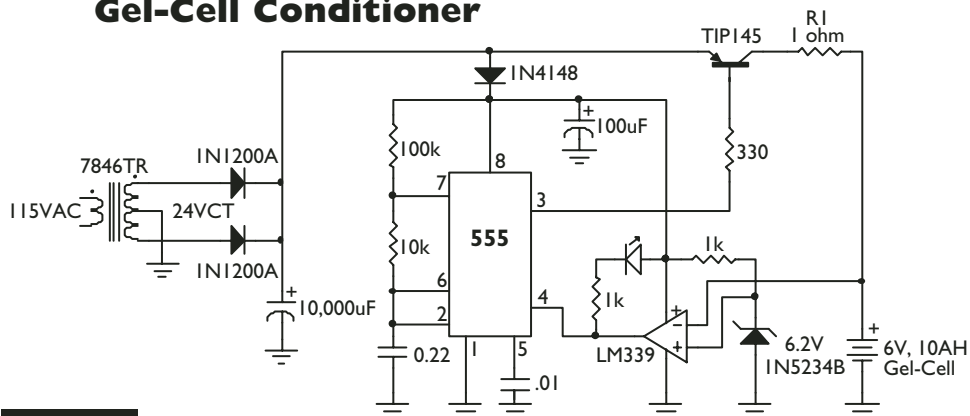


Figure 6

**Figure 7**

## Dip Meter

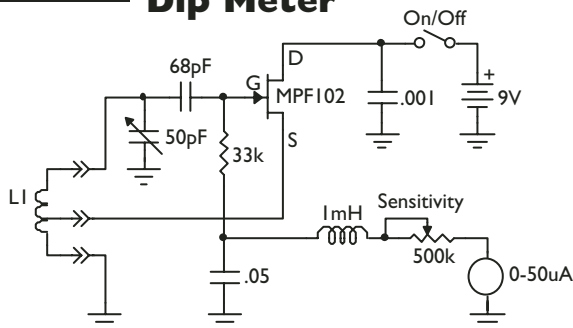

found an NTE replacement, go to the FindChips website at [www.findchips.com](http://www.findchips.com) and enter the NTE number.

Jameco and Mouser both have in-depth stocks of these devices, but they can be more expensive than a generic replacement.

For example, the HEP724 cross references to an NTE123A — which is the equivalent of a 2N2222 that sells for one-third the price.

The NTE website has data sheets that you can use to find a cheaper generic. Follow the guidelines in the question below (“Transistor Selection”) to find a suitable replacement from a data sheet. And — yes — the MPF102 is an acceptable substitute for the TIS59, according to their data sheets.

## Specialty Transistors

**Q.** I am an electronics hobbyist and I was wondering if I know of any websites that I could visit for semiconductor equivalents. I have been looking for a transistor whose reference is H8N80FI and can't find it in any

transistor catalog.

**Elimane Bathily**  
via Internet

**A.** Not all transistors have a cross reference — especially those which are privately labeled like the H8N80FI. In cases like this, I do a Google search ([www.google.com](http://www.google.com)). As a rule, I hit nothing, but I got lucky this time and came up with a 2SK1363 — an N-FET power transistor. Unfortunately, this transistor is only available overseas and not stateside, as are many specialty transistors and ICs. Try Donberg Electronics at [www.donberg.ie](http://www.donberg.ie)

(Before you send that letter, let me say that the 2SK1363 was also used in an Apple CRT monitor and an Apple repair center may still have one or two on a dusty shelf.)

## Transistor Selection

**Q.** My question is what the determining factor is in transistor choice? How interchangeable are the different types? I have a circuit that calls for a 2N3707, which I have never even heard of.

**B. Brown**  
via Internet

**A.** From an engineering point of view, there are four critical parameters when it comes to choosing transistors: voltage, current, gain, and frequency.

Supposedly, each transistor is custom fit (as in a specific 2N number) to fill a niche for performance and cost. That is, you don't want to pay for performance you don't need, but you do not want to be caught short with a marginal part, either. Hence, all the various numbers.

However, like most electronic devices, a transistor with better specs can always replace one with lesser expectations.

As for the 2N3707 — which is now obsolete — it's an NPN general-purpose audio transistor rated at 30 volts, 200 mA, and a gain of 100 to 400.


To me, that sure sounds like a 2N2222, which is rated at 60 volts, 800 mA, with a gain of 300 at 150 mA. Both are of the same sex — NPN as opposed to PNP — both are silicon (not germanium), and both have an upper frequency limit of 250 MHz. So, why does your design specify the 2N3707? Probably because the designer got a good deal (price break) on this transistor at a time when he needed those parameters.

## Radioactive Peanuts

A couple of years ago — January 2003, to be exact — I published a circuit for a Geiger counter using an NE-2 neon lamp. I found the design in an old copy of *Experimente mit Strahlenquellen*.

**Figure 8**

## Dip Meter with Counter Out

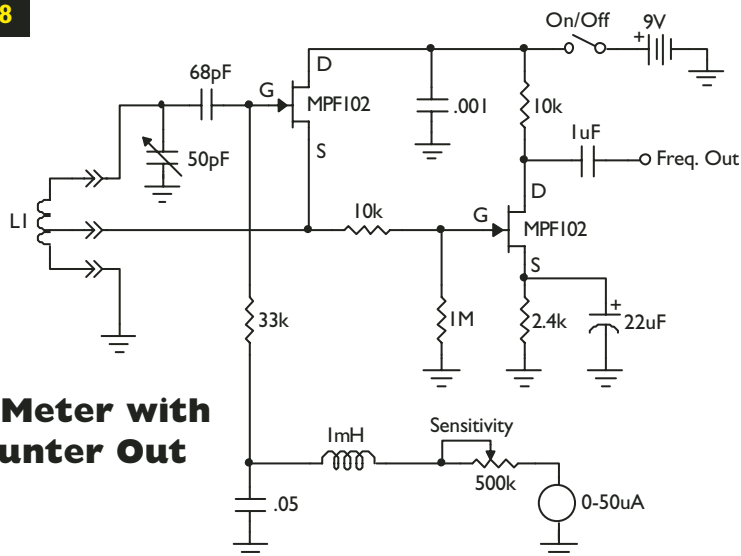



Many of you had problems with that circuit in that there was too much variation between the NE-2 lamps, making it unusable or impossible to calibrate the counter.

Well, I have done a little research since then and think I have found a better design that uses — of all things — a peanut can. The “Cheap, but Sensitive Radiation Detector” can be found at [www.techlib.com/science/ion.html](http://www.techlib.com/science/ion.html). The design is by Charles Wenzel, whose designs I trust. Figure 9 shows the basic concept. His commentary is self-explanatory, so I won’t go into it here.

The second missing part of the equation was a radiation source. I found that on eBay under the guise of a Coleman lantern mantle. One mantel produces 1.5 mr/hr (about 750 counts per minute) and sells for about \$5.00. You can also find them from time to time at K-Mart and camping supply houses. Look for the brand that says “Made in India.”

The radioactive ingredient in the mantle is thorium-232. By itself, thorium is only slightly radioactive, emitting only alpha particles that are easily blocked by a thin piece of paper.

However, thorium breaks down into two parts: a small part — the alpha radiation — and a larger part called the decay product. The decay products include radium and radon, which emit alpha and beta particles and gamma rays.

In fact, the longer thorium stands (half-life is 14 billion years), the more radioactive it gets — but that’s another story.


## Three Coins in a Fountain

**Q.** I want to hook up one or more submersible fountain pumps (typically 115 VAC, 0.8 A) to a circuit that will vary the flow of water in concert with the input from a sound source. Should the circuit change the voltage or current?

**Bob Slusher**  
via Internet

| Frequency MHz | Number of Turns | Tap at Turn No. | Wire AWG | Coil Diameter | Winding Length |
|---------------|-----------------|-----------------|----------|---------------|----------------|
| 1.8-3.8       | 82              | 12              | #26      | 1 1/4         | 1 9/16         |
| 3.6-7.3       | 29              | 5               | #26      | 1 1/4         | 9/16           |
| 7.3-14.4      | 18              | 3               | #22      | 1             | 3/4            |
| 14.4-32       | 7               | 2               | #22      | 1             | 1/2            |
| 29-64         | 3 1/2           | 3/4             | #18      | 1             | 3/4            |


**Table 1.** Dip meter coil data.

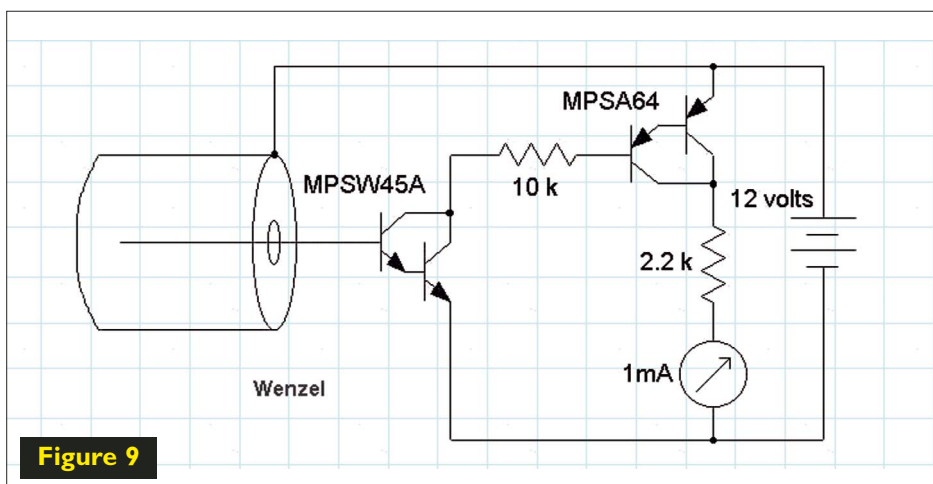

**Figure 9**

**A.** Controlling the speed of an AC motor is fairly simple. It’s done all the time in hand drills, but what you’re trying to control is a flow of water, which has a lot of latency — resistance to change in flow. No matter how hard you try, the fountain-head won’t follow the fast-moving audio. The controller needs a low frequency filter to turn sporadic into rhythmic. Here’s what I’d do (Figure 10).

In this circuit, I’ve used the control voltage input (pin 5) of a 555 timer to PWM (pulse width modulate) the speed of the motor. With this design, the motor is never completely off — for good reason. Starting a water flow from a stall takes a lot longer than revving it up from a trickle, making your fountain slightly more responsive. It also takes care of the low frequency filter I mentioned earlier by using the inertia of the

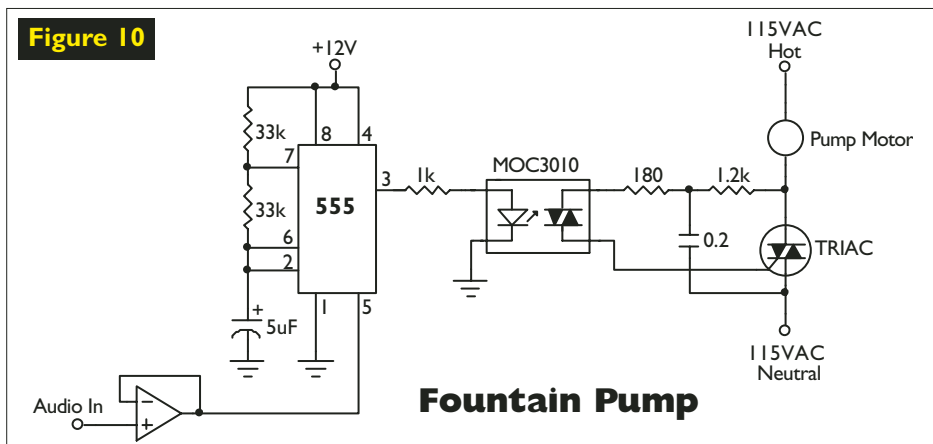

**Figure 10**

**Fountain Pump**

motor itself.

Like the previous question, you have to provide the audio interface. Just make sure that the voltage sweep on pin 5 is between the Vcc and GND limits or you'll fry the 555 chip.

This input is not linear over this range, which is okay for the type of output you desire. Also, 5  $\mu$ F may not be ideal for your particular pumps. Play with it until it works right for your display.

## MAILBAG

Dear TJ,

In reference to the thermocouple answer (November 2004), back when I was still gainfully employed, we routinely made thermocouples for plant use. The process consisted of twisting the two materials together so that they were in intimate contact and discharging a large

capacitor through the junction.

**Dave Schoepf**  
via Internet

Dear TJ,

If you put 12 amps through a 1  $\Omega$  resistor, it better be 144 watts instead of 10 W (November 2004 issue)!

**Charles D. Geillker**  
Professor of Physics

**Response:** *That would be true if the current flowed 24/7, but the thermocouple welder shown in that answer has the current flowing for about 1/10 of a second while the user taps the wires to the carbon rod. This isn't nearly enough time for the resistor to heat up to even 10 watts. It's called duty cycle. — TJ*

Dear TJ,

Your block diagram for a slide

viewer will indeed invert negatives, but the color will not be correct. All negative color film uses an orange mask that corrects for impurities in the magenta and cyan dyes. This will make the inverted image appear to have a sickly blue cast.

**Bill Runkle**  
via Internet

## Cool Websites!

Learn to speak Aussie.

[www.aussieenglishcd.com/  
multimedia\\_samples.php](http://www.aussieenglishcd.com/multimedia_samples.php)

Lots of high voltage stuff.

[http://205.243.100.155/frames/  
lichtenbergs.html](http://205.243.100.155/frames/lichtenbergs.html)

What's up? Kennedy Space Center.

[www.ksc.nasa.gov](http://www.ksc.nasa.gov)

# Microprocessor Training System

Compact Rugged Design

8085A Microprocessor

Easy to Use

Standalone Use

PC Connectivity

Manuals on CD

Self-Instruction Manual

Application Manual

Serial Port


Lab Manual

Analog I/O

Digital I/O

Fully Assembled or Kit

High Level Languages

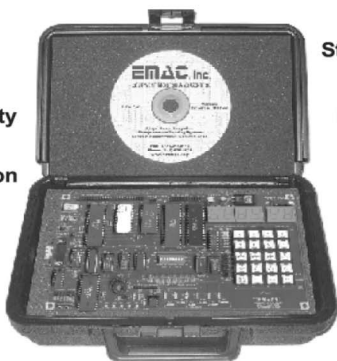

Primer Trainer Prices Start at \$120.00 USD

\* Primer PAK Shown in Picture \*

Since 1985  
OVER  
19  
YEARS OF  
SINGLE BOARD  
SOLUTIONS

**ENAC, inc.**  
EQUIPMENT MONITOR AND CONTROL

Phone: (618) 529-4525 • WWW: <http://www.emacinc.com>

## APEC 2005

March 6-10, 2005  
Austin Hilton Austin, TX

The Premier Global  
Event In Power Electronics

- Plenary with Industry Executives sharing their vision of the future
- 329 Presentations from 28 Countries
- 14 In-depth Professional Education Seminars
- 150 Vendor Exhibition Booths
- Catered Reception with Exhibitors
- 12 Exhibitor Seminars
- 3 Lively, Informal Rap Sessions
- 19th Annual Micro Mouse Contest

Networking Events throughout  
the Conference

Keep checking  
[www.apec-conf.org](http://www.apec-conf.org)  
for updates!



SPONSORED BY





## CCFL Florescent Light Inverter




New power inverter drives 2 lamps up to 5W each! Simple to use, 12 VDC in, connect florescent lamps to output. Module generates correct starting and operating voltage, lamp current and is even dimmable!

0128520R .....\$9.95
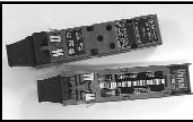
## Fiber Optic Transceiver

New, by Infineon. Has laser transmitter and receiver in one package! 1.25 Gb/s data rate up to 700 M on low cost multimode fiber! Super small size, complete specs on the web. Make your own fiber optic link!



0125461R (Set of two) .....\$19.95



## Hitachi LCD display

16 character by 2 lines 5x8 dot matrix character 64.5 x 13.8 mm viewing area STN neutral mode reflective LCD recently discontinued by

Hitachi but a very common and most used part. Directly crosses over to the Optrex DMC16249, brand new stock!

0123260R .....\$4.95



## Laser Scanner Bar Code Module

Wow! What a cool item!

Brand new laser scanner module (size 1x1x1.5") includes red laser, beam splitting mirror, opamps, photo sensor, transistors, processor, ICs, etc. From handheld laser barcode reader. We sold out of the last style we had! No specs, but buyers figured out the hook up for the last group, we'll post on the web any new info on this one, should be easy, has just 12 pins on the connector.

0131346R .....\$14.95



## C size Nicad Battery

This is the real deal, a true 2 A Hr Nicad. Button top works in any device too! Brand new by Sanyo.

0130380R .....\$2.00



## Powerful DC Motor

Made by Johnson Electric 12 VDC @ 0.85 A no load, 17,000 rpm, 3 vdc @ .51 amps 4,200 rpm, 6 vdc @ .6 amps 8,500 rpm.

Similar to Johnson Electric HC313MG series but higher power. Actually runs as low as 1 volt operation! (1200 rpm .46 amps). Size: 2" l x 1.5" dia 7/8" long eccentric brass shaft end easily broken off to form a .5" long x .312 dia round shaft end.

0123850R .....\$4.95

## LED BLOWOUT !!!



Here's a deal that just will not last long Windsor's LED Blowout! Super high quality, factory prime bright LEDs. Ideal for all those projects that you've wanted to build, but just didn't have the quantity of LEDs needed. You will not find pricing like this ever again we bought out two factory inventories! Here's the scoop: Big bag o leds have 500 pcs and are all RED jumbo 5 mm size with crystal clear bulbs. You pick the luminous intensity, bear in mind that the 2500 mcd high bright units are flashlight intense! Big buyers will love the 2,000 LED boxes! These LEDs are the smaller T 1 size with full leads, available in Red or Green. Imagine 2,000 Leds for less than a penny each!

0131288R High Bright 500pc bag .....\$15.00  
0131292R Standard Bright 500 pc bag .....\$15.00  
0130956R Box o leds Red 2,000pcs .....\$19.95  
0130955R Box o leds Green 2,000pcs .....\$19.95


## Windsor's Blue LED Special



Holy Smokes! Can you believe the price on this BLUE LEDs? First quality from our factory buyout. Big and bright! These normally sell for \$1.50 each and that's in big quantities! We're crazy to sell 'em so cheap!!

0131297R 50pcs .....\$19.95  
0131297 500pcs .....\$99.95

## Laser Fiber Optic Transmitter

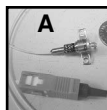

Brand new HP Agilent model LST2829 Laser transmitter module. Capable of 622 MB/s data rates, 1 mW output power, 1300 nm wavelength, includes on chip power monitor diode. These are high end quality lasers and not often found on the surplus market! Two style available, A: 32" long thin pigtail fiber and B: 16" long encased fiber. Each has the

same electrical specs. Price: \$9.95 each  
Item A: 0128526R Item B: 0128536R

## Cellphone CMOS Camera Module



Wow! Here's the guts of the camera in all the new cellphones. Brand new assemblies made by PicTos, model 0187837M11.

Camera head has neat rotating head and snazzy look. Flexible circuit board has tiny connector on end for hook up. Opening the camera head reveals a super tiny single chip camera IC that is only 3/8" square including built in lens! Sorry we have no specs on this unit, but should be easy to research on the net or with a scope.

0128842R .....\$8.95

## Tool Set



Well made quality 3 piece plier set. Includes deluxe padded zipper case. Pliers are big 8" in size, you get: needlenose, diagonal and lineman style with handy crimper and stripper dies on each tool! Get a few for the car, gifts and toolbox, they are that nice!

0128871R .....\$12.95



## Truck Stereo

New in dash cassette stereo AM/FM radio, LCD display, drives 4 speakers (80 watts!) Even has Weather band! Quality fully enclosed case, easy hookup, great for in wall home installations! Runs on 12 VDC.

0128872R .....\$29.95




## Ion Generator

Build your own Ion Breeze air purifier! New module, 120 VAC in, 7.5KV out! Surplus from air cleaner maker who sold them for \$200!

0128873R .....\$7.95


## Cellular Bi Directional Amp

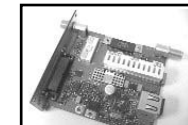

Super rugged unit features powerful 3 watt RF amplifier for transmit and sensitive receive amplifier. Utilizes duplexer ceramic filters. Additional circuitry for protection, regulation, etc. Sorry, we have no specs on this, but it's a treasure trove for the experimenter and RF guru. Brand new. Size: 4.5 x 5 x 1.5" in rugged extruded aluminum heat sink style case. Uses mini UHF connectors.

0127460R .....\$14.95

## Rechargeable Battery Blowout!

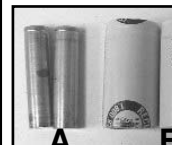


Popular Nicad batteries. 1.25V all brand new, recent stock. A & B are NiCad and C is NiMH.  
A: AAA 400mah 0125339R 2 for \$1.00  
B: Sub C 2500 mah 0125443R 2 for \$1.75  
C: 3.6 Volts 750mah 0125348R 2 for \$3.00



Nice, new 5 AA cell nicad pack. 6 Volt 700mah with 6" wire leads. Great for projects or cordless phone replacements.



0125345R .....\$2.50

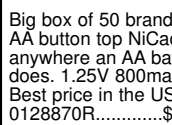

Big box of 50 brand new AA button top NiCads. Fit anywhere an AA battery does. 1.25V 800mah. Best price in the USA!

0128870R .....\$19.95

## Lithium Ion Rechargeables !!

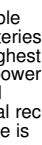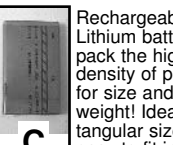

Rechargeable Lithium batteries pack the highest density of power for size and weight! Ideal rectangular size is easy to fit in your project. All 3.6 Volt and approx rated Amp Hour capacity.  
A: 1Ah 1.95x1.34x.4" 0125337R .....\$1.50  
B: .8Ah 1.95x1.34x.25" 0125349R .....\$1.25  
C: .8Ah 1.95x1.24x.23" 0125350R .....\$1.25

# Windsor

WINDSOR DISTRIBUTORS COMPANY

19 Freeman Street

Newark, New Jersey 07105 3708

Ph: 973 344 5700 Fax: 973 344 3282



**ORDERING INFO:** Shipping and insurance charges made after order is packed. You will be notified by Email. Orders under \$25 add \$5.00 small order fee. Credit cards will only be authorized on US and Canadian banks. Please contact Windsor regarding payment instructions for other countries.

Check our web site for more great deals!

[www.shopatwindsor.com](http://www.shopatwindsor.com)

Approaching the Final Frontier

# Near Space

## Adapting Cell Phone Battery Cells for Near Space Use

**D**ue to the extreme cold of near space (NS), hobbyists must be careful when selecting power sources for their NS craft. On one or two occasions, I have lost track of a NS craft, apparently due to cold batteries. To reduce this risk, most of us involved in amateur NS use lithium cells, which can be rated to -60° F.

My source of these cells is S & G Photographics or Fair Radio Sales. These cells come from surplus military battery packs. Each package contains either five or 10 cells that are either D cells or a slightly shortened version thereof. The only risk I face using these surplus cells is that they are 10 years beyond their expiration date. Since the cells are based on a lithium sulfate chemistry, they self-discharge very slowly and still retain most of their original capacity, but — every once in a while — I'll find a bad cell.

If I discover a bad cell before I assemble the battery pack, that's fine. It's the possibility of discovering a bad cell during a mission that has me worried, so I've kept my eye open for an alternative. One alternative is

using rechargeable cells that aren't sensitive to cold temperatures. NSTAR's Mark Conner has had success with NiHM cells, for example. However, I hesitate to use NiCd's and NiMH's because of their memory effect.

Recently, hobbyists have been able to purchase cell phone batteries through surplus electronics dealers. These batteries use a lithium-ion chemistry, so they're reasonably energy dense (high capacity for their size and weight) and rechargeable. Batteries this good are usually expensive (just wait until you have to replace your cell phone battery), but now that they can be purchased surplus, their cost has become very reasonable.

I purchased several 7.2 V 1,200 mAH batteries from All Electronics for \$6.50 each (part number LBAT-35) and the charger for \$4.50 (part number BC-9). Being lithium-ion batteries, they don't suffer from the memory effect found in NiCd's and they are less susceptible to failure due to cold temperatures. On the negative side, however, is the fact that they are designed for cell phone battery compartments. The battery connector found in a cell phone is not very friendly for use in NS or robotics projects.

In this month's column, I'll describe how you can adapt these inexpensive batteries for your projects. The modification is simple and — when you're done — you'll have a great rechargeable battery to use

in your robotic or NS projects.

### Battery Mod

The cells for this battery are sealed in a hard plastic case. Two "springy" metal pins in the cell phone battery case make contact with the metal tabs molded into the battery case. Since I couldn't find a battery holder for cell phone batteries at my local RadioShack, I decided to modify the electrical connection to the battery to suit my needs. Figure 1 shows what the battery looked like before the modification. The cap covering the battery's tabs prevents short circuits when carrying a charged battery in your pocket.

#### Materials

- Two lengths of 12 gauge, stranded wire (use red and black)
- Note:* I used the silicon rubber insulated wire available at R/C car stores
- 2" diameter heat shrink tubing and heat gun
- Two connectors suitable for your projects *Note:* I used a pair of Anderson Power Pole connectors
- Solder and soldering iron
- Wire cutters and strippers
- Electrician's tape
- Masking tape

#### Procedure

First, a few words of warning. Do not charge your battery before making this modification. Also, watch that you do not accidentally short the battery while modifying it. The modification is safe, but you

**Figure 1.** The cell phone battery in its native state.





need to watch what you are doing.

This modification involves soldering two #12 AWG gauge wires to the battery's tabs and then covering the exposed connection with tape and heat shrink.

So, begin by firing up your soldering iron. After it warms up, apply a thin coat of solder to the entire exposed surface of the electrical contacts of the lithium-ion battery. Do this quickly, as you don't want to heat the metal contacts any longer than necessary. The battery chemistry may not respond favorably to high heat and you certainly do not want to melt the plastic case. I found that the gold-colored contacts soldered very easily.

Cut a red and a black wire to the same length. These wires will become the battery's new power cable, so select the power connectors you plan to use and crimp and/or solder them to one end of each wire. It's easier to terminate your wires now than later, when the battery is hanging from the other end. In my example, I cut my wires 4" long and crimped Anderson Power Poles on the ends.

Strip between 1/8" and 1/4" of insulation from the other ends of the two wires. Bend the ends of the exposed wires at right angles where the insulation ends and tin the exposed ends with solder. Watch out — the wires will stay hot for a while, so be careful when you handle them.

Look at the front of the battery and beneath the tinned electrical contacts. There, you'll see a small positive and a small negative mark imprinted on the plastic battery case. These represent the polarization of the electrical contacts. After determining the polarization of the tinned contacts, solder the wires onto the battery contact. Be sure you solder the red wire to the positive contact and the black wire to the negative contact.

To solder the wires to the battery, I recommend laying a 12 gauge wire on the front of the battery case with its tinned end touching a tinned battery contact. Wrap a strip of masking

tape around the battery and wire to hold them together while you solder the wire to the battery contact. When soldering the wire to the contact, quickly apply a well-tinned soldering iron to the wire and battery contact. The solder in the tinned wire and battery contact will melt and fuse together. Remove the soldering iron as soon as the connection is made. Repeat the process on the other wire.

Once the solder has cooled, cut two pieces of electrician's tape and cover the exposed solder joints on the top of the battery. Cut the tape long enough to not only cover the top of the battery, but also to partially cover the sides of the battery. For good measure, wrap a strip of electrician's tape around the top of the battery and cover the ends of the first two strips.

Finish the battery modification by cutting a 2-1/2" length of 2" diameter heat shrink tubing. Slide the tubing over the battery and fully cover both the body of the battery and the ends of the electrician's tape that was used to cover the solder on the battery. Shrink the tubing down.



**Figure 2.** The modified lithium-ion cell phone battery. Now you can use these great and inexpensive batteries in your hobbies.

When completed, your battery should look like the one in Figure 2. Repeat this modification for the rest of your cell phone batteries.


## Charger Mod

Once a battery has been modified, it can no longer charge on its original charger, so let's modify that, too.

### Materials

- Small Phillips screwdriver
- 22 gauge stranded wire (in red and black)
- 3/16" heat shrink tubing
- Power connectors to mate to the
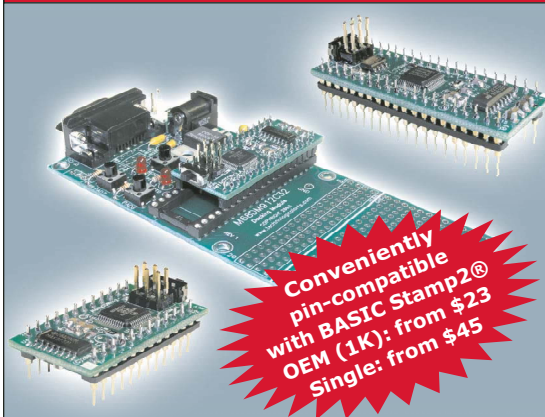
## NanoCore12™ for best performance and price! 9S12C microcontroller modules starting at \$45!




Conveniently  
pin-compatible  
with BASIC Stamp2®  
OEM (1K): from \$23  
Single: from \$45

### NanoCore12™ Features:

- on-board RS232C interface
- up to 33 I/O lines, with multi-property programmability (e.g. direction, pull-up/pull-down, reduced drive, invert polarity, etc.)
- up to 8 key wake-up interrupt inputs, with digital filtering
- SCI • SPI • CAN
- 8-channel 10-bit ADCs
- multiple PWM channels
- 4-channel timers, supporting input capture/output compare, event counting, gated time accumulation, and simple PWM
- 32K multi-sector Flash • 2K RAM
- operates up to 48MHz via PLL
- 3.3 V or 5 V operation
- advanced CISC architecture
- on-chip Serial Monitor
- supports BDM debugging

**www.technologicalarts.com**  
**Toll-free: 1-877-963-8996**  
**(USA & Canada)**

™ NanoCore12 is a trademark of Technological Arts, Inc.  
© BASIC Stamp is a registered trademark of Parallax, Inc.

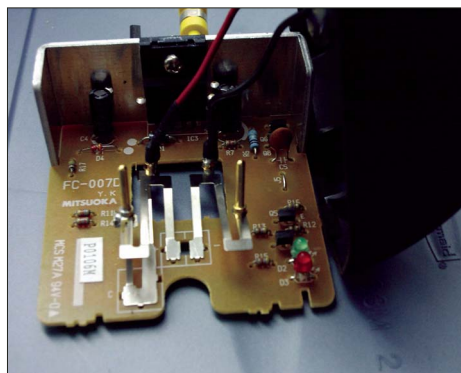

**Figure 3.** This is what the inside of my charger looks like.

power connectors in the modified battery

- Wire cutters and strippers
- Solder and a soldering iron
- Heatsink clip or other small clamp

## Procedure

It shouldn't be necessary to say this, but please make this modification while the charger's wall wart is

disconnected from the charger base. Under no circumstances should you make this modification while the charger is plugged into the wall.

Look at the pocket of the charger. You will see two pairs of metal pins. Two metal pins make an electrical connection with the battery and the two other metal pins detect the presence of the battery. Unless a battery is pressed into the charger pocket, the charging pins are not pressed into contact with the charge circuit. In this way, there is no voltage present at the charging pins when the battery is not located in the pocket. It's been a while since I modified my charger, but this is how I made it.

The case of the charger is held together with two Phillips screws located in the bottom of the charger case. Remove these two screws and the case should pop open. The two bottom pins (the battery detecting pins) pull right through the holes

in the case. The charging pins also pulled out of the case when I opened it.

Now, look inside the charger and identify the two pairs of leaf springs containing the two battery detecting pins and the two charging pins. The top leaf spring contains the battery detecting pins that protrude from the bottom two holes of the charger pocket. The bottom leaf spring is connected to the two charging pins that protrude from the top two holes of the charger pocket. Notice that the two leaf springs form the switch inside the plastic case that lets current flow into the cell phone battery when it is dropped into the charger pocket.

The first modification to make involves soldering the two leaf springs together so there's always power from the recharge circuit. Use a heatsink clamp and clamp the top and bottom leaves together on the side of the springs where the battery sensing

## Surplus Sales of Nebraska

### Gray Power Cord (COL) 368-0110-00



BELDEN UL / CSA rated SJT cord. 18/3, molded plug. Collins gray. 10 amp / 10 foot long.

**\$14.00 each**

### 8 foot Cheater Cord (WCC) CHEATCORD



Socket end 2 round pins, same size, non polarized. AC cord 2 blade, non polarized. UL Listed. 16 gauge rated at 7 amps.

**\$1.00 each**

### Leviton AC Outlet (CNE) LEV-1



15 amp, pre-wired grounded AC outlet. Snaps into 15/16" square hole. Leviton brand.

**\$1.50 each**

### 3 Blade Receptacle (CNE) EAC309



AC socket fits all 3 blade business machine style PH-386 plugs. Fits in 7/8" x 1-1/4" hole. Mounting holes are on 1-5/8" centers.

**\$1.25 each**

### Silver Bearing Solder (ADH) 24-7040-8807



Silver Bearing, Lead-Free High Temperature Solder made by Kester. 221°C melting point. 1 lb roll. .020" diameter wire.

**\$25.00 per roll**

**Please visit our website with over 2,000 pages and 10,000 images • [www.surplussales.com](http://www.surplussales.com)**



**Power Supplies:** Low Voltage, High Voltage, Lighting, Precision.



**Teflon® Wire:** From 10 gauge to 26 gauge



**Heatsinks:** All Sizes and Shapes. Large Quantities for Manufacturers



**Telephones:** Rotary, Touch-Tone, Multi-Line, etc.



**Fingerstock:** Over 20 styles and sizes



**HI Manuals:** 1,000s of radio, military and test equipment manuals on hand!!



**Fujitsu Pen Computers**



**Motors & Pumps:** Synchronous, gear reduction, projector motors, etc.



**Transformers:** High & Low voltage, chokes.



**Rotary Switches:** Ceramic, phenolic.



**Vacuum Tubes:** Over 1,000,000 vacuum tubes in stock!!



**Variacs:** From 3 amps to 245 amps.



**Split Beads:** For are all of your interference problems.



**EMI / RFI Filters:** Single Phase / Three Phase & Single Lead styles.



**High Impact Shipping Containers**

1502 Jones Street, Omaha, NE 68102 • Fax: 402-346-2939 • e-mail: [grinnell@surplussales.com](mailto:grinnell@surplussales.com) • Visa, Mastercard, American Express or Discover  
Call or e-mail for shipping and total charges. All SPECIALS in this Ad only good for 30 day advertising cycle. No exceptions please.

Visit our website @  
**[www.surplussales.com](http://www.surplussales.com)**

**800-244-4567 • 402-346-4750**



pins are closed to the leaf contacts (in my charger, this is on the left side of the leaves). Now, solder the leaves together (the leaves appear to be made of brass). After the solder cools, remove the heatsink clamp. The leaves will remain in contact if the soldered connection is good.

The next step is to connect wires and connectors to the charger that can interface with the modified cell phone battery. Cut two lengths of wire (red and black) about 8" long. For my charger, I used #22 AWG stranded wire. We can get by with thinner gauge wire on the charger unit than on the battery because the charger recharges the battery at a low current, whereas the battery may be discharged at a high current.

Crimp and/or solder the same type of connectors used in the battery mod to one end of both wires. Now strip about 1/4" of insulation from the other ends of each wire and tin them.

Slide a short length of heat shrink tubing over the wires and push them away from the bare ends of the wires and close to the crimped connectors on the other end (you want to keep the heat shrink away from where you will be soldering). Thoroughly tin the battery charging pins.

If the front of the charger is pointed at you (the front of the charger has the two LED indicators), then the right charging pin is negative and the left charging pin is positive. You can verify this by looking at the charging circuit's PCB silk screening.

Pass the two #22 AWG gauge wires through the two charging pin holes in the pocket of the charger case. Be sure to pass the black wire through the right hole and the red wire through the left hole. Press one of the tinned ends of wire into contact with a tinned charging pin and heat both of them with a well-tinned soldering iron. Hold the wire in place until



**Figure 4.** With the case closed, the charger "almost" looks normal.

the solder cools. Repeat the same thing with the other pin. Once the solder cools, slide the heat shrink over the soldered connection and shrink.

Now, you can close the charger case. Be sure a wire doesn't get pinched in the case.

I have used my new batteries twice on NS missions and, so far, I'm pleased with the results. **NV**

## Turn Your Interest Into Income!

**Get a Good Paying Job in Industrial Electronics  
...We Train You at Home in Your Spare Time**

Turn your hobby into a career you enjoy! A high-demand career that offers a stable future and pays top dollar. No night school, no travel. You do it at home using our government approved distance learning system. Includes one-on-one consultations, valuable International Society of Certified Electronics Technicians training, bench skills, professional instruments you keep and use on the job. Check us out!

- Industrial Robotics
- Numerical Control Machine Tools
- Computer Integrated Manufacturing Systems
- Process Controls
- Flexible Manufacturing Systems



### For FREE Brochure

Call Toll-Free  
**1.800.658.1180**  
or visit [www.aiilearn.com](http://www.aiilearn.com)

If using coupon, please print all information clearly.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

or Mail Coupon  
Atlantic International Institute  
Department 1-045  
2725 College Street  
Jacksonville, FL 32205

## DATA ACQUISITION INVENTORY CONTROL

### GOING WIRELESS IS EASY!

#### BLUETOOTH MODULES - RS-232

Low Cost  
Easy To Use



Long Range  
Class I & II

#### 900 MHz WIRELESS RF MODULES

Transmitters, Receivers, Transceivers,  
High Speed, Long Range, UHF Modems



Call Toll Free 866-345-3667

## LE MOS

INTERNATIONAL  
Electronic Manufacturers Representatives  
RF & Microwave Specialists

[www.lemosint.com](http://www.lemosint.com)

UHF MODEMS  
RS-232  
REMOTE CONTROL

INDUSTRIAL APPLICATIONS  
DATA LOGGERS



**SERIAL LCD DISPLAYS**

**NEW!**

- packed with features
- total control / easy to use
- very low power

See the SMARD4™ at [www.cruxanalysis.com](http://www.cruxanalysis.com)

**EARTH.LCD.COM**

See the *World's Largest* Collection of *LCDs* and *LCD Products*

**superbrightleds.com**

**LEDs    LED Bulbs    LED Products**


**[www.gatewayelectronics.com](http://www.gatewayelectronics.com)**

(Electronically Speaking, Gateway's Got It!)

MAIL ORDERS CALL TOLL-FREE-1-800-669-5810

Save up to **60%** on electronic components and microcontrollers

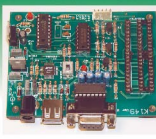**[www.futurlec.com](http://www.futurlec.com)**



**USB/Serial Pic Programmer Kit \$34.95**

- \* Free software and updates Windows 9x/2000/Nt/XP
- \* Quality PCB and Silkscreen for easy assembly

See all of our Educational Electronic Kits visit us at [www.ElectronicKits.com](http://www.ElectronicKits.com)

Bus Embedded Internet PC RTOS CAN-Bus Embedded Internet PC RTOS CA

**CCS C Compiler**

For the PIC® MCU

262-797-0455

[www.ccsinfo.com/env](http://www.ccsinfo.com/env)

**ramsey**

[www.ramseykits.com](http://www.ramseykits.com)

AM/FM Broadcasters • Hobby Kits  
Learning Kits • Test Equipment  
...AND LOTS OF NEAT STUFF!

**audioX PRESS**

[www.audioxpress.com](http://www.audioxpress.com)

For the do-it-yourself audio enthusiast...

- Helpful articles
- Hands-on projects
- Expert advice
- New technologies

12 issues just \$29.95 — save \$54!

Subscribe & Save 65%!

Call 1-888-924-9465 to subscribe today!

Your BASIC Stamp Headquarters

**PARALLAX**

[www.parallax.com](http://www.parallax.com)

**USB** Add USB to your next project— it's easier than you might think!

**DLP Design**

- USB-FIFO • USB-UART • USB/Microcontroller boards

Absolutely NO driver software development required!

[www.dlpdesign.com](http://www.dlpdesign.com)    Design services available

**C&S SALES**

The one-stop source for all electronic needs!

**[www.cs-sales.com](http://www.cs-sales.com)**

**Geiger Counters:**  
Digital, PC & Analog

As sold to **NASA** and **US Government**

**IMAGES SI INC.**

[www.imagesco.com/geiger](http://www.imagesco.com/geiger)

**MCUmart.com**

PICmicro MCU Development Tools

**BASIC Compilers**  
Device Programmers  
Prototyping Boards  
Experimenter Boards  
Books



*World's Smallest Ethernet Web Server*

**[www.netmedia.com](http://www.netmedia.com)**

**electronicsurplus.com**

**ONE PASSircuit™**

"The Future of Proto-typing"

[www.onepasinc.com](http://www.onepasinc.com)

**[www.CircuitSpecialists.com](http://www.CircuitSpecialists.com)**

OVER 8,000 ELECTRONIC ITEMS ONLINE!  
Deals You Won't Believe!



# Remember when...

*...electronics stores were stocked to the rafters  
with every component imaginable and there was ALWAYS  
a knowledgeable person there to help you?*



*My friend Jim at his  
electronics shop, 1983*



**Think those days are gone?**

**Well they're not!**

**You just need a little Jameco@Home.**

**Call for a FREE catalog today.**

 **@ HOME  
JAMECO®**  
1-800-455-6119

We have the electronic components and knowledgeable Technical Support people who can help **bring back the fun** in your electronics hobbies, inventions, and DIY projects.

Be sure to visit our new website at  
**[www.Jameco.com/nvb](http://www.Jameco.com/nvb)**

**Jameco@Home**  
—where electronics is still fun!

Electronic Theories and Applications From A to Z

# Let's Get Technical

## Hop, Skip, and Jump — Pseudo-Random Frequency Hopping

Everyone seems to be jumping onto the wireless networking bandwagon. With more and more devices going wireless, the airwaves are constantly filled with numerous digital “conversations.” For ordinary, law abiding wireless users, the congestion is handled using a wireless protocol that allows for reliable communication in a noisy, competitive environment.

However, due to the broadcast nature of wireless networking, other users may try to tap into the wireless network, eavesdropping on the flow of information and looking for useful data.

How, then, can a user enjoy a sense of privacy when using a

wireless device? Certainly, we can encrypt the data so that — if intercepted — its meaning remains hidden. For strong encryption, a key with many bits must be used; this, in turn, requires a large set of calculations. Without a fast, dedicated processor, strong encryption may not be feasible for many applications, particularly mobile wireless devices.

One electronic method of providing privacy to a transmitted signal is called Frequency Hopping. In this method, a band of frequencies is broken up into several smaller bands.

After a portion of information is transmitted at one frequency, the transmitter changes frequencies


and continues transmission. When changing frequencies, the transmitter randomly (at least it appears random) selects a new frequency from the set of frequencies in the band.

By choosing a random frequency to jump to for each new transmission, anyone listening in to the transmission must also switch to the new frequency or lose reception of the information.

If enough frequencies are used and the hopping around is composed of a large number of jumps, it will be very difficult for the eavesdropper to receive a valid stream of information.

Figure 1 shows a simple circuit that generates a pseudo-random

**Figure 1.** Pseudo-random frequency hopping circuit. The first 555 timer clocks the four-bit shift register. The XNOR feedback circuit helps the shift register generate a 15 pattern sequence. Each pattern causes the second 555 timer to oscillate at a different frequency.

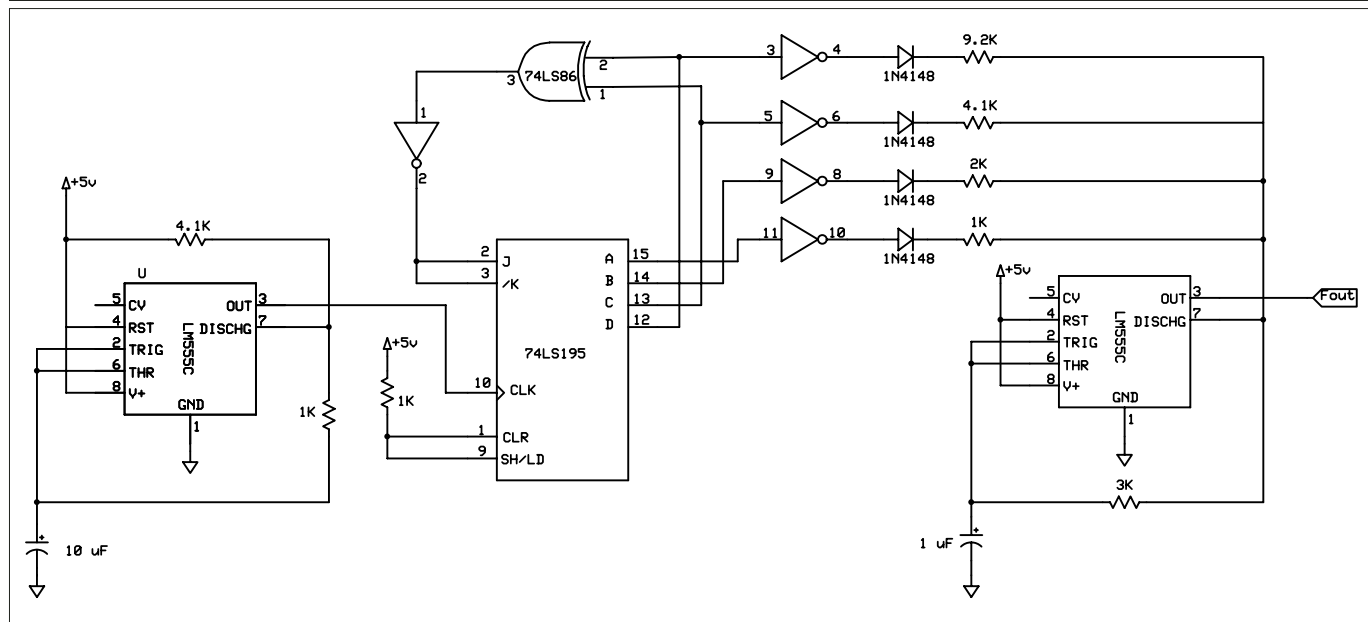



sequence of 15 different frequencies, as indicated in Table 1. An Exclusive NOR (XNOR) feedback circuit uses the last two bits of a four-bit shift register to determine the next bit clocked into the shift register. Each new bit clocked into the shift register causes the four-bit output pattern to change.

Note the seemingly random sequence at the DCBA outputs. It is not really random, since the same 15 pattern sequence will repeat over and over. This is because, when the outputs are 0001, the next output will be 0000, which is where we started.

So, the four-bit shift register provides 15 patterns. A five-bit shift register could provide 31 patterns. A 16-bit shift register could provide 65,535 patterns, none of which are the same, with the entire sequence repeating every 65,535 patterns. That would probably be secure enough.

| Pattern | Output<br>D C B A | Decimal<br>Value | Frequency (Hz) | Direction of<br>Change |
|---------|-------------------|------------------|----------------|------------------------|
| 1       | 0 0 0 0           | 0                | 219            | N/A                    |
| 2       | 1 0 0 0           | 8                | 218            | Down                   |
| 3       | 1 1 0 0           | 12               | 215            | Down                   |
| 4       | 1 1 1 0           | 14               | 204            | Down                   |
| 5       | 0 1 1 1           | 7                | 94             | Down                   |
| 6       | 1 0 1 1           | 11               | 142            | Up                     |
| 7       | 1 1 0 1           | 13               | 179            | Up                     |
| 8       | 0 1 1 0           | 6                | 207            | Up                     |
| 9       | 0 0 1 1           | 3                | 162            | Down                   |
| 10      | 1 0 0 1           | 9                | 195            | Up                     |
| 11      | 0 1 0 0           | 4                | 216            | Up                     |
| 12      | 1 0 1 0           | 10               | 210            | Down                   |
| 13      | 0 1 0 1           | 5                | 187            | Down                   |
| 14      | 0 0 1 0           | 2                | 212            | Up                     |
| 15      | 0 0 0 1           | 1                | 199            | Down                   |

**Table 1.** Output sequence of the frequency hopping circuit with associated output frequencies. This group of 15 patterns repeats endlessly.

The inverters are used to provide a little extra current drive to the second 555 timer circuit. The diodes allow the resistors to be connected in parallel whenever the associated inverter output is high. With 15 different output patterns,

there will be 15 different combinations of the four frequency resistors, which — in turn — leads to 15 different timing scenarios for the second 555 timer.

Look at Figure 2 to see a student's breadboard of the frequency

## ELECTRONIX EXPRESS

Visit Our Website At <http://www.elexp.com>


|  |  |  |   |
|--|--|--|---|
| <b>RSR 3MHZ SWEEP FUNCTION GENERATORS</b><br>6 Waveform Functions, Int/Ext Counter, lin/log sweep<br><b>MODEL FG-30</b> (No Digital Display) <b>\$120<sup>00</sup></b><br><b>MODEL FG-32</b> (5 Digit Display) <b>\$185<sup>00</sup></b> | <b>INSTEK OSCILLOSCOPE</b><br><b>MODEL GOS-620</b><br>Dual Channel — 20MHZ<br>(INCLUDES PROBES) <b>\$289<sup>00</sup></b>  | <b>DC POWER SUPPLIES</b><br><b>MODEL HY3003</b> — DIGITAL DISPLAY<br>Variable output, 0-30 VDC, 0-3 Amp <b>\$88<sup>00</sup></b><br><b>MODEL HY3003-3</b> — TRIPLE OUTPUT<br>Two 0-30 VDC, 0-3 Amp variable outputs plus 5V 3A fixed. Digital Display. <b>\$175<sup>00</sup></b>             | <b>Weller® SOLDERING STATION</b><br><b>#1 BEST SELLING STATION</b> <b>\$36<sup>95</sup></b><br><b>MODEL WLC 100</b><br>V0603WLC100  |
| <b>BENCH DMM WITH RS232 INTERFACE</b><br><b>MODEL DM9803R</b><br>True RMS, digital and bar graph display, AC/DC Cap, Res, frequency functions. Includes software, AC or DC operation. <b>\$99<sup>00</sup></b>                           | <b>DIGITAL MULTIMETER</b><br>32 Ranges — 3 1/2 Digit<br><b>MODEL MY-64</b> <b>\$27<sup>95</sup></b><br>AC/DC Volt/Current, Res. Cap., Frequency. Rubber Holster Included           | <b>ALLIGATOR LEADS</b><br><b>SET OF 10</b> <b>\$2<sup>10</sup></b><br><b>SOUND SENSOR CAR</b><br>REQUIRES SOLDERING<br>Reverses direction whenever it detects noise, or touches an obstacle. <b>\$8<sup>95</sup></b><br>#V3221881  | <b>RSR HIGH PERFORMANCE 3-WIRE IRON</b><br><b>#V060509</b> <b>\$5<sup>50</sup></b><br><b>RSR DIGITAL MULTIMETER</b> <b>\$52<sup>50</sup></b><br><b>ECONOMY MODEL 820B</b><br>1-9 ..... \$7.50<br>10-49 ... \$6.50<br>#V01DM820B |
| <b>SWITCHES</b><br>8 POS DIP (V17DIP8SS) 1-9 .90 10-99 .85 100+ .70<br>Toggle Mini SPDT (V17TOGSD-M) 1.15 .95 .70<br>Toggle Mini DPDT (V17TOGDD-M) \$1.30 1.10 .90   | <b>POTENTIOMETERS</b><br>Cermet (STS Series) 1-9 85¢ 10-99 75¢ 100+ 65¢<br>Multiturn (MTT Series) 85¢ 75¢ 55¢<br>Panel Mount (PMA Series) 95¢ 65¢ 55¢<br>Standard Values Available | <b>ROTARY TOOL KIT</b> <b>\$33<sup>95</sup></b><br>Variable speed tool (37,000 RPM) with accessory kit in a hard plastic carry case. #V29DR101<br><div style="border: 1px solid black; padding: 5px; text-align: center;"> <b>MORE Low-Priced Items In Our FREE 300+ Page Catalog</b> </div> |   |

TERMS: Min. \$20 + shipping. School Purchase Orders, VISA/ MC, Money Order, Prepaid. NO PERSONAL CHECKS, NO COD. NJ Residents: Add 6% Sales Tax.

**In NJ: 732-381-8020**  
**FAX: 732-381-1006**

**365 Blair Road • Avenel, NJ 07001-2293**  
**800-972-2225**

**<http://www.elexp.com>**  
**email: [electron@elexp.com](mailto:electron@elexp.com)**

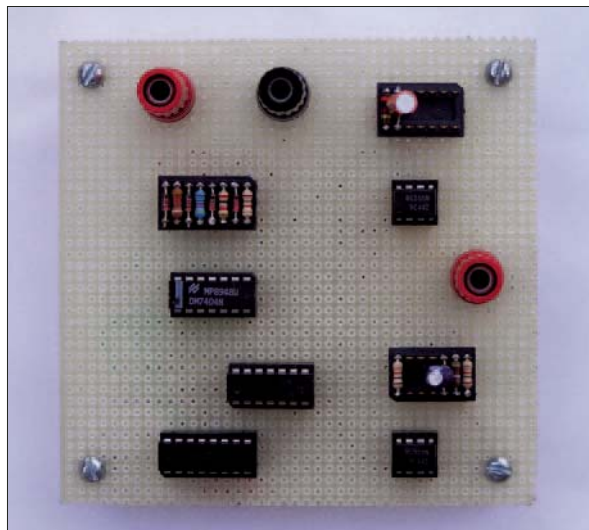

**Figure 2.** An actual frequency hopping circuit, wire-wrapped on a breadboard.

hopping circuit. In just one afternoon, the student was introduced to the topic during lecture and the circuit was breadboarded and tested in lab.

One problem with the range of generated frequencies in Table 1 is the distribution.

Notice that some frequency changes between output patterns are very small (just 1 Hz between patterns 1 and 2, for example). The four frequency resistors need to be adjusted in this case. The entire set of generated frequencies will change, so a little experimentation or work with the 555 timer equation will be necessary to obtain the desired frequency spread.

One last point deserves mention. What happens if the shift register begins with an initial pattern of 1111? Through the feedback circuit, another 1 will get clocked in, making the next pattern 1111, the

same as the last pattern.

This is an illegal state for the pseudo-random sequencer to start in because it can never get out of it. In addition — due to the inverters — there will be no resistance to pin 7 of the second 555 timer, which would prevent oscillation during the 1111 pattern. A power-on reset or some other initialization signal is required to prevent the 1111 pattern from appearing. **NV**

## About the Author

*James Antonakos is a Professor in the Departments of Electrical Engineering Technology and Computer Studies at Broome Community College. He is also the author of numerous textbooks on those subjects. You may visit his website at [www.sunybroome.edu/~antonakos\\_j](http://www.sunybroome.edu/~antonakos_j)*

**Why settle for black & white?**

**LCD**

**When you can have COLOR for the same price!**

**EARTHLCD.COM**

ezLCD-001 LCD Display Module

- Easy & affordable color LCD integration
- Color 240x160 2.7" TFT
- Serial+USB+I<sup>2</sup>C+Parallel
- ASCII Graphic/Text Commands
- Downloadable Fonts

**EarthLCD.com** We Make LCDs Work.™

**New electronics software for hobbyists...**

**Livewire** State-of-the-art software for designing and simulating electronic circuits. **NEW**  
Home edition only \$49.99.

**PCB Wizard 3** Highly innovative PCB designer for creating single and double-sided boards. **NEW**  
Home edition only \$49.99.

Dealer enquiries welcome

**For free demonstration software, please visit our website at [www.pulsar.gs/nwc](http://www.pulsar.gs/nwc)**

**PULSAR**, 1947 Sandalwood Place, Clearwater FL 33760-1713  
E-mail: [mail@pulsar.gs](mailto:mail@pulsar.gs) • Order line: (727) 524-1500  
Technical support: (727) 524-8822 • Fax: (727) 524-1225



# Something "fishy" is going on in Test and Measurement



## **STINGRAY** Dual Channel Oscilloscope, Signal Generator & Multi-Function Instrument

**STINGRAY** is the value-for-money dual-channel PC oscilloscope with signal generator, data logger, spectrum analyzer, voltmeter and frequency meter capabilities. Despite its low cost, **STINGRAY** offers a wealth of features including 1M S/s sampling with 12-bit conversion, advanced digital trigger modes, AC/DC coupling and a built-in signal generator with 10 bit resolution.

**STINGRAY**  
only \$199



## **STINGRAY** Features

- Dual-channel standard BNC input connectors
- 12-bit simultaneous ADC sampling on both channels
- 20M S/s sampling rate (repetitive) 1M S/s native
- Signal Generator Output/External Trigger Input
- Maximum input voltage +/- 50V
- AC/DC Coupling
- Edge, min/max pulse width and delayed trigger modes
- Analog Bandwidth 200KHz
- Self-Powered USB Interface - no external PSU required
- 3rd Party application software support provided
- Hardware upgradeable over USB
- Dimensions: W: 116mm x H: 30mm x D: 100mm
- Weight: 5oz without cable


## **SWORDFISH** Hand Held USB Oscilloscope

A unique hand-held device that combines the functions of an oscilloscope, data logger, spectrum analyzer, voltmeter and frequency meter in a single instrument. **SWORDFISH** features a user-replaceable precision spring-loaded probe tip which can be used to probe even small SMD components. The probe cap can be removed to allow **SWORDFISH** to connect to standard oscilloscope probes or BNC cables if required. **SWORDFISH** comes complete with oscilloscope and data logging software. Supplied Windows DLL's allow 3rd party applications use. Sample code in several popular programming languages are provided. Windows CE and Linux drivers are also available upon request.

## **SWORDFISH** Features

- 10 Bit ADC Resolution
- 1G S/s sampling rate (repetitive) 40M S/s native
- Maximum input voltage +/- 50V
- AC/DC Coupling
- Edge, min/max pulse width and delayed trigger modes
- Analog Bandwidth 5MHz
- Self Powered USB Interface - no external PSU required
- Precision spring-loaded probe tip or standard BNC connection
- 3rd Party application software support provided
- Hardware upgradeable over USB
- Dimensions: W: 34mm x H: 24mm x D: 240mm excluding USB cable
- Weight: 5oz with cable

**SWORDFISH**  
only \$245

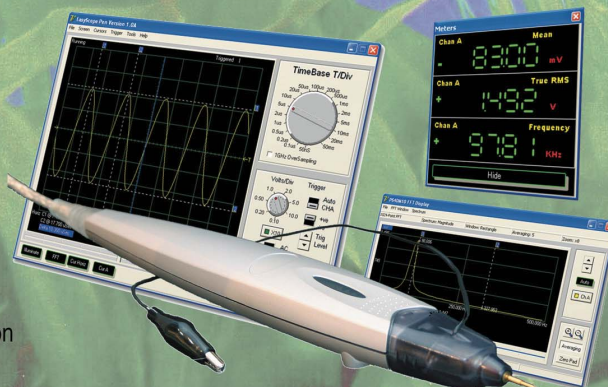

Detailed specifications, information and downloads at [www.usb-instruments.com](http://www.usb-instruments.com)

**Saelig Co Inc** 1160-D2 Pittsford-Victor Road Pittsford NY 14534 USA T: 585-385-1750 F: 585-385-1768  
[info@saelig.com](mailto:info@saelig.com) [www.saelig.com/ad/cctestfish.htm](http://www.saelig.com/ad/cctestfish.htm)

**NEW!**



## CURRENT TRANSFORMERS FIT SMALL FOOTPRINT WITH VARIOUS MOUNTING OPTIONS

**A** new line of current transformers from Foster Transformer features compact construction and multiple mounting options to meet any design parameter. They are ideal for use in motor control applications, UPS systems, appliances, or any application where isolated current monitoring is desirable.

Standard models feature a 1:500 turn ratio and handle rated currents from 0.1 to 30.0 amps. Operating frequency range is from 50 Hz to 400 Hz.

Each size and model includes UL Recognized Class 130 (B) insulation. Optional 1/4" quick connect terminals keep high current off of the printed circuit board and simplify connections. Pricing starts at \$1.10 each in 1,000 piece quantities.


For more information, contact:

### FOSTER TRANSFORMER

3820 Colerain Ave.  
Cincinnati, OH 45223  
Tel: **800-963-9799**

Email: **info@foster-transformer.com**  
Web: **www.foster-transformer.com**


Circle #110 on the Reader Service Card.

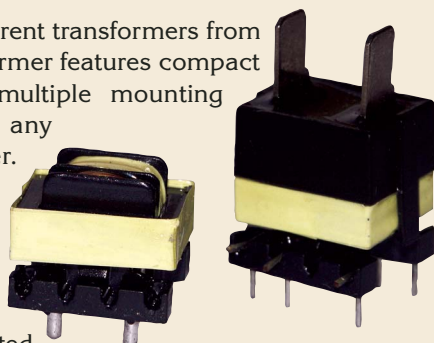
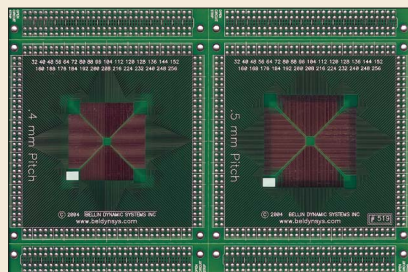
## UNIVERSAL QUAD SMT ADAPTERS

**B**ellin Dynamic Systems, Inc., announced the latest Snap-Apart™ adapter board — the P519. The P519 is a Universal Quad Adapter that will work with most SMT Quad ICs on .4 or .5 mm spacing. It is designed to carry Quad ICs with 32 to 256 leads. Each adapter takes SMT Quad chips and breaks out the leads into dual row, .100" header pins. The kit holds one Snap-Apart board with two adapters and eight 80-pin .100" header strips. The P519 is a quick and economical solution to Quad SMT prototyping.

Pictures, product information, and printable data fit check sheets are available at Bellin's website. The P519 is



currently available for \$59.95 each.

For more information, contact:

### BELLIN DYNAMIC SYSTEMS, INC.

211 S. State College Blvd. #319  
Anaheim, CA 92806

**714-630-8024** Fax: **714-630-8025**

Email: **jsohn@beldynsys.com**

Web: **www.beldynsys.com**

Circle #126 on the Reader Service Card.

## NEW COMPACT POWER PACKAGE

**D**iodes Inc., now has available a New PowerDITM5 Compact Power Package which includes the introduction of new high voltage Schottky barrier rectifiers: PDS3200 and PDS5100H. The new

PowerDITM5 compact, low profile package — with its patent-pending flat lead frame and heatsink solder pad — offers higher power dissipation and surge capabilities.

The new components occupy only 26.7 mm<sup>2</sup> of printed circuit board (PCB) area while offering higher power dissipation. It also delivers major improvements for compact applications where circuit board space is at a premium.

With this new product release, Diodes, Inc., continues to extend its product range of subminiature discretes and arrays benefiting automotive devices, power conversion, industrial, server and network applications, and more.

For more information, contact:

### DIODES, INC.

**805-446-4800** Fax: **805-381-3838**

Web: **www.diodes.com**

Circle #131 on the Reader Service Card.



**PowerDI 5**

## COOLGUARD

**W**eber Sensors, Inc., announces the introduction of CoolGuard.

This first-of-a-kind flow-captor is two sensors in one. It monitors the flow rate and also the temperature of the flowing medium and provides a solidstate switch if flow is lost or temperature is exceeded.

The CoolGuard is solidstate, with no moving parts. In addition, it is the ideal replacement for old fashioned





mechanical flow switches. It won't foul, stick, wear out, or be damaged by excessive flow rates. It can be mounted horizontally or vertically with no effect on the switching point. It has Normally Open "fail safe" switching logic — unlike mechanical switches that often fail, indicating flow is okay when no flow exists. CoolGuard is simple to install and is factory pre-set, so it requires no calibration or adjustment.

Priced right for the OEM as well as the small quantity user, the CoolGuard offers a low cost solution to solidstate flow and temperature monitoring. The CoolGuard — for small quantities — is listed at \$195.00. For higher volume quantities, it is less than \$100.00. Purchase from their website or by phone.

For more information, contact:

## WEBER SENSORS, INC.

2230 Towne Lake Pkwy.

Building 900 #200

Woodstock, GA 30189

Tel: **770-592-6630**

Web: **www.captor.com**

Circle #144 on the Reader Service Card.

## COMPLIANT DEVELOPMENT PLATFORM

OnEarth Solutions Corporation is growing as the IEEE 802.15.4 wireless application platform — a precursor to the emerging ZigBee standard — enables them to assist with custom design projects as you develop or add wireless capabilities to existing products.


They currently offer an IEEE 802.15.4-Compliant Development Platform — OES-ZUSB-1000 — which enables customers — in a rapid and cost-effective manner — to design, develop, and ultimately test scalable wireless networks (e.g., peer-to-peer, star, cluster-tree, and mesh) conducive for low data rate transmission, within the rubric of low power consumption (e.g., multi-month/year battery life).

Additionally, OES-ZUSB-1000 allows for greater ease in adding wireless capabilities to existing products. The OES-ZUSB-1000's hardware, software, and documentation are crafted for personal computer, laptop, or embedded hardware use via

its USB Gateway.

Moreover, OES-ZUSB-1000 contributes to reduced risk for developers, as it has the requisite security features to protect data that is transmitted, while also being fairly immune to RF interference. Indeed, the self-replicating capabilities of a wireless network allow for ever-expanding transmission of data carried out over low frequencies with limited interference. The sensors that come with the OES-ZUSB-1000 allow for viewing respective data in a real time basis — all due to the functioning of the wireless networks.

OES-ZUSB-1000's functionality — while allowing for flexibility and greater productivity — is especially geared for developers in applications that require robust and reliable wireless networks with low power usage for monitoring and control over long distances, often without the need for substantial levels of data transmission (e.g., mostly text, graphics, and Internet) for automation and/or control of the ultimate product.

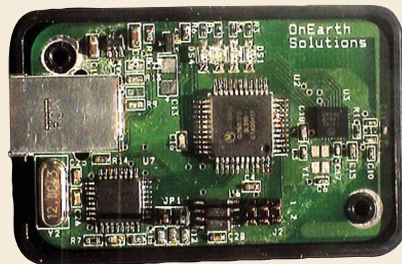


## Learn the basics of programming and networking

# imagnetools.com



reg. \$179  
**\$149**

limited  
time offer

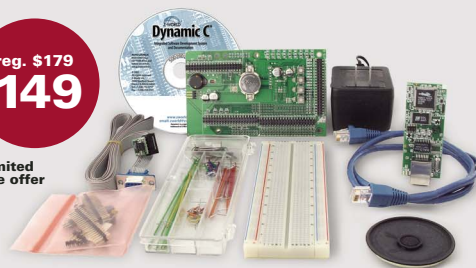

### Ethernet Starter Kit

C-Programmable 8-bit Rabbit 3000® Microprocessor core module with Ethernet, experimentation board, and Dynamic C Lite with compiler, editor, and debugger.

Learn by doing!  
The Imagine Tools™  
Ethernet Starter Kit  
gives you all the  
tools to begin your  
development.

Think  
Learn  
Build



Circle #151 on the Reader Service Card.

Included with the IEEE 802.15.4-compliant Development Platform, OES-ZUSB-1000 is the following:

- One USB-based 802.15.4 radio transceiver.
- Five battery-operated ready sensors (endpoints), which can be configured as radio repeater/router units.
- Selected sensors.
- Software API and development utilities.

This platform allows for the potential integration of 802.15.4 wireless solutions into existing and prospective products. The IEEE 802.15.4-compliant Development Platform, OES-ZUSB-1000, is available for \$2,950.00.

For more information, contact:

## ONEARTH SOLUTIONS CORP.

5284 Randolph Rd. #216

Rockville, MD 20852


**240-221-0256** Fax: **301-299-2142**

Email: [dalexander@onearthsolutions.com](mailto:dalexander@onearthsolutions.com)

Web: [www.onearthsolutions.com](http://www.onearthsolutions.com)

Circle #152 on the Reader Service Card.

## THERMOCOUPLE DATA LOGGER

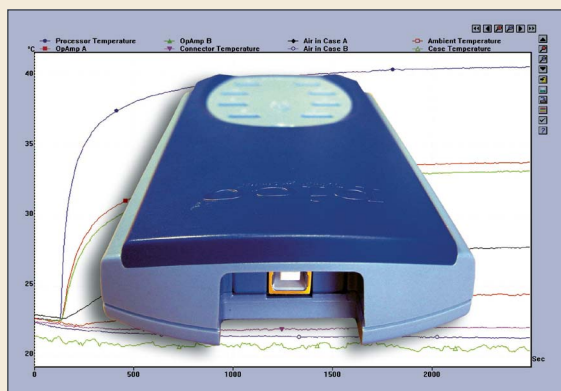

**P**ico Technology — the PC-based test and measurement company — has introduced a USB (v1.1) version of its popular TC-08 eight-channel thermocouple data logger. The new unit samples at up to 10 readings per second (more than twice the speed of the serial port version), features built-in cold junction compensation (CJC), and covers the temperature range of -270 to 1,820 degrees C.

The TC-08 can be used with thermocouple types B, E, J, K, N, R, S, and T and outputs can be viewed in degrees C or mV. The unit is accurate to 0.2 percent  $\pm 0.5$  degrees C and has a resolution of better than 0.1 degrees C for most thermocouple types.

The TC-08's USB connectivity allows multiple units to be run on a single PC, making it easy to create systems

with up to 80 thermocouples. The TC-08 is supplied with PicoLog software free of charge. Full and demo versions of the PicoLog software can be downloaded from Pico Technology's website.

Alan Tong, Pico Technology's Technical Director, comments: "The serial version of the TC-08 was launched in 1995 and — with temperature being the most common parameter users wish to measure — quickly became one of our most popular data logging products. However, with serial ports no longer provided on modern PCs, customers had to buy serial-to-USB adapters — but no more. The new TC-08 connects to a PC via USB, dispensing with the need for an adapter and delivering enhanced performance."

With the free PicoLog Recorder software, the user can configure multiple (USB) TC-08s, set the sampling interval from 0.1 seconds to several hours, and set the maximum number of readings. The user can also tell the PicoLog Recorder what to do once the thermocouple readings have been taken. Options include Stop; Repeat Immediately (start again); Scroll (oldest recordings disappear); or Repeat After Delay (where the delay is set by the user). The user can also perform mathematical operations on the thermocouple outputs. For example, the user can output one temperature relative to another.

Using PicoLog Recorder, TC-08 data can be viewed in a spreadsheet and/or in a graph as it is being recorded. TC-08 data collected from previous recordings can also be viewed in PicoLog Player. The TC-08 (USB version) is available immediately and retails for approximately \$470.00, plus tax.

For more information, contact:

## PICO TECHNOLOGY LTD.

Mill House

Cambridge St.

St. Neots PE19 1QB

United Kingdom

**+44 1480 396395** Fax: **+44 1480 396296**

Email: [enquiry@picotech.com](mailto:enquiry@picotech.com)

Web: [www.picotech.com](http://www.picotech.com)

Circle #114 on the Reader Service Card.

## Working on Something Cool?

If you are launching a new product, let us know! Send us a short write-up (including product specs, applications, and price), a high res photo of the product, and customer contact information.

Send your announcement to [newproducts@nutsvolts.com](mailto:newproducts@nutsvolts.com) today to be considered for future New Product News installments!



## VIDEO CRIME STOPPERS AND JAW DROPPERS!!!

**110%  
LOW PRICE  
GUARANTEE**  
Some restrictions  
apply



### OUTDOOR FLOOD LIGHT CAMERA

Powered by  
and transmits  
video through  
AC lines!

Receiver  
Included

**\$99.95**

### WEATHERPROOF INFRARED CAMERA



**\$49.95**

Tough metal turret-style  
housing. Easy installation  
& precise camera aiming

### SEND VIDEO & AUDIO UP TO 300 FEET!



**\$49.95**

This 2.4GHz audio/video link  
works with any video camera.  
Operation is easy and license free.

### SEND AUDIO/VIDEO OVER 1 MILE



**\$199.95**

Operates on 900 MHz ARS  
band. Strong 500 milliwatt out-  
put makes it great for RC aerial or  
robotic applications.

### WORLD'S SMALLEST CAMERA

Featured in the  
Guinness Book of  
World Records!



Tiny 0.375" square  
by 0.625" size!

**\$89.95**

### MICRO AUDIO SYSTEM



**\$9.95**

Super high gain microphone  
with built in preamplifier!

### 2.4GHZ WIRELESS VIDEO KIT

Transmits up to 150'  
and produces a sharp  
300 lines of resolution



### SUPER EASY TO USE!



**\$89.95**


### 18 INCH FIBER OPTIC SCOPE

Needs only 1/2"  
opening. Built-in  
high intensity  
halogen light.  
Lengths available up  
to 72"



**\$249.95**

### B/W MICROVIDEO CAMERA

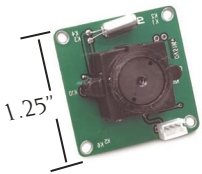

**320 Lines  
Of Resolution**  
Only \$11.95—  
World's Best Value  
Video Camera!

**\$11.95**

Put it on your R/C plane with our  
video xmitter for a bird's eye view!

### 2 CH VIDEO SERVER

Easily connects to LAN's  
or even directly to PC's



View video live from anywhere in  
the world using any browser.  
Features include auto email of  
video during alarm conditions.

**\$249.95**

### 1280 HOUR TIME LAPSE VCR



**Record indefinitely with  
endless loop recording!**

This time lapse VCR lets you  
record 1280 hours-- that's  
nearly 2 months!

**\$159.95**

### QUAD/DVR VIDEO CARD



View and  
record video up  
to 4 cameras  
on your PC!

Records up to 1000 hours of  
video on an 80 GB hard drive!

**\$89.95**

### 1" MINI MONITOR



New! Handheld  
pocket size  
mini field monitor!



Runs up to 24 hours on  
3 AAA batteries!

**\$119.95**

### NEW! MICRO DIGITAL VIDEO RECORDER

Records up to 40 Hours!



World's smallest hard-  
drive based digital  
video recorder!



**\$499.95**

### WIRED COVERT SMOKE DETECTOR CAMERAS

Covers almost  
any room with  
30° oblique  
camera angle

Covert  
camera  
location



Ask about our super stealth  
versions for phenomenal low  
light rating of 0.0003 lux.

700 foot wireless  
version available for  
\$189.95

**\$59.95**

### 4 CAMERA B/W DOME VIDEO SECURITY SYSTEM



4-Dome cameras  
1-Realtime b/w quad processor, &  
power supplies  
1-12" B/W monitor  
4-12 volt power supplies,  
2-3' video cable  
4-100' integrated  
video/power cables  
Comes complete  
for only..... **\$279.95**

### UNDERWATER VIDEO SYSTEM WITH MONITOR AND 4 HOUR BATTERY



5" CRT  
Display

Complete, plug and  
play with 65 foot  
cable!

Underwater  
Camera w/  
Infrared Lighting

**\$99.95**

### WEATHERPROOF OUTDOOR CAMERA WITH ZOOM LENS

Installation is a  
snap with easy  
external mag-  
netic zoom  
adjustment.



Comes with versatile 2.8-10 MM  
varifocal zoom/auto iris lens.

Also available with 5-50 MM lens



**\$159.95**

## SUPERCIRCUITS

See Hundreds Of Amazing  
Video Products Online At  
[www.supercircuits.com](http://www.supercircuits.com)  
or Call Us Today To Order  
or Request A Free Catalog

**1-800-335-9777**

One Supercircuits Plaza, Liberty Hill, TX 78642  
Phone 1-512-778-6950 Fax 1-866-267-9777  
Prices, specifications and availability are  
subject to change without notice. See catalog  
or website for details of 110% low price guar-  
antee. Published terms & conditions apply.  
Copyright 2004 Supercircuits, Inc.



Please call us at 1-800-335-9777 to be rushed your free Microvideo and Security Catalog!



# A Simple Shaded Pole AC Motor

## How Could Tesla Be Wrong?

### This Month's Projects

Pole AC Motor . . . . 36  
Ever-Shrinking  $\mu\text{C}$  . . 42  
Calculating Current . . 50



### The Fuzzball Rating System

To find out the level of difficulty for each of these projects, turn to Fuzzball for the answers.

The scale is from 1-4, with four Fuzzballs being the more difficult or advanced projects. Just look for the Fuzzballs in the opening header.

You'll also find information included in each article on any special tools or skills you'll need to complete the project.

Let the soldering begin!

As early as 1821, Michael Faraday demonstrated that continuous rotary motion could be produced by passing a DC (Direct Current) current through a wire in the presence of a magnetic field.

Many pioneers followed in his footsteps, but failed to develop a commercially successful DC motor. Development was hampered because batteries were the only source of electrical power. Batteries, while large and heavy, were constructed from expensive materials that could provide little energy. As a result, electric power was unable to compete with the current technology — steam power. Steam could be obtained cheaply from just water and coal-fired boilers. Thus, funding for the development of electric motors was nonexistent and they were relegated to being laboratory curiosities.

Further development of electric motors was delayed until the 1870s, when a number of experimenters developed the principle of the self-excited DC generator. At this time, they discovered the reciprocity theorem, in which a motor could act as a generator or vice versa. This discovery was widely publicized in 1873 by the French engineer, Hippolyte Fontaine, who recorded the results of an

accident where a worker mistakenly wired two generators together.


DC generators rapidly replaced the energy deficient batteries with a source of endless electric power. Steam power was now harnessed to drive these generators. The transmission of electric power permitted these plants to be located farther away so that noise and pollution were hidden.

Countless small DC motors were rapidly introduced to power fans, sewing machines, and other light tasks for the upper class. Cities had grown into heavily populated metropolises and a cleaner and cheaper means of transportation was desired to replace the horse-drawn buggy. In 1897, thousands of visitors at Germany's Berlin Exhibition were transported by the first practical electrically-powered motor vehicle, developed by Werner von Siemens.

Many companies began with the production of electrically-powered cars from about 1897 to 1914. In 1898, 23-year-old Ferdinand Porsche landed his first job in the automotive field with Jacob Lohner. He devised a system to eliminate the conventional front wheel hubs, transmission, gears, and chains by installing electric motors integral to each front wheel hub. In 1900, this car made its debut at the World's Fair in Paris, France and went on to set several Austrian land speed records. Porsche realized that the weight and the storage capacity of batteries were serious limitations, but he also recognized the advantage of electric motors to be quiet, smooth, and very reliable. After the exposition, he designed a car that employed an internal combustion engine to drive a generator that, in turn, supplied the electrical power to the twin hub motors. This is a century before Honda, Toyota, and others would introduce their hybrids.

In spite of the great accomplishments, further applications of DC motors were limited since DC power could only be transmitted a

**Figure 1.** A capacitor produces a phase shifted field.

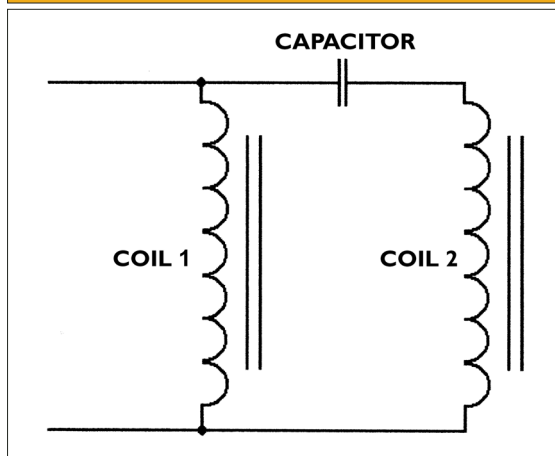



# A Simple Shaded Pole AC Motor

few tens of miles from the generators due to losses in the transmission lines. The advantage that AC (Alternating Current) power could be transmitted over long distances had already been recognized, but its advantage could not be utilized until the AC motor was developed.

DC power design had been rather simple and developed by trial and error. AC power development, however, required a fundamental understanding of AC theory. In 1888, Galileo Ferraris — an Italian professor — published his observations that two out-of-phase light waves would produce a rotating beam of light. From this simple idea, he was led to describe a rotating magnetic field produced by two out-of-phase magnetic fields. In this paper, he described how a single AC current could be split into two out-of-phase components that would produce a traveling magnetic field, but — unfortunately — he erroneously concluded that such a motor was impractical and was only another laboratory curiosity.

A year earlier, Nikola Tesla (1856-1943) applied for a patent on an AC induction motor that employed a traveling magnetic field that rotated. Tesla was born in Yugoslavia and moved to the US in 1884 to work with Thomas Edison. Unfortunately, the two had a personality conflict and Tesla left Edison a year later to begin an arc lamp business. The conflict between these two inventors continued with Edison pushing for DC systems and Tesla supporting AC systems. During the period of 1888 to 1896, Tesla obtained extensive patent coverage over most of the features of AC motors, including multiphase systems.

By 1893, both Westinghouse and General Electric had introduced AC induction motors. At this time, Tesla demonstrated his system of lighting at the Chicago World Columbian Exposition in the futuristic "White City." The commercial success of AC power was assured in 1896 by the construction of the Niagara Falls hydroelectric plant that provided the staggering power of 11 megawatts. Later, several more generators were added to raise this level to 37 megawatts.

Eventually, this power would enable the Pittsburgh Reduction Company (later to become the Aluminum Company of America) to produce the aluminum that would nurture the aircraft industry. Thus, by the 1900s, all the major features of both DC and AC electric power systems were firmly in place.

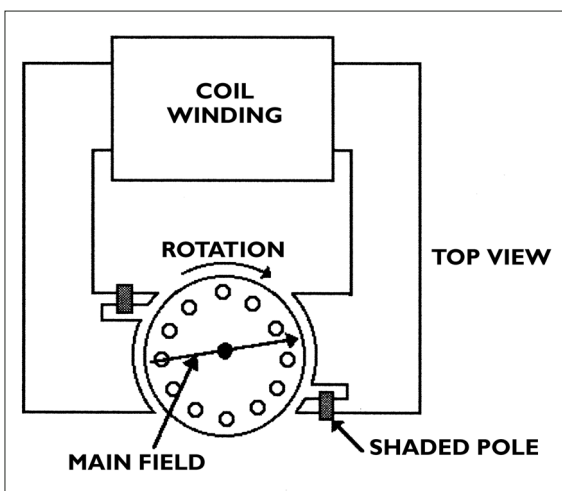


Figure 2. A typical shaded pole motor.


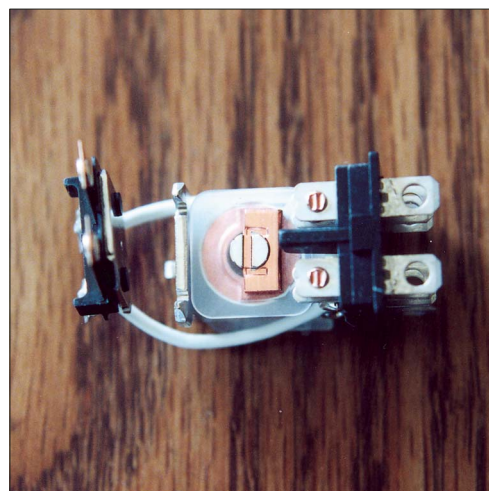


Figure 3. A shaded pole AC relay.

In some AC motor designs, two out-of-phase magnetic fields can be generated by the reactive impedance of a capacitor, as illustrated in Figure 1. Such motors are called capacitive motors. One design employs the extra phased winding only for starting torque and these motors are called capacitive start motors. Still another version — the shaded pole motor — produces two out-of-phase magnetic

## WHAT CAN YOU DO WITH THE ezVID?

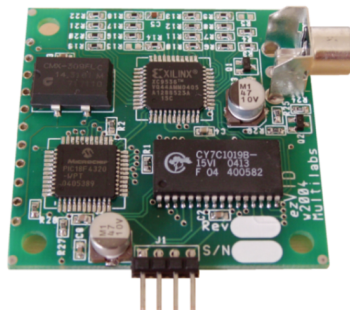

ezVID - THE SIMPLE TO USE SERIAL VIDEO CARD

- ▶ 9600 BAUD TTL LEVEL SERIAL INTERFACE
- ▶ SCREEN RESOLUTION OF 188 BY 254
- ▶ TRUE BITMAP WITH NO CHARACTER CELLS SO CUSTOM CHARACTERS CAN BE COMBINED TO FORM GRAPHICS
- ▶ 14 DIFFERENT COLORS AVAILABLE
- ▶ 63 BUILT-IN STANDARD CHARACTERS
- ▶ 256 USER-DEFINABLE CHARACTERS
- ▶ STANDARD COMPOSITE NTSC NON-INTERLACED VIDEO OUTPUT


\$59.95

LEARN MORE AT  
WWW.MULTILABS.NET



ADDRESS:  
1105 BELLECOUR WAY  
LAKE FOREST, CA 92630  
EMAIL:  
SUPPORT@MULTILABS.NET  
WEB:  
WWW.MULTILABS.NET


## GAMING

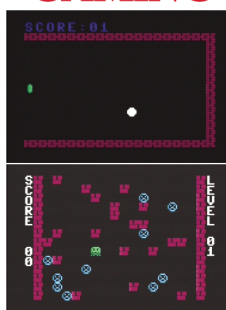


## GRAPHICS



## TEXT

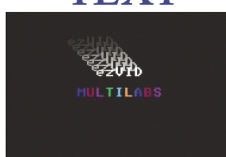

Circle #68 on the Reader Service Card.

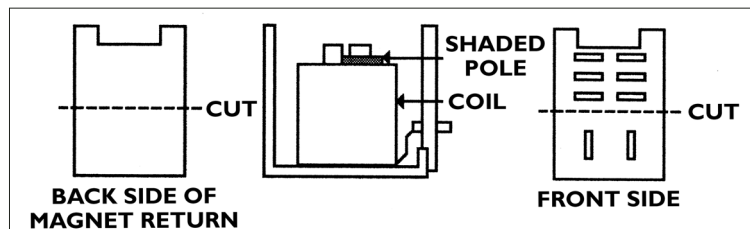

**Figure 4.** Preparation of the AC coil.

fields by means of the shading coil. An example of this type is illustrated in Figure 2, where a shorted coil (the shaded pole) encircles part of the magnetic pole. Since the current induced in the shorted turn is a function of the rate of change of the main pole flux, it is out-of-phase and lags the main field.

John Fleming introduced the design of the shaded pole motor around 1890. Fleming would go on to help Guglielmo Marconi design his equipment for the first transatlantic wireless message in 1901 and he would later patent the first vacuum tube (a “thermionic valve”) in 1904. About this same time, Elihu Thomson patented the shaded pole design in the US and, in 1892, his company merged with the Edison General Electric Company to become the General Electric Company.

Interestingly, the design of the shaded pole motor to produce a rotating magnetic field is also employed in the design of AC relays and contactors. You can identify AC relay coils from DC designs by looking at the shaded pole, as illustrated in Figure 3. The shaded pole design for AC relays is used to delay one component of the magnetic field to prevent the relay from chattering. Without the shaded pole, an AC relay contact would chatter every time the AC current goes through zero and the magnetic field would be unable to hold the contacts closed against the spring. The delayed field continues to hold the relay contacts closed while the main field goes through zero and visa versa.

The design of our shaded pole motor starts with two AC relay coils. For ease of construction, the relay coils can be obtained from RadioShack (part number 275-217), but other coils will work. These relays are Omron LY-2-AC 110/120 coils rated at 1.1 VA at 110 to 120 VAC. Typically, the coils draw about 10 mA when the contacts are closed. Some relays operate at 2-3 VA, especially 3PDT and larger relays that will produce larger magnetic fields for larger gaps or that can operate a motor with greater

bearing friction. The plastic case, the hinged metal return that supports the contacts, and the return force spring can be discarded.

Carefully place the coil in a vise and cut the rear of the magnet return down low with a fine-toothed hacksaw blade, as illustrated in Figure 4. As you cut through the steel return, it is advisable to place a 1/16” thick plastic sheet between the steel and the coil to prevent the hacksaw blade from breaking through and damaging the coil. In our application, the magnetic path is essentially through an air gap that reduces the magnetic field and the self-inductance of the coils. This results in larger coil current. The open circuited coil will typically run about 25 ma and will, thus, run thermally warmer.


The plastic terminal block has to be cut down, similar to the metal magnet return, as illustrated in Figure 4. The solder contact just above the relay coil terminals can be removed by unsoldering the attached wires and pulling the pins outward. It is convenient to cut at this same level. Again, it is helpful to put a piece of plastic between the coil and contact block to prevent the saw blade from damaging the coil. Also, use extra caution on this side of the coil because the fine coil leads are also located here.

All the metal parts — including the aluminum sheet, brass sheet, tubing, and rods — were obtained from a hardware store. The magnetic return for the two coils was fabricated from a 3” x 3” x 3/4” steel corner bracket. The

bracket was bent in the vise, as illustrated in Figure 5. The spacing is not too critical, but the poles of the coils should be spaced on the order of 3/16”. The coils were epoxied to the steel return using a five minute epoxy, such as Loctite. It is always a good practice to roughen the surfaces to be epoxied with either a file or sandpaper to provide a rough, clean surface for the adhesive. This completes the shaded pole coil assembly.

The rotor for our motor is fabricated from 1/16” thick aluminum. A compass or divider can be used to inscribe the circle with a 2.5” diameter. A sharp pair of tin snips can be used to cut along the mark to produce the rotor. The main thing is not to distort the aluminum. It must be relatively flat to run between the gap of the pole pieces. Various size rotors have been employed in different designs.

**Figure 5.** A steel bracket for magnet return, pivot, and bearing.

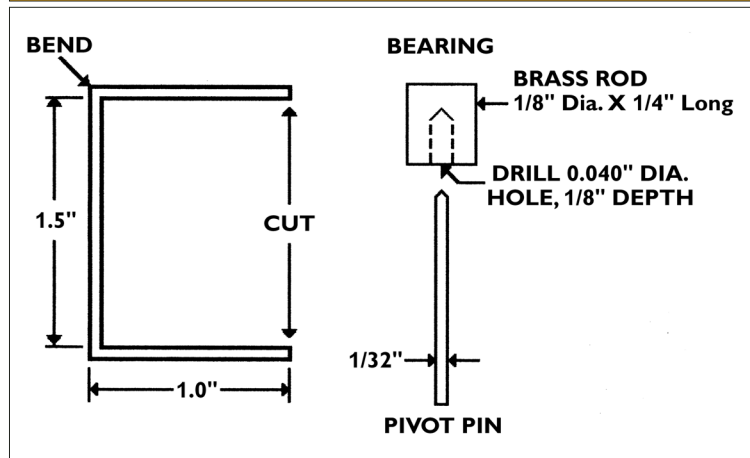



## A Simple Shaded Pole AC Motor

Larger diameter rotors tend to wobble more and may brush against the pole and stop turning. Rotors as thin as 0.003" have been made and also work. Material of this thickness can be cut with an ordinary pair of scissors. Thinner material will not work because the resistance of the material becomes too high and the material also becomes mechanically unstable. A 1/8" diameter hole can be punched in the rotor at the center of the circle. Either use a hand punch or drill the hole by sandwiching the aluminum between two heavy sheets of plastic to prevent the drill from ripping through.

The central rotor bearing was made from a 1/4" long piece of 1/8" brass rod, as seen in Figure 5. The rod was drilled with a 0.040" diameter drill bit to a depth of 1/8". Most general-purpose drill bits have a 118° point. The central bearing was placed in the central hole of the aluminum rotor and a piece of Scotch tape was placed on the underside to hold the bearing in position and to seal the 0.040" hole. Epoxy was applied with a toothpick to glue the bearing and rotor together. Since the mass of the aluminum disc is about 1/8" below the support pivot, it will be unconditionally stable and will not fall off the pivot.

As an alternative, some models of this motor have been built using the plastic top of a three in one multi-purpose oil can (3 fl oz size) in place of the brass bearing. The closed end of the red plastic spout was cut off with a razor blade about 3/16" from the top and used as the bearing. The brass bearing is, of course, more rugged and provides a better bearing if the hole is drilled true. A small lathe is useful here, if you have one.

The pivot point was fabricated from a 1/32" brass rod, as shown in Figure 5. The point of the rod was ground by turning the rod against fine emery paper. The rod was held at about a 25° angle above the paper to produce the point. This produces a point of about 50°, as compared to the drill bit point of 118°, to ensure a point of contact and lower friction. In another version of the motor design, a steel needle was used as the pivot point.

The completed motor can be seen in Figure 6. The mounting base was made from a piece of 1/16" thick brass that is 4" square. A metal base is useful to help dissipate the additional coil heat. At the center of the base, a 4-40 brass nut was soldered. To the center of the nut, a 3/32" O.D. brass tube was soldered and the 1/32" brass pivot rod was soldered into this tube. The tube helped to stiffen the smaller pivot rod and also allowed less heat to be applied to the pivot rod for adjustment of the height of the pivot to locate the rotor between the pole pieces.

Other models have been built with a wooden base that employed the steel needle pivot mentioned earlier. In such a design, the needle can be pushed further into the wood to adjust the pivot height to center the rotor between the pole pieces.

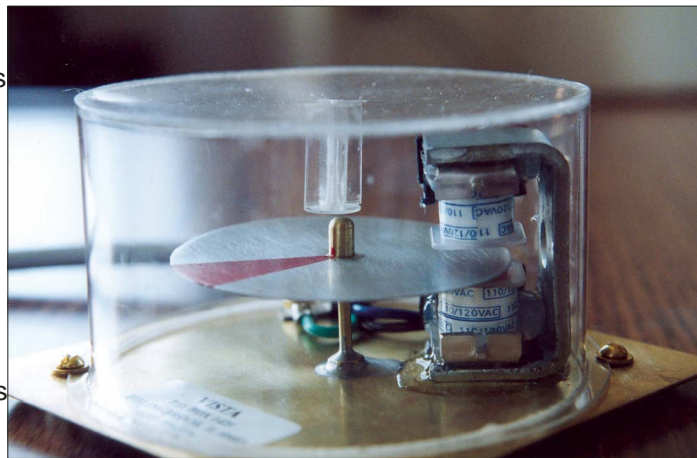


Figure 6. 

Once the final position has been determined, the pin position can be secured with a drop of epoxy between the base and pin.

After the rotor has been assembled and a pivot rod is available, you can test the bearing and rotor run out. Softly blow on the underside of the disc to see that it spins easily. Also notice if the disc tends to always stop with one side low. It is helpful to mark the rotor with a pen to provide a



# SERIAL ANALYZER

Transparent troubleshooting and emulation of serial interfaces...

- ▶ Serial link passes through base unit without retransmission distortion or delay.
- ▶ Captures full duplex data with precise time tagging and line states.
- ▶ Measures transmit and receive line voltages.
- ▶ Allows a PC to emulate one serial device while capturing full transaction.
- ▶ Data can be easily exported to third application.



All hardware, cables/adapters, Windows® compatible software and documentation are included.

**NEW** Serial Analyzer can now capture data to PC hard disk for extended periods!

**Toll Free 1-866-442-7767**  
**www.smartronix.com**

**Interested in building more products like these?**  
We are always looking for talented engineers, please visit the employment section on our website. (EOE/M/F/V/D)

reference mark to gauge if the rotor always droops to the same side. If one side is heavier than the other, trim a little off the edge of the rotor that always dips until a reasonable balance is achieved.

The coil assembly is positioned on the base plate so that the rotor passes fully between the pole pieces. The rotor height must be adjusted so that the rotor will spin freely through the pole faces without touching them. When you are sure of the positioning, place some epoxy on the base and locate the coil assembly permanently. Again, be sure the surfaces to be glued are roughened and clean.

Once the coil assembly is secured to the base, the coils may be wired. A thin, 18 gauge appliance cord can be used to supply power. Because the top coil is driven out of phase with the lower coil, the line is connected to pin 7 of the lower coil and pin 8 of the upper coil. Similarly, the neutral is connected to pin 8 of the lower coil and pin 7 of the upper coil.

Because the top coil is turned over from the position of the lower coil, pin 7 of the lower coil is on the same side of pin 8 of the upper coil. The electrical connections should be insulated with silicon rubber sealant placed over all exposed connections. While the motor draws little power, it is connected to 120 VAC and deserves respect.

For safety „ if a metal base is employed „ the base should also be electrically grounded through a three-pronged plug.

When the coils are energized, the rotor will spin in the direction of the shaded pole (the shaded pole lags the main field). The rotor speed is about 20 RPM. Very little torque is developed by this design, since the electrons can slip within the aluminum rotor. The 1/16" aluminum rotor is heavy enough that a light wind should not bother the operation. Thinner, lighter rotors will require shielding from air currents. An acrylic hemisphere for displaying models or the bottom third of a plastic 2 L soft drink bottle can provide a suitable cover.

The cover for this model was fabricated from a sheet of 0.020" Lexan (polycarbonate) that I had available. The 3" diameter top circle and lower circular ring were scribed with a compass and cut out with a pair of scissors. These circular pieces are used to form the 2" tall strip into a circular tube. The seams were glued with a solvent cement supplied by McMaster Carr Supply Company (www.mcmaster.com), part number 7528A13. The top has a support hanging down that is terminated about 1/16" above the top of the brass bearing to prevent the rotor from coming off the pivot pin if the motor is jostled around at your next science fair. **NV**

## SAELIG BRINGS YOU EASY-TO-USE SOLUTIONS!

|  |  |  |  |   |   |
|--|--|--|--|---|---|
| <b>USB in one IC!</b><br><br><b>FT232RL</b> Single chip USB-232 solution with Windows/Mac/Linux drivers. No programming/USB knowledge required! Easiest answer to update RS232 devices! <b>Only \$2.55 (10k)</b>                            | <b>USB&lt;&gt;RS485</b><br><br><b>USB-COM!</b> (non-isolated) or <b>USB-COM!SI</b> (isolated) offer self-powered USB to RS485 conversion with baud rates 184kbps - 3Mbps. PC thinks it's talking to a COMport! <b>only \$48/\$85!</b> | <b>USB Logic Analyzer</b><br><br><b>ANT8</b> Matchbox-sized USB-powered logic analyzer. Sample 8 channels at up to 500 MS/s. View traces on PC. Print or save for later review! (16-ch. ver. tool) <b>only \$222!</b>             | <b>easyRADIO</b><br><br><b>easyRADIO™ ER900TRS</b> Transceiver Modules make wireless data transmission simple for USA and Europe! Add wireless capability to your project today! <b>from \$155!</b>                                       | <b>USB Bus Analyzers</b><br><br><b>Tracker 110/Explorer 200</b> high-performance, economical USB 1.1/2.0 protocol analyzers. Perfect for troubleshooting USB, optimizing data flow and USB training! <b>Only \$899/\$2700!</b>                                     | <b>USB-Serial Adapter</b><br><br><b>Serial port for laptops</b> without one! <b>US232B</b> instantly updates older RS232 products to USB! PC thinks it's using COMport but uses the USB connection. <b>Only \$39 (1) or \$29 (100)</b>                               |
| <b>CANbus Cards</b><br><br><b>CANbus</b> - Starter Packs and cards for almost any board format & OS. CAN/Ethernet bridges, industrial automation solutions from Janz AG as used by top companies all over the world.                        | <b>Industrial PCs</b><br><br><b>ATX Ruggedized Industrial PCs</b> for guaranteed long production life, economy, reliability. AMD Athlon XP1700, shock-mounted 40GB hard drive. 100% Burn-in. CE EMC. <b>only \$899</b>                | <b>Mini Web Server</b><br><br><b>PicoServ™</b> Miniature Web Server allows remote I/O and servicing. Collect analog & digital data over a web connection. Remote sensing/control, SCADA, building control, etc. <b>from \$189</b> | <b>PC Scope Adapter</b><br><br><b>STINGRAY-</b> 1 MS/s sampling 12-bit 2-ch USB scope adapter for PC. Looks like a "Digital Scope" on your PC screen! Great for laptops, and servicing. <b>DS1M12 only \$189</b>                          | <b>RS232&lt;&gt;422/485</b><br><br><b>K2 9p-9p self-pwr'd RS-422/485</b><br><b>K3 9p-9p isolated RS-422/485</b><br><b>K3-232 9p-9p isolated RS232</b><br><b>K232-ISOL 25p -25p RS232</b><br><b>KD485-STD DINrail - isolated</b><br><b>KD485-PROG programmable!</b> | <b>I2C for PCs</b><br><br><b>PCI93LV:</b> industry-standard I2C card for PCs. <b>WINI2C/PCI</b> software gives windows-interface to develop and debug I2C bus systems. <b>UCA93LV</b> is new USB version. NOW! - transparently monitor at 400kHz! <b>only \$499!</b> |
| <b>Power Supply</b><br><br><ul style="list-style-type: none"> <li>1.5 to 30V d.c. output</li> <li>0 to 1A output current</li> <li>100 to 240 V a.c. input</li> <li>Over-volt/current &amp; short circuit protection</li> </ul> <b>\$79!</b> | <b>Dataloggers</b><br><br><b>TDS2020F</b> makes a custom CF card A/D datalogger or controller - quickly! High-level software completes projects in hours. Store <b>GPS/CANbus/A or D</b> data to card. <b>only \$199 (50 qty)</b>     | <b>PC Scope Adapters</b><br><br><b>ADC-212/100</b> turns your PC into a great high-speed scope. Sampling to 100MS/s at 12-bit res'n. FREE s/w turns PC into powerful 2-ch scope, DVM & spectrum analyzer. <b>\$95 - \$1145</b>    | <b>BASIC modules</b><br><br><b>Tigers</b> - tiny multitasking BASIC modules for quick projects. >100,000 instr's/s! <b>ICOM200</b> ready-made controller with LCD and keypad. <b>Touch240</b> controller - with touchpad and LCD display. | <b>Crystals / Oscillators</b><br><br><b>Euroquartz</b> - Europe's largest mfr of quartz crystals, oscillators, filters and frequency products. Custom filters, high rel. rad tol. oscillators. Novel <b>EQ-HM</b> spread-spectrum oscs reduce EMI problems         | <b>SM PCB Adapters</b><br><br><b>OM-Adapt</b> SM miniboards have two footprints on either side. Now use your ultra fine pitch SMD components with more useful 0.1" inline spaced holes. One-to-one pinouts. <b>\$6.99</b>  |

**Customer Comment of the month:** "Impressive response! Nice and clear...seems like your company has a 'can do' attitude. In today's world, good customer service is becoming scarce." (P.A.)

### Saelig Co. Inc.

ph 585-385-1750 fx 585-385-1768

www.saelig.com/ad/nv11.htm • info@saelig.com

Saelig Co. brings to USA unique, easy-to-use control and instrumentation products from overseas. Customers include: Intel, Philips, NEC, Kodak, Nokia, US Military, Microsoft, Dell, Xerox, Universities, T.I., Harris, Sony, J&J, Thomson, Sandisk, General Dynamics, H-P/Compaq, etc.



# ALL ELECTRONICS

C O R P O R A T I O N

**QUALITY Parts**  
**FAST Shipping**  
**DISCOUNT Pricing**

**CALL, WRITE, FAX or E-MAIL**  
**for a FREE 96 page catalog.**  
Outside the U.S.A. send \$3.00 postage.

## SPST NEON LIGHTED ROCKER SWITCH

Conveniently snap-mounts in 0.82" diameter hole. Round red rocker. Matte black bezel is 0.91" diameter. Switch rated 13 Amps @ 125 Vac. Solder / 0.187" qc terminals.

**CAT# LRS-25**

10 for \$1.15 each

**\$1.35**  
each



## 3-INPUT AUDIO/ VIDEO SWITCHER



Recoton / Jensen #JV500. Connect up to three audio/ video components, VCR, DVD, video game, etc, to your television RCA inputs. Rotary selector switch on front panel of switch. Includes a 6 ft. 3-conductor, video / stereo audio cable with RCA plugs. New units in original packaging, but the packaging may be old or scuffed.

**CAT# AVS-500**

**\$7.50**  
each

## "BED-O-NAILS" TEST CLIPS

J.S. Popper "Bed-of-nails" test clips with insulating boots on approximately 46" long leads. Bed-of-nails clips have multiple spikes in the middle of the clip enabling measurement through insulated wire. The jaws at the front of the clip grab and hold securely to plugs or terminals. The leads are stranded copper litz wire with red and black woven cloth insulation. Leads were cut from new equipment and may require a crimp terminal to facilitate attachment.

**CAT# ALG-22**

**\$5.00**  
each

10 for \$4.50 each  
50 for \$4.00 each



## 12 VDC 92 MM COOLING FAN

Papst Multifan #3312. 3.63" square x 1.27" ball bearing cooling fan. 12 Vdc, (6-15 Vdc) 290 mA. Fiberglass reinforced plastic PBTP housing, PA impeller. 47.1 CFM. 3000 RPM. 12" 22 AWG leads. UL, CSA, CE, VDE.

**CAT# CF-204**

10 for \$3.25 each

**\$3.50**  
each



## 0.56" DUAL 7-SEGMENT DISPLAY, RED C.C.

0.56" character height. 24 pin DIP socket. Red C.C. Dual Digits.

**CAT# TDC-565**

**\$1.00**  
each

10 for 85¢ each  
100 for 75¢ each




## SOLAR CELLS w/ CHARGING CIRCUIT - 3 LED'S

Here's a great start for a solar cell project. From not-yet-assembled solar-powered garden lights, these assemblies include two glass photovoltaic cells mounted on a plastic base. Output is approximately 2.6 Vdc @ 25 mA in bright sunlight. Under the photocells is a bracket for a two cell rechargeable AA pack & a small circuit board with three red LEDs. There is a photoresistor on top of the panel between the solar cells to sense light and dark conditions. In daylight the cells charge the battery. When it gets dark, the LEDs light. These are working units but the batteries packs are old and may not take a charge. Our two AA cell nickel-metal-hydrate pack, CAT# NMH-2AA (\$2.00 ea.) is a good replacement. Solar cell surface area: 3.78" X 1.98".

**\$4.50**  
each

10 for \$4.25 each  
100 for \$4.00 each

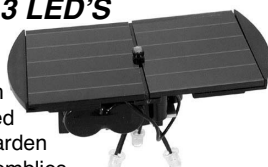

## 4-28 VDC PIEZO BEEPER WITH VOLUME CONTROL

Shogyo #3650VC. Solid-state audio indicator emits a medium-loud, high-pitched tone. Screwdriver adjustable trimmer on back of device controls volume. Operates on 4-28 Vdc @ 6 mA. Black plastic face is 1.45" diameter x 0.16" thick. 1.25" diameter threaded mounting bushing with large plastic nut mounts in panels up to 0.5" thick. 0.187" qc or solder terminals.

**CAT# SBZ-365**

**\$3.95**  
each

10 for \$3.50 each  
100 for \$2.75 each



## FAN-COOLED 6-12 VDC MOTOR

Smooth, powerful DC motor with internal cooling fan. Operates on 3-12 Vdc. 11,500 RPM @ 6Vdc, 1.35 Amps. 1.45" dia. x 2.25" long. 0.125" diameter flatted shaft is 0.7" long. Two threaded mounting holes on face of motor on 1" mounting centers. Solder lug terminals.

**CAT# DCM-231**

**\$3.75**  
each

10 for \$3.50 each  
75 for \$3.00 each




## 24 CHARACTER X 2 LINE LCD w/ EL BACKLIGHT, USED

24 character x 2 line LCD with electroluminescent backlight. 0.64" x 3.7" viewing area. Module size, 1.53" x 4.7". Includes a detachable 7" ribbon cable with 14 contact socket connector and 5" leads on the el terminals. Removed, in good condition, from used equipment.

**CAT# LCD-107**

10 for \$3.50 each

**\$4.00**  
each

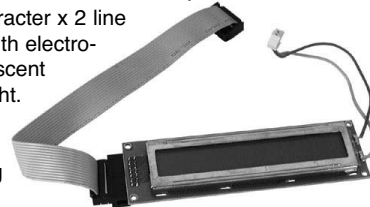

**Shop ON-LINE [www.allelectronics.com](http://www.allelectronics.com)**  
**ORDER TOLL FREE 1-800-826-5432**


MAIL ORDERS TO:  
ALL ELECTRONICS CORP.  
P.O. BOX 567 • VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524  
E-MAIL [allcorp@allcorp.com](mailto:allcorp@allcorp.com)

NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D. • Shipping and Handling \$6.00 for the 48 Continental United States • ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

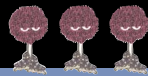**MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.**





# The Ever-Shrinking $\mu$ C — Part 2

## Six Pins and One MIP — If You Can See It!

If, after reading Part 1 last month, you've been wondering why there are two PIC10F206s on the Little Bits Development Board, here's part of that answer: The inverter pair we just implemented can be tested by simply moving jumpers carrying the desired logic levels between the inverter inputs and watching the inverter outputs on the LEDs. Instead of swapping around jumpers, the second PIC10F206 can be used as stimulus for the first PIC10F206. I wrote a small piece of code called

TOGGLER that does nothing but count from 0 to 7 continually. Using jumpers, I feed the output of the PIC10F206 running TOGGLER to the input of the inverter pins of the PIC10F206 running the inverter code. As the count progresses, all of the possible inverter input combinations are provided to the inputs of the inverter pair we realized with the other PIC10F206. The C source for TOGGLER is shown in Listing 3.

I think you have the idea now. So, I've included some C code for a two-input AND gate in Listing 3, as well. There's always more than one way to skin a cat when coding. I've also included an optimized version of the two-input AND gate code in Listing 3 for your approval. From the example code I've presented, you should now be able to create many other logic gates, including a three-input AND gate, an EXCLUSIVE OR/NOR gate, and an OR/NOR gate.

For instance, to fabricate a NAND gate, all you have to do is invert the output levels within the case statements of the AND gate code. An OR gate can be fabricated from the AND gate code by simply changing the output within the case statements to 1 for any case statement that contains a 1 as its argument. To get the NOR function, invert the output of the OR gate within the OR gate case statements.

You can also emulate clocked logic with the PIC10F206 as well, provided that the clocked logic module you're emulating doesn't have more than three output pins. A clocked logic block that immediately comes to mind is the D flip-flop. When clocked, the Q output of a D flip-flop will follow the logic level of the D input with the NOT-Q output complementing the logic level of the D input.

Compile the D flip-flop code in Listing 3 and jumper the D and NOT-Q GPIO pins together. This will divide the incoming clock by 2 and produce the divided clock on the Q output pin. Feed the CLK

**Listing 3.** Remember, the PIC10F206 has a 1 mS instruction cycle time. So, although the logic will work as designed, the logic blocks we emulate with the PIC10F206 won't be as fast as the real thing.

```
//*****
/* HI-TECH C SOURCE CODE FOR TOGGLER MODULE
*****
void main()
{
    unsigned int x,y;

    TRIS = 0b00001000;    //GP3 input : all others output
    FOSC4 = 0;            //GP2 is an I/O pin
    CMCON = 0b11110111;   //comparator off:pullups off:wakeup off
    OPTION = 0b11001111;  //prescaler assigned to WDT
    while(1)
    {
        ++GPIO;           //increment output pin set GP0, GP1, GP2
        for(x=0;x<0xFFFF;++x) //delay by incrementing y 65534 times
            ++y;           //increment y
    } //while(1)           //loop forever
} //main TOGGLER

//*****
/* HI-TECH C SOURCE CODE FOR 2-INPUT AND GATE MODULE
*****
void main()
{
    TRIS = 0b11111011;    //GP2=output:all other GPIO=input
    FOSC4 = 0;            //GP2 is an I/O pin
    CMCON = 0b11110111;   //comparator off:pullups off:wakeup off
    OPTION = 0b11001111;  //prescaler assigned to WDT

    while(1)
    {
        switch (GPIO & 0b00000011)
        {
            case 0b00000000:    //GP0 = LOW:GP1=LOW
                GP2 = 0;        //GP2 = LOW
                break;
            case 0b00000001:    //GP0 = HIGH:GP1=LOW
                GP2 = 0;        //GP2 = LOW
                break;
        }
    }
}
```

(continued)



input of your PIC10F206 D FLIP-FLOP divide-by-2 emulator from one of the three PIC10F206 TOGGLER outputs. You'll see the division of whatever TOGGLER output clock you feed to the CLK input on the Q output of the D flip-flop emulated by the second PIC10F206. Figure 1 (see Part 1 in last month's issue) physically depicts all of the logic we've emulated or talked about so far. The view from way up here is tremendous, isn't it?

## Pulse Generation and Signal Conditioning With Little Bits

The 555 is a wonderful device. However, it has its shortcomings, as it programs in an analog fashion rather than a digital one. For instance, it takes a few choice components and some steering diodes to get a true %50 duty cycle pulse train directly from the output of a 555. With the small bit of C in Listing 4 and a single PIC10F206, I've created a 60 Hz pulse train with a 50% duty cycle.

The beginning of the code is very similar to our logic examples, except that the OPTION argument value has now assigned the prescaler to TMR0 (Timer 0) by clearing bit 3 of the OPTION register. Bits 0, 1, and 2 set the prescaler value to 1:64, which instructs TMR0 to increment once every 64 instruction cycles.

The meat of the 60 Hz code is centered on the TMR0 instructions. First, the TMR0 register is loaded with 0x80. After a couple of synchronization cycles, TMR0 begins to count upwards from 0x80. Visualizing this in binary, the first count will be 0b10000001. The second count will be 0b10000010 and so forth until the count reaches 0b11111111 and then rolls over to 0b00000000.

When the count rolls over to 0b00000000, the most significant bit is no longer set and the while(TMR0 & 0x80); becomes false, allowing the code to fall through to the next statement, which is GP2 = 0;. At this point, the code shifts the logic level of GP2 to low and spins in the TMR0 loop, just as it did when GP2 was high. You can alter the frequency of the TMR0-generated pulse train by toying with the three least significant bits of the OPTION register. You can also change the frequency by altering the value loaded to TMR0 and then checking for that value in the following while statement.

### (Listing 3, continued)

```
case 0b00000010:    //GP0 = LOW:GP1=HIGH
    GP2 = 0;        //GP2 = LOW
    break;
case 0b00000011:    //GP0 = HIGH:GP1=HIGH
    GP2 = 1;        //GP2 = HIGH
    break;
} //switch
} //while(1)
} //main

//*****
/*  HI-TECH C SOURCE CODE FOR 2-INPUT AND GATE MODULE OPTIMIZED
//*****
void main()
{
    TRIS = 0b11111011;    //GP2=output:all other GPIO=input
    FOSC4 = 0;            //GP2 is an I/O pin
    CMCON = 0b11110111;   //comparator off:pullups off:wakeup off
    OPTION = 0b11001111;  //prescaler assigned to WDT

    while(1)
    {
        switch (GPIO & 0b00000011)
        {
            case 0b00000011:    //GP2=HIGH only if both GP0 and GP1 are HIGH
                GP2 = 1;
                break;
            default:
                GP2 = 0;
                break;
        } //switch
    } //while(1)
} //main

//*****
/*  HI-TECH C SOURCE CODE FOR D FLIP-FLOP MODULE
//*****
void main()
{
    TRIS = 0b11111100;    //GP0=Q:GP1=NOT-Q:GP2=CLK:GP3=D
    FOSC4 = 0;
    CMCON = 0b11110111;
    OPTION = 0b11001111;

    //power-up clear operation
    while(GP2);           //wait for CLK to go LOW
    GP0 = 0;              //set Q
    GP1 = 1;              //clr Q

    while(1)
    {
        while(!GP2);      //wait for CLK to go HIGH
        switch (GPIO & 0b00001000)
        {
            case 0b00000000:    //D = 0
                GP0 = 0;        //clr Q
                GP1 = 1;        //set NOT-Q
                break;
            case 0b00001000:    //D = 1
                GP0 = 1;        //set Q
                GP1 = 0;        //clr NOT-Q
                break;
        } //switch
        while(GP2);         //wait for clock to go LOW
    } //while(1)
} //main
```

**Listing 4.** I'm sure there are some really weird analog things that you can do with a 555, but the PIC10F206 can hold its own against the 555 when it comes to handling and generating pulses.

```

//*****
/* HI-TECH C SOURCE CODE FOR PULSE GENERATOR MODULE
//*****
void main()
{
    TRIS = 0b00001000;    //GP3 input : all others output
    FOSC4 = 0;            //GP2 is an I/O pin
    CMCON = 0b11110111;   //comparator off:pullups off:wakeup off
    OPTION = 0b11000101;  //prescaler assigned to TMR0 @ 1:64

    while(1)              //loop forever
    {
        GP2 = 1;          //GP2 = HIGH
        TMR0 = 0x80;       //load TMR0
        while(TMR0 & 0x80); //count from 0b10000000 to 0b00000000

        GP2 = 0;          //GP2 = LOW
        TMR0 = 0x80;       //load TMR0
        while(TMR0 & 0x80); //count from 0x80 to 0x00
    } //while(1)
} //main

//*****
/* HI-TECH C SOURCE CODE FOR LED DIMMER MODULE
//*****
void main()
{
    unsigned char x,y,z;

    TRIS = 0b00001000;    //GP3 input : all others output
    FOSC4 = 0;            //GP2 is an I/O pin
    CMCON = 0b11110111;   //comparator off:pullups off:wakeup off
    OPTION = 0b11000010;  //prescaler assigned to TMR0 @ 1:8

    y = 0x04;             //initialize y
    z = 0x80;             //initialize z

    while(1)              //loop forever
    {
        do                //outer do loop
        {
            x=0xFF;

            do             //inner do loop
            {
                GP2 = 1;   //GP2 = HIGH
                TMR0 = y;   //load TMR0
                while(TMR0 & y); //count for y time

                GP2 = 0;   //GP2 = LOW
                TMR0 = z;   //load TMR0
                while(TMR0 & z); //count for z time
            } while(--x);  //do inner loop until x is decremented to 0

            y *= 2;        //multiply y x 2
            z /= 2;        //divide z by 2
        } while(y);       //do outer loop until y = 0

        y = 0x04;         //reinitialize y
        z = 0x80;         //reinitialize z
    } //while(1)
} //main

```

(continued)

It stands to reason that, if we can control the frequency of a pulse train generated by TMR0, we can also control the duty cycle of that pulse train. A 50% duty cycle means that every cycle has equal high and low logic levels with respect to time. If we apply that voltage to an LED, it will be on for half the time and off for half the time. If the frequency is high enough, the LED may appear to be dimmer than it would seem to be when full voltage is applied to it. If we switch between on and off fast enough, our eyes and mind will fool us into thinking that the LED is really never turning off. We can use this phenomenon to our advantage with the second code listing you see in Listing 4.

Let's work our way through the LED dimmer code inside out, beginning with the inner do loop. The GP2 = 1 code is exactly the same as our 60 Hz pulse train generator except that the 0x80 hard-coded value is replaced with a variable of y. The y variable is initialized to a value of 0x04 in the beginning of the code sequence. Recall that the TMR0 register increments every instruction cycle. So, the y count begins at 0b00000100 and ends at 0b00001000 when the TMR0 register rolls over to 0b00001000 from 0b00000111.

Looking at the GP2 = 0 code, it is exactly the same as our previous 60 Hz code for GP2 in a low logic state with the only exception being the variable z holding the 0x80 value, which was loaded right after the y value. What all of this means is that, initially, the high part of the cycle is much smaller than the low part of the cycle with respect to time, which, in turn, says that the LED will initially be off longer than it is on and will appear to be very dim. Each duty cycle period is alive as long as x is not equal to zero. The while(--x) decrements x with each pass through the inner do loop. The outer do loop initializes x, doubles y, and halves z at the completion of each pulse train cycle.

Since y is the variable that determines the high level time of each cycle and z is the variable that determines the low level time of each cycle and the values are approaching each other from the opposite directions, when y is equal to 0b10000000, z will be equal to 0b00000010. At this point, the LED will be at its brightest, since the high part of the cycle (y) will be much longer than the low part of the cycle (z). The



visual effect you will see is the LED going from dim to bright continually.

Delays and pulse trains can also be created with the PIC10F206 by utilizing code similar to that which is used in TOGGLER (Listing 3). Delays that last for seconds can easily be achieved by looping on a for construct like the one used in the TOGGLER code (available at [www.nutsvolts.com](http://www.nutsvolts.com)).

Take a look at the voltage booster circuit in Schematic 1 (see Part 1 in last month's issue). The 2N2222A alternately builds and collapses the field formed by the inductor. The steering diode routes the inductor's energy into the 100  $\mu$ F capacitor. The build-up and collapse of the magnetic field is caused by switching the transistor on and off rapidly with a pulse train provided by a PIC10F206. The code (part of Listing 4) is identical to the 60 Hz pulse train code, except that the TMR0 prescaler is set for 1:2 and the duty cycle of the pulse train is heavily biased to the logic low level. This may, at first, seem backward. However, the energy from the inductor is transferred to the capacitor when the transistor is turned off. When the transistor is on, the inductor is allowed to ramp up a charge.

By rapidly switching the inductor on and off, we are able to feed the inductor's energy through the diode and charge the output capacitor to a voltage that is higher than the input voltage at the inductor. The little circuit you see in Schematic 1, in combination with the voltage booster code in Listing 4, generates about +10 VDC across the output capacitor. You can obtain a much higher voltage by tweaking the pulse train's duty cycle.

In addition to generating pulses, the PIC10F206 can also be programmed to condition pulses. Let's use some TMR0 code we've already written and create a one-shot timer with a built-in switch debouncer. We'll only need a push-button switch and a resistor, as shown by the one-shot section of Schematic 1.

The C code is straightforward. GP3 is the input from the switch/resistor combination. When the switch is open, GP3 is held low by the 20K resistor. The while(!GP3) loops waiting for GP3 to go high. When the switch is closed, GP3 goes high and the TMR0 debounce code is executed; 35 mS later, GP2 goes high and the one-shot delay loop runs. When the one-shot delay loop falls through, GP2 is cleared to a logic low level and — if the switch is still depressed — the while(GP3) statement loops until the push-button is

## (Listing 4, continued)

```

/*****
/*  HI-TECH C SOURCE CODE FOR VOLTAGE BOOSTER MODULE
*****/
void main()
{
    TRIS = 0b00001000;    //GP3 input : all others output
    FOSC4 = 0;            //GP2 is an I/O pin
    CMCON = 0b11110111;   //comparator off:pullups off:wakeup off
    OPTION = 0b11000000;  //prescaler assigned to TMR0 @ 1:2

    while(1)              //loop forever
    {
        GP2 = 1;          //GP2 = HIGH
        TMR0 = 0x04;       //load TMR0
        while(TMR0 & 0x04); //count from 0b00000100 to 0b00001000


        GP2 = 0;          //GP2 = LOW
        TMR0 = 0x80;       //load TMR0
        while(TMR0 & 0x80); //count from 0x80 to 0x00
    } //while(1)
} //main
/*****
/*  HI-TECH C SOURCE CODE FOR ONE-SHOT MODULE
*****/
void main()
{
    unsigned int x,y;
    TRIS = 0b00001000;    //GP3 input : all others output
    FOSC4 = 0;            //GP2 is an I/O pin
    CMCON = 0b11110111;   //comparator off:pullups off:wakeup off
    OPTION = 0b11000111;  //prescaler assigned to TMR0 @ 1:256

    GP2 = 0x00;           //clear GP2
    while(1)              //loop forever
    {
        while(!GP3);      //wait for GP3 to go HIGH
        TMR0 = 0x80;       //debounce the switch closure
        while(TMR0 & 0x80); //loop for 35mS using TMR0 with prescaler @ 1:256
        GP2 = 1;          //set GP2
        for(x=0;x<0xFFFF;++x) //delay for one-shot time
            ++y;
        GP2 = 0;          //clear GP2
        while(GP3);       //wait for button release:GP3 to go LOW
        TMR0 = 0x80;       //debounce button release
        while(TMR0 & 0x80); //loop for 35mS
    }
}

```

released. The switch is again debounced when released and the one-shot-switch-debounce process repeats from the beginning statement (while(!GP3)).

Now you can see that handling pulse trains and delays with the PIC10F206 is easy to do. So far, we have enabled a crude PWM (Pulse Width Modulation) function with our LED dimmer code and the one-shot code conjures up lots of other possibilities. The same one-shot code could be used to enable a pulse stretcher or pulse shrinker. A missing pulse detector is yet another coding possibility. The bottom line is that precious microcontroller CPU cycles can be offloaded to the PIC10F206 as it can perform mundane tasks, such as debouncing switches and conditioning incoming signals.

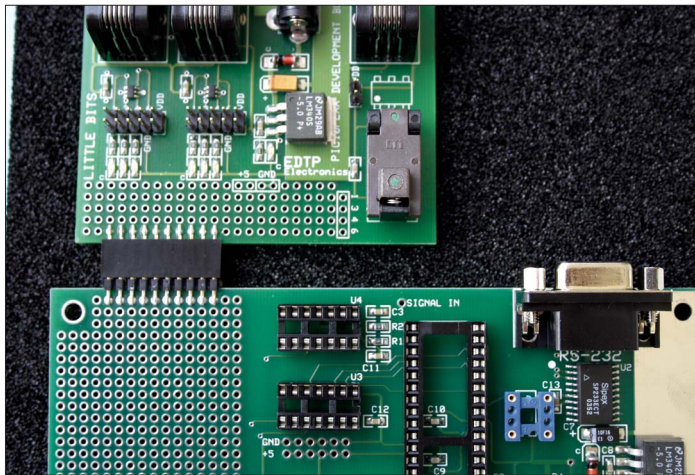

**Figure 6.** The Digital Filter Development Board is teamed up with a Little Bits to complete the realization of a PIC10F206 bit-bang serial port.

## Communicating With Little Bits

There are no USARTs (Universal Synchronous Asynchronous Receiver Transmitters) or UARTs (Universal Asynchronous Receiver Transmitters) contained within the PIC10F206 silicon. So, there's no native PIC10F206 serial

communications functionality. Just because the specialized UART hardware doesn't exist doesn't mean we can't implement a software PIC10F206 UART of our own.

In fact, we can do just that and — thanks to the HI-TECH PICC C compiler — we won't have to write any of the serial communications drivers from scratch. All of the bit-bang serial driver code that comes with HI-TECH PICC C compiler is shown in Listing 5. You can study the code in detail if you wish. However, the only things you have to know about the serial driver are the serial functions that you will use when applying the driver code. To send a character, use the putch function. To receive a character, use the getch function. A optional function called getch echoes the incoming character.

This is where the 20-pin female connector I added to my Little Bits comes into play. As you can see in Figure 6, I've called upon a Digital Filter Development Board to aid the Little Bits in getting its serial port operational. I've wired the Digital Filter Development Board's SP233ECT RS-232 IC into one of the PIC10F206 microcontrollers on Little Bits via a 20-pin male header on the Digital Filter Development Board. Only four connections are necessary, with power and ground being givens. Look again at the beginning of the code in Listing 5. You'll see that I've designated GP2 as the transmit pin and GP3 as the receive pin and specified a baud rate of 9600 bps. I've detailed the PIC10F206-to-Digital Filter


## Seetron Serial LCDs

Interface a sharp LCD display to your BASIC Stamp® or other micro-controller project with ease. No-solder wiring harnesses and easy mounting kits available too. See [www.seetron.com](http://www.seetron.com) today.

- 3.2 x 1.4 in. supertwist LCD **\$45** BPI-216N
- 2400/9600 baud serial
- Low ( $\approx 2\text{mA}$ ) current draw
- Great with BASIC Stamps®



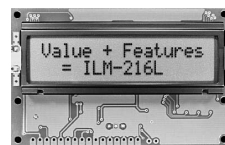- 3.2 x 2 in. backlit LCD **\$49** ILM-216L
- 1200-9600 baud serial
- Advanced protocol, 4 switch inputs
- EEPROM for configuration settings
- Favorite for OEM applications



- 3.2 x 1.4 in. graphics LCD **\$99** SGX-120L
- 2400/9600 baud serial
- Font and 15 screens in EEPROM
- Easily draw points, lines, screens



- 3 x 2 in. supertwist LCD **\$119** TRM-425L
- 1200-9600 baud serial
- ESD-protected, 4x4 keypad input
- Store up to 95 screens in EEPROM



**Scott Edwards Electronics, Inc.**  
1939 S. Frontage Rd. #F, Sierra Vista, AZ 85635  
phone 520-459-4802 • fax 520-459-0623  
[www.seetron.com](http://www.seetron.com) • [sales@seetron.com](mailto:sales@seetron.com)

More displays available,  
including bright VFDs.  
See [www.seetron.com](http://www.seetron.com)

## Wireless - 40 Miles - \$299

### New 1 Watt 9XTend Stand-Alone RF Modem

The best price-to-performance value on the market

| FEATURES                           | MaxStream's 9XTend | Low Cost Competitor | High Cost Competitor |
|------------------------------------|--------------------|---------------------|----------------------|
| <b>Price</b>                       | ★ < \$300          | ★ < \$300           | ✗ > \$1,200          |
| <b>Max. Range</b><br>line-of-sight | ★ Up to 40 Mi.     | ✗ Up to 20 Mi.      | ★ Up to 60 Mi.       |
| <b>Data Throughput</b>             | ★ 115 kbps         | ✗ 57 kbps           | ★ 115 kbps           |
| <b>Encryption</b>                  | ★ 256-Bit AES      | ✗ 56-Bit DES        | ✗ None               |
| <b>Max. Sensitivity</b>            | ★ -110 dBm         | ✗ -99 dBm           | ★ -110 dBm           |
| <b>Interference Immunity</b>       | ★ YES              | ✗ NO                | ★ YES                |

Call for aggressive volume discounts & development specials.



RS-232/485

**MaxStream**  
[www.maxstream.net](http://www.maxstream.net)  
toll-free 866-765-9885

Development Board hardware connections in the RS-232 box of Schematic 1.

Now we're ready to send some characters. I set up a Tera Term Pro session on my personal computer and tuned it in for 9600 bps. I then wrote the C code you see at the bottom of Listing 5. The code sends the string NUTS & VOLTS continually. The string I defined at the beginning of my code is actually stored in the PIC10F206's program Flash area and is automatically terminated with a null or zero character by the HI-TECH PICC C compiler.

I've pulled the psect that details how the characters in the string are stored and placed it under my code so you can see how the HI-TECH PICC C compiler handles strings in the Flash memory area. Putting the string in the program Flash memory area is a good thing, as the PIC10F206 doesn't have enough SRAM to hold the string and do other SRAM related things at the same time. Pretty clever, huh?

The null character that signifies the end of the string comes in handy, as I can simply test for it as I send characters

**Listing 5.** This code takes up almost half of the PIC10F206's program Flash. That still leaves enough room to make effective use of the serial port this code creates.

```
// *
// *   Serial port driver (uses bit-banging)
// *   for 16Cxx series parts.
// *
// *   IMPORTANT: Compile this file with FULL opti-
// *   mization
// *
// *   Copyright (C)1996 HI-TECH Software.
// *   Freely distributable.
// *   Adapted for use with the PIC10F20X by Peter
// *   Best

#include<pic.h>
__CONFIG(MCLRDIS & WDTRDIS & UNPROTECT);

//Tunable parameters
//Transmit and Receive port bits
#define SERIAL_PORT    GPIO
#define SERIAL_TRIS    TRIS
#define TX_PIN         2    //GP2
#define RX_PIN         3    //GP3

//Xtal frequency
#define XTAL            4000000

//Baud rate
#define BRATE          9600
```

(continued)

## Sources

HI-TECH Software  
HI-TECH PICC C compiler  
[www.htsoft.com](http://www.htsoft.com)

Microchip  
MPLAB ICE 2000  
PIC10F206  
MPLAB IDE  
[www.microchip.com](http://www.microchip.com)

EDTP Electronics, Inc.  
Little Bits  
Digital Filter Development Board  
[www.edtp.com](http://www.edtp.com)

# Be an FCC LICENSED ELECTRONIC TECHNICIAN

Learn at home in your spare time.



Earn up to \$100 an hour and more!



No previous experience needed!

## You can earn more money if you get an FCC License!

Not satisfied with your present income? Add prestige and earning power to your electronics career by getting your FCC Government License.

The Original Home-Study course prepares you for the "FCC Commercial Radiotelephone License" at home in your spare time.

This valuable license is your professional "ticket" to thousands of exciting jobs in: Communications, Radio-TV, Microwave, Maritime, Radar, Avionics & more...you can even start your own business!

No need to quit your job or go to school. This proven "self-study" course is easy, fast and low cost!

**GUARANTEED TO PASS** – You get your FCC License or your money will be refunded.

**Call for FREE facts now!**  
**(800) 932-4268** Ext. 220  
[www.LicenseTraining.com](http://www.LicenseTraining.com)

**COMMAND PRODUCTIONS**  
FCC LICENSE TRAINING - Dept. 220  
P.O. Box 3000 • Sausalito, CA 94966  
Please rush FREE details immediately!

or mail coupon today

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



## (Listing 5, continued)

```
//Don't change anything else
#define SCALER 10000000
#define ITIME 4*SCALER/XTAL // Instruction cycle time
#if BRATE > 1200
    #define DLY 3 // cycles per null loop
    #define TX_OHEAD 13 // overhead cycles per loop
#else
    #define DLY 9 // cycles per null loop
    #define TX_OHEAD 14
#endif
#define RX_OHEAD 12 // receiver overhead per loop

#define DELAY(ohd) (( (SCALER/BRATE) - (ohd*ITIME) ) / (DLY*ITIME) )

static bit TxData @ (unsigned)&SERIAL_PORT*8+TX_PIN; // Map TxData to pin
static bit RxData @ (unsigned)&SERIAL_PORT*8+RX_PIN; // Map RxData to pin
#define INIT_PORT SERIAL_TRIS = 1<<RX_PIN // set up I/O direction

void putch(char c)
{
    unsigned char bitno;
    #if BRATE > 1200
        unsigned char dly;
    #else
        unsigned int dly;
    #endif

    INIT_PORT;
    TxData = 0; // start bit
    bitno = 12;
    do
    {
        dly = DELAY(TX_OHEAD); // wait one bit time
        do // waiting in delay loop
            while(--dly);
        if(c & 1)
            TxData = 1;
        if(!(c & 1))
            TxData = 0;
        c = (c >> 1) | 0x80;
    }while(--bitno);
    NOP();
}

char getch(void)
{
    unsigned char c, bitno;
    #if BRATE > 1200
        unsigned char dly;
    #else
        unsigned int dly;
    #endif

    for(;;)
    {
        while(RxData)
            continue; // wait for start bit
        dly = DELAY(3)/2;
        do // waiting in delay loop
            while(--dly);
        if(RxData)
            continue; // twas just noise
        bitno = 8;
        c = 0;
    }
}
```

(continued)

out of the PIC10F206 serial port. Once I encounter a null, I know that I have sent the entire string and I send a carriage return and line feed combination. A simple delay loop is executed and the bit-bang serial process sends another NUTS & VOLTS message.

## Good Things in Small Packages

Okay, let's begin our descent and land this thing. As you have seen, lots of useful things can be done with a tiny PIC10F206, its four I/O lines, and a good C compiler like the HI-TECH PICC C compiler. The air is really clear at 23,000 feet. You have seen for yourself that using a C compiler with a tiny PIC like the PIC10F206 is not necessarily a bad thing.

Whether you code in assembler or C, the PIC10F20X series of micro-controllers is a blast to work with. I'm sure you'll want to try your hand at some tiny applications, as well. So, I'll make all of the Little Bits code in the listings available for download from the *Nuts & Volts* FTP server ([www.nutsvolts.com](http://www.nutsvolts.com)).

For those of you who want to melt some solder around a PIC10F206, either the Wahl Iso Tip portable soldering iron with a 7566-100 micro tip or a Metcal Soldering Station with a SSC-645A soldering element is perfect for the task. If you don't want to roll your own Little Bits, you can get a kit of parts or an assembled Little Bits unit from EDTP Electronics ([www.edtp.com](http://www.edtp.com)). **NV**

## (Listing 5, continued)

```

do
{
    dly = DELAY(RX_OHEAD);
    do // waiting in delay loop
        while(--dly);
    c = (c >> 1) | (RxData << 7);
}while(--bitno);
return c;
}
}

char getche(void)
{
    char c;

    putch(c = getch());
    return c;
}

/*****
** HI-TECH C SOURCE CODE FOR RS-232 MODULE
***/

const char * string = "NUTS & VOLTS";


void main()
{
    unsigned char x;
    unsigned int y,z;

    FOSC4 = 0;
    CMCON = 0b11110111;
    OPTION = 0b11001111;

    while(1) //loop forever
    {
        x = 0; //initialize character index
        do
        {
            putch(string[x++]); //send character indexed by x: increment x
        }while(string[x] != 0); //look for null character at end of string
        putch(0x0D); //send carriage return
        putch(0x0A); //send line feed
        for(y=0;y<0xFFFF;++y) //delay for a while
            ++z;
    }
}


/*****
** HOW THE STRING IS STORED IN FLASH
***/
248                                psect    strings
249 018                            u19
250 018 84E                        retlw    78      ;'N'
251 019 855                        retlw    85      ;'U'
252 01A 854                        retlw    84      ;'T'
253 01B 853                        retlw    83      ;'S'
254 01C 820                        retlw    32
255 01D 826                        retlw    38      ;' '
256 01E 820                        retlw    32
257 01F 856                        retlw    86      ;'V'
258 020 84F                        retlw    79      ;'O'
259 021 84C                        retlw    76      ;'L'
260 022 854                        retlw    84      ;'T'
261 023 853                        retlw    83      ;'S'
262 024 800                        retlw    0

```

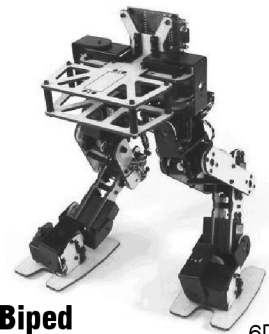


**Biped Scout**

6DOF Biped Walker

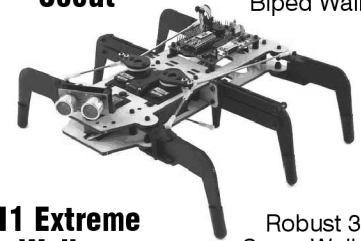

**H1 Extreme Walker**

Robust 3 Servo Walker

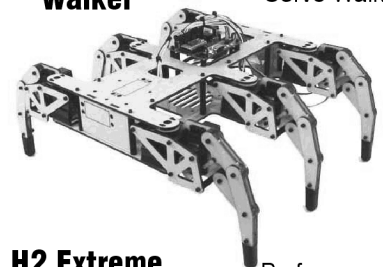

**H2 Extreme Walker**

Performance 12 Servo Walker



**Lynx 6 Robotic Arm**

Five DOF Arm



**4WD2 Rover**

Articulating Chassis

**We have many more unique robot kits. Our robots feature:**

- Precision Laser-Cut Lexan
- Preassembled Electronics
- Custom Aluminum Components
- Injection Molded Components
- Very High Coolness Factor

**Toll Free: 866-512-1024**  
**Web: www.lynxmotion.com**



# Calculating Current

## Limiting Resistor Values for LED Circuits

**A**n LED is one of those product components that just has to work. If I look at my computer from across the room and don't see its LED winking back at me, I assume it's turned off; I never expect that the LED might have burned out. There's good reason for that: When operated within specs, an LED has a lifetime of 100,000 hours or more.

The key to maximizing LED life is limiting the current that runs through it. This is frequently done with a simple resistor whose value is calculated using Ohm's Law. This article reviews how to apply Ohm's Law to single and clustered LED circuits. I have also provided an Excel spreadsheet to simplify — and speed up — the process.

### Single LEDs

When computing the value of a current limiting resistor for a single LED, the basic form of Ohm's Law —  $V = IR$  — becomes:

$$R = \frac{V_{batt} - V_{led}}{I_{led}}$$

where:

$V_{batt}$  is the voltage across the resistor and the LED.

$V_{led}$  is the forward voltage of the LED.

$I_{led}$  is the forward current of the LED.

Figure 1(a) shows an example of a single LED circuit. Incidentally,  $V_{batt} - V_{led}$  is the voltage drop across the

resistor, and  $(I_{led})^2 R$  is the power dissipated by the resistor. Calculating the power dissipation is a step that many people — hobbyists and professionals alike — tend to skip. So, what do you call a 1/8 W resistor that needs to dissipate 1/2 W? Charcoal.

### LEDs in Series

The equation above gets only slightly more complicated when you connect multiple LEDs in series. The voltage drop across the LEDs increases, reducing the voltage drop across the resistor. The current through the resistor (and the LEDs) remains the same:

$$R = \frac{V_{batt} - nV_{led}}{I_{led}}$$

where  $n$  is the number of LEDs in series. Figure 1(b) shows an example with three LEDs connected in series. The voltage drop across the LEDs is three times the voltage drop of a single LED.

### LEDs in Parallel

If you connect multiple LEDs in parallel, the current through the resistor increases (though the current through each LED remains the same). The voltage drop across the LEDs is unaffected, as is the voltage drop across the resistor:

$$R = \frac{V_{batt} - V_{led}}{mI_{led}}$$

where  $m$


is the number of LEDs in parallel. Figure 1(c) shows an example with three LEDs connected in parallel. The current through the circuit is three times the current of a single LED.

### LED Arrays

If you connect multiple LEDs in an array,

JANUARY 2005

**Figure 1.** Simple LED circuits. (a) Single LED circuit. (b) LEDs in series. (c) LEDs in parallel.

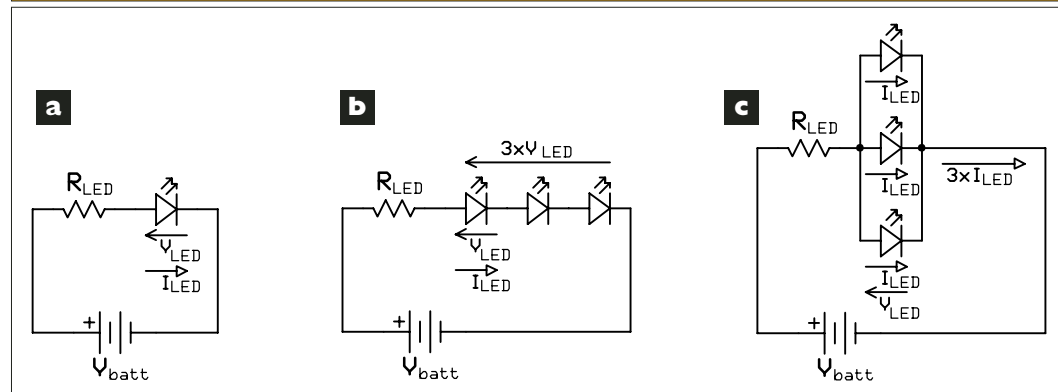



you just need to combine the serial and parallel forms of the equations:

$$R = \frac{V_{batt} - nV_{led}}{mI_{led}}$$

It's important that there are  $n$  LEDs (connected in series) in each of the  $m$  parallel branches of the circuit and that the LEDs all have the same  $V_{led}$  and  $I_{led}$ . Otherwise, all bets are off. Figure 2(a) shows four LEDs connected in such a way that the previous equation does not apply. Figure 2(b) shows one of several "proper" ways to connect four LEDs.

## Brightness Control

Brightness control is useful for gadgets that might be used under different ambient lighting conditions (outside/inside, night/day, etc.). This feature requires two resistors — one fixed ( $R_f$ ) and one variable ( $R_v$ ).  $R_f$  limits the current when  $R_v$  is at its minimum setting — usually  $0 \Omega$  — which allows maximum current to flow through the LED. The value of  $R_f$  is calculated when  $R_v = 0$ :

$$R_f = \frac{V_{batt} - nV_{led}}{mI_{led(max)}}$$

where  $I_{led(max)}$  is the maximum current you want through the LED.

Increasing the  $R_v$  setting adds resistance to the circuit, decreasing the current through the LED. When  $R_v$  is at its maximum setting, the minimum amount of current flows through the LED. The value of  $R_v$  is given by:

$$R_v = \frac{V_{batt} - nV_{led}}{mI_{led(min)}} - R_f$$

where  $I_{led(min)}$  is the minimum current you want through the LED.

## Design Steps

There are four steps to selecting the proper current limiting resistor value(s):

- Using the desired operating characteristics and LED specs, solve the appropriate equations for the

JANUARY 2005

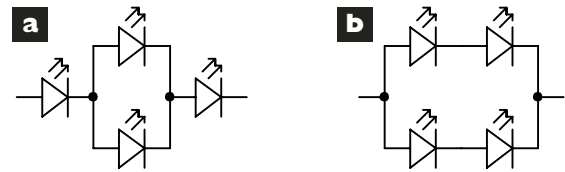


Figure 2. LED arrays.

"ideal" resistor values.

- Select appropriate "real" resistor values. If the calculations specify a  $132.27 \Omega$  resistor, the nearest "real" resistor values are  $130 \Omega$  and  $150 \Omega$  (5% tolerance). Of course, you could select other values based on what you have on hand.
- Plug the values of the resistors you selected back into the calculations to see if they will satisfy the desired operating characteristics.
- Run through the calculations using the selected resistor values at the extremes of tolerance. A  $150 \Omega$  resistor with 5% tolerance can range from  $142.5 \Omega$  to  $157.5 \Omega$  and will seldom be precisely  $150 \Omega$ . Also, calculate the current draw of the circuit and the necessary power dissipation of the resistors.

Some folks don't go through any of these steps and just guess at a value. Most go through the first two steps, which is usually fine — as long as you don't operate too close to the LED's limits, where tolerances can push you over the edge. By following all four steps, you can guarantee that your LEDs, at least, are operating safely and should last a good long time.

## Multiple Iterations Are a Drag

Calculating the proper resistors for LED circuits is pretty simple. It takes just a few moments, even when going through all four design steps. That's no big deal, if

Figure 3. Brightness control.


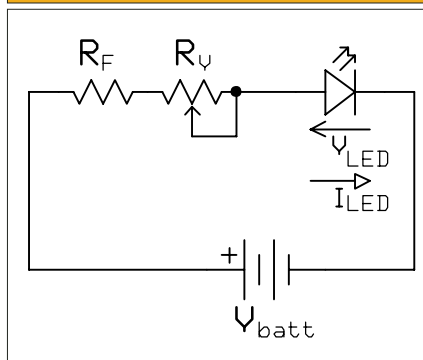


Figure 4. Ways to connect six LEDs.

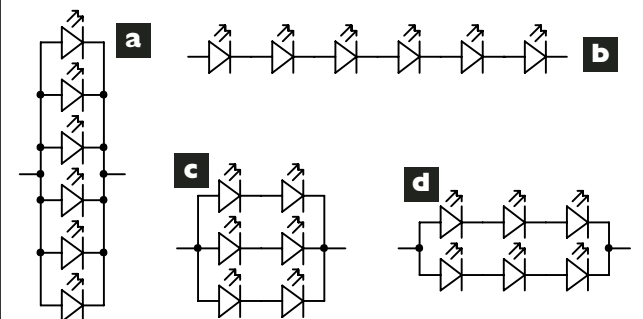

## LED Resistor Calculator

Mark V. Dobrosielski mdoobrosielski@ieee.org

### Circuit characteristics

| Parameter      | Value      |                            |
|----------------|------------|----------------------------|
| $V_{batt}$     | <b>5.0</b> | V Battery voltage          |
| $V_{led}$      | <b>1.9</b> | V LED forward voltage      |
| $I_{led(max)}$ | <b>2.0</b> | mA Max desired LED current |
| $I_{led(min)}$ | <b>2.0</b> | mA Min desired LED current |
| # leds/branch  | <b>1</b>   | # LEDs in series           |
| # branches     | <b>1</b>   | # LEDs in parallel         |

### Calculated (ideal) I & R values and suggested (real) resistor values

| Parameter        | Value  |  |
|------------------|--------|--|
| $R_{f(ideal)}$   | 1550.0 | ohm Calculated fixed resistor value              |
| $R_{v(ideal)}$   | 0.0    | ohm Calculated variable resistor value           |
| $I_{max(ideal)}$ | 2.0    | mA Max current using calculated resistor values  |
| $I_{min(ideal)}$ | 2.0    | mA Min current using calculated resistor values  |
| $R_{f(real)}$    | 1600   | ohm Corresponding "real" fixed resistor value    |
| $R_{v(real)}$    | 0      | ohm Corresponding "real" variable resistor value |

### Calculated circuit performance using selected resistors

| Parameter  | Value       | Tolerance         |  |
|------------|-------------|-------------------|--|
| $R_f$      | <b>1600</b> | ohm <b>5.0</b> %  | Selected fixed resistor value & tolerance                      |
| $R_v$      | <b>0</b>    | ohm <b>10.0</b> % | Selected variable resistor value & tolerance                   |
| $I_{max}$  | 2.0         | mA                | Max current using selected resistors with worst-case tolerance |
| $I_{min}$  | 1.8         | mA                | Min current using selected resistors with worst-case tolerance |
| $I_{batt}$ | 2.0         | mA                | Peak current battery needs to supply                           |
| $P_f$      | 0.01        | W                 | Power dissipated by fixed resistor at peak current             |
| $P_v$      | 0.00        | W                 | Power dissipated by variable resistor at peak current          |

Figure 5. View of the spreadsheet.

you only have to do it once, but what if you want to see the effect of different resistors in the circuit? What if you have an array of LEDs and you want to determine the best way to hook them up? (Figure 4 illustrates four ways to connect

six LEDs.) The calculations are still simple; you just have to do them a bunch more times. That gets tedious and that's exactly when people tend to make mistakes.

To beat the tedium and the mistakes that go with it, I've put together an Excel spreadsheet that performs all the necessary calculations — including looking up "real" resistor values. It's a real time saver!

## Using the Spreadsheet

The spreadsheet (available on the *Nuts & Volts* website at **www.nutsvolts.com**) is broken down into three sections. The first section, Circuit Characteristics, is where you enter your circuit parameters. The second section, Calculated I & R Values and Suggested Resistors, calculates the needed resistor values and suggests "real" resistors to use in the circuit. The last section, Calculated Performance Using Selected Resistors, lets you plug in resistor values (the suggested values or values of your own choosing) and calculates LED currents, power supply currents, and

resistor power dissipation. It also takes into account resistor tolerance. *Note: Values in blue boldface are the only ones you should change. Plain black text shouldn't be changed.* **NV**

Order online at:  
[www.melabs.com](http://www.melabs.com)

Development Tools for PICmicro MCUs  
*microEngineering Labs, Inc.*


Phone: (719) 520-5323  
Fax: (719) 520-1867  
Box 60039  
Colorado Springs, CO 80960

### Serial Programmer for PICmicro


**\$119.95**
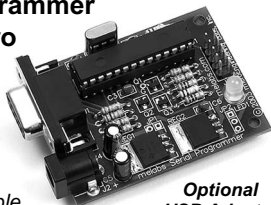
#### Includes:

Programmer  
9-pin Serial Cable  
AC Power Adapter  
ZIF Adapter for 8 to 40-pin DIP  
Software for Windows 98/Me/NT/2K/XP



Optional  
USB Adapter  
**\$39.95**

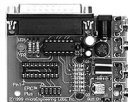

**EPIC Parallel Port Programmer**  
starting at \$59.95

### LAB-X Experimenter Boards



Pre-Assembled Board  
Available for 8, 14, 18, 28,  
and 40-pin PIC MCUs  
2-line, 20-char LCD Module  
9-pin Serial Port  
Sample Programs  
Full Schematic Diagram

Pricing from \$69.95 to \$349.95

### PICProto Prototyping Boards



Double-Sided with Plate-Thru Holes  
Circuitry for Power Supply and Clock  
Large Prototype Area  
Boards Available for most PIC MCUs  
Documentation and Schematic

Pricing from \$8.95 to \$19.95

### BASIC Compilers for PIC MCUs



Easy-To-Use BASIC Commands  
Windows 9x/Me/2K/XP Interface

**PicBasic Compiler \$99.95**

BASIC Stamp 1 Compatible  
Supports most 14-bit Core PICs  
Built-In Serial Comm Commands

**PicBasic Pro Compiler \$249.95**

Supports all PICmicro MCUs  
Direct Access to Internal Registers  
Supports In-Line Assembly Language  
Interrupts in PicBasic and Assembly  
Built-In USB, I2C, RS-232 and More  
Source Level Debugging


See our full range of products, including  
Books, Accessories, and Components at:

**[www.melabs.com](http://www.melabs.com)**



Create, Read and Write to FAT16/32 files  
Easy to use, simple protocol  
Directories supported  
Long filenames supported  
Up to 4 files open, using file handles

## SD/MMC Serial Data Module



**1-866-99 ROGUE**  
(416) 238-7054 Fax  
sales@roguerobotics.com  
www.roguerobotics.com

Everything you need to build your own...

## MOBILE ROBOT



- ♦ Sonar Units
- ♦ Web Controls
- ♦ Artificial Intelligence
- ♦ Microprocessors
- ♦ Optics
- ♦ Motor Drivers
- ♦ Vision Systems

**Zagros Robotics**  
PO Box 460342, St. Louis, MO 63146  
(314) 768-1328 info@zagrosrobotics.com  
www.zagrosrobotics.com

**Wireless A/V Transmitter/Receiver**

**140/kit** ASK-2008TR, 2.4, 1.7, 1.2 GHz, 8 Channel Wireless Systems

- Transmit range up to 800'
- 12 Channel Available
- Built-in channel switcher for auto scan
- 1000 mW booster optional


**ASB-2000 2.4 GHz Power Amplifier**

- Amplifies 2.4 GHz radio signal up to 1 W output
- 10-40 mW power input
- Size: 2" x 2" x 3/4" appr.
- Power Supply included

**\$129/ea**

**Matco, Inc.** www.matco.com  
Sales: (800)-719-9605 Fax: (847)-303-0660

## SMT PROTOTYPING ADAPTERS

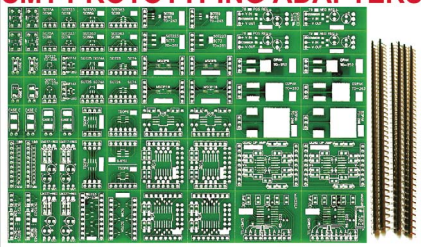

Snap-Apart™ PCB's with .100" pin strips.  
Dozens of assorted adapters on each PCB.  
A variety of PCB's with patterns front & back.

SOIC PLCC SSOP QFP DPAK SOT23 MSOP QSOP SC90 D2PAK  
TSSOP SOT89 D3PAK SOT143 TSOP SC70 SOT88 and many more.

**Beldyn Dynamic Systems Inc.**  
(714) 630-8024 www.beldynsys.com  
- Rapid Development Solutions for the Technical Professional -

## Non-Ladder Logic PLC's

### BSI032ex



**www.bsi0.us**



**The Pocket Programmer** Only \$149.95

The portable programmer that uses the printer port instead of an internal card, with easy to use Windows software that programs E(E)prom, Flash & Dallas Ram.

**Intronics, Inc.** • Tel. (913) 422-2094  
Box 12723 / 612 Newton / Edwardsville, KS 66111  
Add \$8.00 COD  
WWW.IN-KS.COM Visa/MC/Amex/Disc

# Electronics Showcase

**www.Primecell.com**

## Battery rebuilding service

Dead Batteries? Don't toss them. Send them to us - our rebuilds are better than original specifications.



**Tools**  
Hilti Skill Milwaukee  
Panasonic B&D DeWalt  
Makita All 2-36 Volts

**Electronics**  
Bar Code Scanners  
Surveying Printers  
Laptops  
Photography



**Radios**  
APELCO UNIDEN  
G.E. ICOM KENWOOD  
MOTOROLA MIDLAND  
MAXON YAESU  
ALINCO

Visit [www.primecell.com](http://www.primecell.com) for important details  
24 Hr Secure recorder tel-fax (814) 623 7000  
Quotes email: [info@primecell.com](mailto:info@primecell.com)  
Cunard Assoc. Inc. 9343 US RT 220 Bedford PA 15522

## PRINTED CIRCUIT BOARDS

**QUALITY PRODUCT FAST DELIVERY COMPETITIVE PRICING**

- \* UL approved
- \* Single & Double sided
- \* Multilayers to 8 layer
- \* SMOBC, LPI mask
- \* Reverse Engineering
- \* Through hole or SMT
- \* Nickel & Gold Plating
- \* Routing or scoring
- \* Electrical Testing
- \* Artwork or CAD data
- \* Fast quotes

**10 pcs (3 days) 1 or 2 layers \$249**  
**10 pcs (5 days) 4 layers \$695**  
(up to 30 sq. in. ea.)  
includes tooling, artwork, LPI mask & legend

**PROTOTYPE THROUGH PRODUCTION**  
**PULSAR, INC.**  
9901 W. Pacific Ave.  
Franklin Park, IL 60131  
Phone 847.233.0012  
Fax 847.233.0013  
Modem 847.233.0014

*We will beat any competitor's prices!!!*  
[yogii@flash.net](mailto:yogii@flash.net) • [flash.net/~yogii](http://flash.net/~yogii)

## ActiveWire® USB Simple USB Interface!



- Works with MacOS 8/9, Win98/2K/ME/XP
- FreeBSD and Linux!
- 24Mhz CPU core with USB
- Firmware downloadable via USB
- 16 bit parallel Input/Output
- See web-site for add-on boards
- All drivers, manuals, demos are on our web-site for immediate download!

**\$59 plus shipping**

**ActiveWire, Inc.**  
[www.activewireinc.com](http://www.activewireinc.com)  
ph +1.650.465.4000 fax +1.209.391.5060

## QKITS.COM

**THE PCS500!**

**2 CHANNEL PC OSCILLOSCOPE for just \$389.95!**  
Price is in US dollars.



- 9 volt adaptor
- 2 test leads
- PC parallel cable
- sampling frequency: real-time: 1.25KHz to 50MHz
- repetitive: 1 GHz
- spectrum analyzer
- transient recorder

**1-800-GO 4 KITS**  
**GREAT PRICES, GREAT SHIPPING RATES**  
49 McMichael St., Kingston, ON, K7M 1M5 CANADA

ANDRE LAMOTHE'S

## XGAMESTATION

LEARN STEP-BY-STEP HOW TO BUILD AND DESIGN YOUR OWN VIDEO GAME CONSOLE!

Design inspired by the Atari 2600, Apple II & Commodore 64!



**INCLUDES:**

- Great for Hobbyists AND Students!
- The Fun Way to Learn Embedded Systems!
- Fully Assembled XGS Micro Edition Unit!
- Complete Software Development Kit!
- Tools, Demos & Utilities!
- eBook on Designing the XGS Console!
- Cables and Power Supply Included!

Powered by the Ubicom SX52 @ 80 MIPS and Parallax SX-Key Compatible!

**Huge eBook Included!**

**COMPLETE KIT**

**www.XGAMESTATION.COM**  
(925) 736-2098 SUPPORT@NURVE.NET

## CUSTOM PLASTIC PARTS

Mold manufacturing. Production of injection molded parts. No order too small or too big. Very competitive on high labor parts. For very small orders we can inject your parts on manual low pressure machines.



## CUSTOM METAL STAMPING

We manufacture our own tooling  
Site: [www.vandvmachy.com](http://www.vandvmachy.com)  
email: [victor@vandvmachy.com](mailto:victor@vandvmachy.com)

USA Office: V & V Mach. and Equip. Inc. 14019 Whispering Palms Dr. Houston, TX 77066, PH. 281 397 8101, Fax. 281 397 6220.  
Mexico Plant: Marketing Tech. De Mex. SA de CV. Alamo 93 Cuatro Pisos, Santa Monica, Tlal. Edo. De Mexico, 54040 Tels. 011 52(555) 314 5325 & 011 52(555) 360 3648 Fax. 011 52(555) 361 5996.



# The Nuts & Volts Hobbyist Bookstore

**Don't miss the special on all books by Myke Predko ...**


## Handbook of Microcontrollers by Myke Predko

A straight-talking guide to all the most common eight-bit microcontrollers now in use, TAB *Electronics Microcontroller Handbook*, edited by Myke Predko, tells you everything you need to know about the Intel 8051, Motorola 68HC05, Microchip PIC, Atmel AVR, and Parallax Stamp MCUs. Complete with applications and recommendations — from automotive parts and personal computers to household appliances and toys — this authoritative tool shows how each MCU works and interfaces with peripheral devices, explains features, architecture, and the instruction set for the built-in processor, and serves up example applications plus all the data necessary to develop them. **\$79.95**



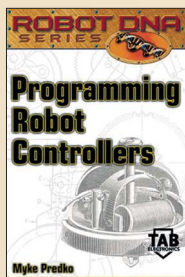
## Robot DNA Series: Programming Robot Controllers by Myke Predko

In this innovative addition to the Robot DNA Series, author Myke Predko tells you everything you need for your robot to perform up to specification and expectation — and for you to fully understand how robot controllers are programmed using the versatile Microchip PICmicro PIC16F627. All you need to get started are inexpensive off-the-shelf parts and the "C" programming language compiler, included on the CD-ROM. **\$24.95**



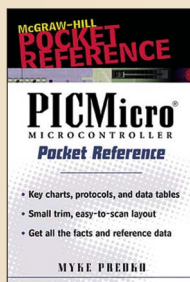
## PICMicro Microcontroller Pocket Reference by Myke Predko

Device, code, and circuit data on one of the most popular microcontrollers around — it's in your pocket with this guide. You'll never again get stuck in the World Wide Wait or shuffle through coffee-stained printouts, looking for the facts you need. Short on verbiage and long on facts, this is the ideal data tool for the experienced applications designer. **\$29.95**


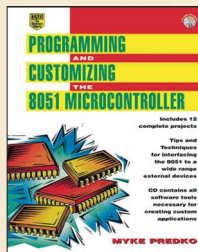
## Programming & Customizing the 8051 Microcontrollers by Myke Predko


For work or fun — projects, exercises, and insights on the world's most popular microcontroller. Over 30 experiments and 13 complete projects demonstrate the 8051's capabilities. The CD-ROM gives you all the software you need to begin developing 8051 applications. This tutorial/disk package is unique in providing you with a complete understanding of the 8051 chip compatibles, along with all the information needed to design and debug tailor-made applications. *Programming & Customizing the 8051 Microcontroller* details the features of the 8051 and demonstrates how to use these embedded chips to access and control many different devices. **\$44.95**


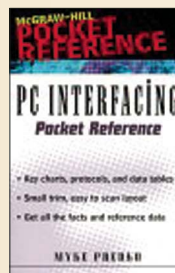
## PC Interfacing Pocket Reference by Myke Predko


PC interfacing answers — in 60 seconds or less! The ultimate at-a-glance data finder for PC hardware and software engineers, *PC Interfacing Pocket Reference* packs everything skilled developers need — traditional ASCII tables, memory and register addresses, and instruction sets, plus BIOS, MS-DOS, DPMI, and Windows APIs. You also get reference information for the leading PC programming languages — PC assembly, BASIC, C, and C++ — as well as time-saving code snippets to use for developing your own applications. What's more, you'll find:

- Sample Windows device drivers (.VxDs, .WDMs, and .DLLs)
- Hardware addresses and device block diagrams with connector pinouts
- ISA, PCI, and USB bus information, along with Plug and Play and Interrupt and DMA interfacing
- Conforms to Intel/Microsoft "PC/9x" baseline specification — so you know information is current **\$59.95**


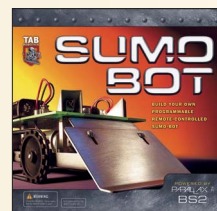
## SUMO BOT — Build Your Own Remote-Controlled Programmable Sumo-Bot by Myke Predko

Here's a fun and affordable way for hobbyists to take their robot building skills to the next level and be part of the hottest new craze in amateur robotics — Sumo competition.




Great for ages 14+, the kit comes complete with:

- Pre-assembled PCB
- Multi-function, dual channel remote control
- Robot hardware, including collision-sensing infrared LED and receivers
- CD-ROM with programming instructions and file chapters of robot building tips and tricks
- A built-in Parallax BASIC Stamp 2 and prototyping area allowing hobbyists to create their own robot application without having to purchase additional Parallax products

Powered by four AA batteries (not included) and featuring a built-in infrared remote control, the Sumo-Bot is pre-programmed with the behavior "built-in" to jumpstart custom applications. **\$99.95**
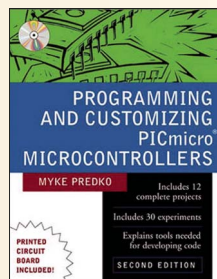
## Programming & Customizing PICMicro Microcontrollers by Myke Predko

This book is a fully updated and revised compendium of PIC programming information. Comprehensive coverage of the PICMicros' hardware architecture and software schemes will complement the host of experiments and projects making this a true "learn as you go" tutorial. New sections on basic electronics and basic programming have been added for less sophisticated users, along with 10 new projects and 20 new experiments. New pedagogical features have also been added, such as "Programmers Tips" and "Hardware Fast FAQs." The CD-ROM contains all source code presented in the book, software tools designed by Microchip and third party vendors for applications, and the complete data sheets for the PIC family in PDF format. **\$49.95**




**WE ACCEPT VISA, MC, AMEX,  
and DISCOVER**  
Prices do not include shipping and  
may be subject to change.  
**Ask about our 10% subscriber  
discount on selected titles.**

**Call 1-800-783-4624 today! Or  
order online at [www.nutsvolts.com](http://www.nutsvolts.com)**

**... Get 10% off your purchase now through Feb. 28, 2005!**

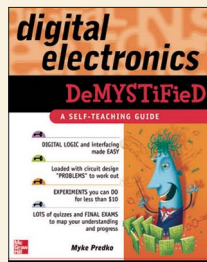
### Digital Electronics Demystified by Myke Predko

Now, anyone can gain a deeper understanding of digital electronics — without formal training, unlimited time, or a genius IQ. In *Digital Electronics Demystified*, electronics expert and author Myke Predko provides a totally painless way to learn enough digital logic and electronics to build your own projects! With *Digital Electronics Demystified*, you master the subject one simple step at a time — at your own speed. This unique guide offers problems at the end of each chapter and section to pin-point weaknesses and a 100-question final exam to reinforce the entire book. So, if you're looking for an enjoyable route into digital logic and electronics, let *Digital Electronics Demystified* be your shortcut! **\$19.95**



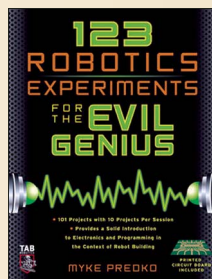
### 123 Robotics Experiments for the Evil Genius by Myke Predko

This book provides 123 steps needed to bring out the genius in every basement hobbyist! If you enjoy tinkering in your workshop and have a fascination for robotics, you'll have hours of fun working through the 123 experiments found in this innovative project book. More than just an enjoyable way to spend time, these exciting experiments will also provide a solid grounding in robotics, electronics, and programming. Each experiment builds on the skills acquired in those before it, so you develop a hands-on, nuts-and-bolts understanding of robotics — from the ground up. Don't miss out on these imaginative experiments that teach the basics! **\$24.95**



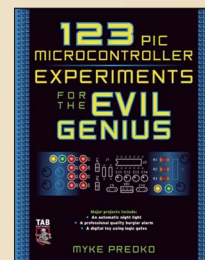
### 123 PIC Microcontroller Experiments for the Evil Genius by Myke Predko

Microchip continually updates its product line with more capable and lower cost products. They also provide excellent development tools. Few books take advantage of all the work done by Microchip. *123 PIC Microcontroller Experiments for the Evil Genius* uses the best parts and does not become dependent on one tool type or version to accommodate the widest audience possible. Building on the success of *123 Robotics Experiments for the Evil Genius*, as well as the unbelievable sales history of *Programming and Customizing the PIC Microcontroller*, this book will combine the format of the evil genius title with the following of the microcontroller audience for a sure-fire hit. **\$24.95**




**Check out these other hot titles from the Nuts & Volts Bookstore!**

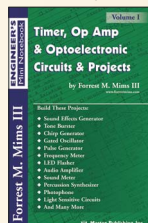
### Engineer's Mini Notebook Collection by Forrest M. Mims III




Volume 1 features more than two dozen 555 timer circuits that you can build. **\$10.95**

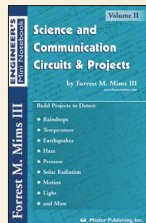

Volume 2 — Study rain, lightning, clouds, sunlight, water, temperature, and much more! **\$10.95**

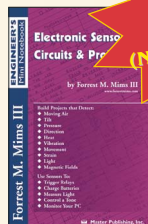

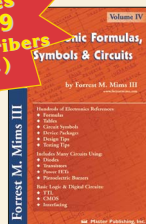Volume 3 — Learn about important sensors and use them to build circuits and projects. **\$10.95**




Volume 4 includes frequently used electronic formulas, tables, circuit symbols, and more! **\$10.95**

**All Four Volumes  
\$39.99  
(NV subscribers  
ONLY!)**

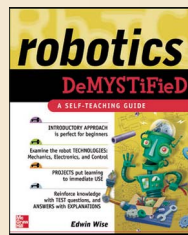
### Robotics Demystified by Edwin Wise

There's no easier, faster, or more practical way to learn the really tough subjects. McGraw-Hill's *Demystified* titles are the most efficient, interestingly written brush-ups you can find. Organized as self-teaching guides, they come complete with key points, background information, questions at the end of each chapter, and even final exams. This complete self-teaching guide takes an introductory approach to robotics, guiding readers through the essential electronics, mechanics, and programming skills necessary to build their own robot. **\$19.95**



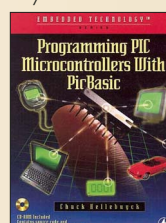
### Programming PIC Microcontrollers with PICBASIC by Chuck Hellebuyck

This comprehensive tutorial assumes no prior experience with PICBASIC. It opens with an introduction to such basic concepts as variables, statements, operators, and structures, followed by a discussion of the two most commonly used PICBASIC compilers. **\$49.99**



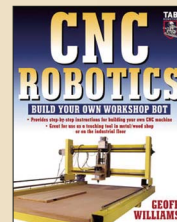
### CNC Robotics by Geoff Williams

Written by an accomplished workshop bot designer/builder, *CNC Robotics* gives you step-by-step, illustrated directions for designing, constructing, and testing a fully functional CNC robot that saves you 80% of the price of an off-the-shelf bot — and can be customized to suit your purposes exactly because you designed it. **\$34.95**


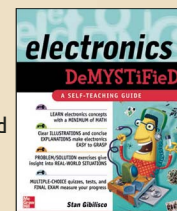
### Electronics Demystified by Stan Gibilisco

Best selling *Demystified* author and electronics expert Stan Gibilisco has penned the perfect introductory book for consumers, hobbyists, and students alike. Coverage includes topics, such as current and power supplies, wireless, digital principles, measurement and monitoring, transducers and sensors, and more. **\$19.95**



If you don't see what you need here, check out our online store at [www.nutsvolts.com](http://www.nutsvolts.com) for a complete listing of the titles available.



# CLASSIFIEDS

## CLASSIFIED ADVERTISING

\$50.00 Per Inch — No extra charge for color (Limited time offer).

Classified ads must be paid in full prior to the closing date. Visa/MC/Amex accepted. Payment for ads received after the closing date will cause the ad to be placed in the following issue, at our discretion. Minimum charge is one inch with half-inch increments.

No proofs will be sent. Ads to be typeset by Nuts & Volts must be received by the closing date. Supplied ads must be received by the artwork due date.

Call the office at 951-371-8497 or Email [classads@nutsvolts.com](mailto:classads@nutsvolts.com) for closing dates, available sizes, and special prepay discount offers.

## Components



**RF PARTS™ CO.**  
From Milliwatts to Kilowatts<sup>sm</sup>

Tubes, Transistors, Power Components.  
Email: [rpf@rfparts.com](mailto:rpf@rfparts.com) • Web: [www.rfparts.com](http://www.rfparts.com)  
**800-737-2787 Fax 888-744-1943**


## Miscellaneous Electronics For Sale

**MAKE SUPER STRONG 3D PARTS FAST**

**SHAPELOCK PLASTIC™**

RAPIDLY CREATE PROTOTYPES, PARTS, SCULPTURES, BRACKETS, HOUSINGS, MOLDS  
AMAZING PLASTIC MELTS IN HOT WATER, LOCKS RIGIDLY AT ROOM TEMPERATURE  
INCREDIBLY TOUGH, LIGHTWEIGHT, MACHINEABLE, PAINTABLE, INEXPENSIVE  
SHAPE BY HAND AND RESHAPE REPEATEDLY **WWW.SHAPELOCK.COM**

**Floating Point Coprocessor**

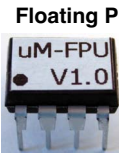

8-pin DIP or SMT  
uP compatible  
SPI interface  
32-bit IEEE 754  
32-bit integer  
Math functions  
User defined functions

**www.micromegacorp.com**

**CStamp™**

ADC PWM char  
int long float

Small format computers in 'C'  
**www.cstamp.com**

**RS485/422/232/TTL**

**ASC24T \$45**

- Converters
- Repeaters
- Fiber Optics
- Digital I/O
- Multidrop RS232
- Custom Units
- Auto TX Enable



**OVER 4,300 ITEMS IN STOCK**

**Surplus & Refurbished Electronic Equipment Parts & Accessories**

Audio, Communication, Computer, Telephone, & Video Equipment. Repair Parts & Service Manuals.

**SMC ELECTRONICS**  
**www.smcelectronics.com**

**RF Transistors, Aluminum Boxes, Heat Sinks, Copper Boards, Transformers**

**25C1969 25C2879 SD1446 25C2290**

See our website for other products  
**www.westgateparts.com**  
Westgate 1-800-213-4563

**Education**

**Affordable Robotics Training Courses in:**

**Extensive Interface Product Line**

RS232 "Extension Cords"  
Up to 115.2 Kbps, 4000 ft. ++  
Large Multidrop Networks.  
Isolated Units. Smart Units  
Remote Relay "Extension Cords"

**On Sale Now**

Cordless Telephone Battery Packs  
**50 - 75% OFF RETAIL PRICES!**

**FREE 120 Pg CATALOG**

Electronic components, kits, test equipment, tools, and supplies for hams, hobbyists, and businesses. Many hard-to-find items like variable capacitors, vernier dials, coil forms, magnet wire, and toroids.

Ocean State Electronics  
**www.oselectronics.com**

**Basic Electronics**  
**Digital Electronics**  
**Relay Control**  
**Servo Controllers**  
**PLC Systems**  
**Hydraulic Systems**

From Basic to Advanced!  
**WWW.UCANDO-CORP.COM**  
**1-800-678-6113**

**Call the RS485 Wizards at (513) 874-4796**

**RES R.E. Smith**  
**www.rs485.com**

**Robotics**


**ARobot Kit** from Arrick Robotics uses the Basic Stamp II. Quality metal construction. Easy to assemble and very expandable.  
**\$235.00**  
**www.robotics.com/arobot**

**Scientific Organizations**

UCANDO VCR Educational Products Co.  
(Est. 1988)

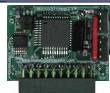**Microcontrollers**

**MicroStamp11**  
World's Smallest 68HC11 Microcontroller Module!



- telemetry
- microrobotics
- smart toys
- animatronics
- model railroading
- home automation

**ROBOTIC CONTROLLERS**

Robot Bases. PIC, OOPic, Stamp and servo controllers. New Walking Machine Controller. Chips, kits, assembled.

**www.oricomtech.com**

**Amateur Scientists Unite!**

**www.sas.org/unite**

**Vacuum Tubes**

**WANTED**

To buy **COMPLETE** \*vacuum tube collections, **ANY** quantity. Will buy new, new w/o boxes, and used. We buy all types and will not cherry pick your collection. Will travel to inspect and pick up large hoards.

Paul, Sound Ideas, 3215 NW 13th Street, Gainesville, FL 32609.  
**pwb@soundideasstereo.com**  
\*please list tubes in the note line of your email  
**352-378-0192**  
FAX #1 352-371-1791  
FAX #2 352-336-6821  
(10 am-7 pm EST M-F, 10 am-5 pm Sat)

**Spark Fun Electronics**

**Specializing In:**  
Serial LCD's and Accelerometers  
PIC, AVR, MSP, and LPC products  
Development tools for hobbyists and professionals.

Spark Fun electronics is the largest **OLIMEX** dealer in North America.

**www.sparkfun.com**

**Join our ONLINE electronics forums!**

**www.nutsvolts.com**

\* includes MicroStamp11, manual, PC software (assemblers, SBASIC compiler, MicroLoad utility, and sample programs), serial cable, Docking Module, & accessories.

**www.technologicalarts.com**  
**Toll-free (USA & Canada): 1-877-963-8996**  
Visa • MasterCard • Discover • Amex



# CLASSIFIEDS

## Connectors Wire/Cable

**The RF Connection**  
213 N. Frederick Ave., Ste. 11N  
Gaithersburg, MD USA 20877  
<http://www.therfc.com/>

### Complete Selection of MIL-Spec Coax, RF Connectors and Relays

UG-21B/U N Male for RG-213/214 \$5.00  
UG-21D/U N Male for RG-213/214 \$3.25  
N Connectors for 9913/Flexi4XL/9096  
UG-21B/9913 .....\$6.00 / Pins Only.....\$1.50  
UG-21D/9913 .....\$4.00 / Extra Gasket.\$0.75  
Amphenol 83-1SP-1050 PL-259 \$0.90  
UG-176/U Reducer RG-59/8X, \$0.25  
or 5/\$1.00  
UG-175/U Reducer RG-58/58A, \$0.25  
or 5/\$1.00  
Silver Teflon PL-259/Gold Pin, \$1.00  
or 10/\$9.00

MIL-Spec Coax Available (Teflon, PVC IIA)  
New Product: Belden 9913F, 9913 with  
High Density PE Foam dielectric,  
stranded center cond. and Duobond  
III Jacket \$0.80/ft. or \$76.00/100ft.  
Also New: 9092, RG8X with Type II Jacket.  
Intro Price .....\$23.00/100ft.

### Call for Specials of the Month

Full Line of Audio Connectors for Icom,  
Kenwood, and Yaesu  
8 Pin Mike Female \$2.50  
8 Pin Mike Male Panel \$2.50  
13 Pin DIN for Kenwood \$2.75  
8 Pin DIN for Icom \$1.00  
8 Pin DIN for Kenwood \$1.50

Prices Do Not Include Shipping

Orders **800-783-2666**  
Info **301-840-5477**  
FAX **301-869-3680**

## Audio/Video

[www.matco.com](http://www.matco.com)

### 2 Input Digital Video Web Server

DVR-1000-VS allows up to  
2 composite video sources  
for broadcast on the Internet,  
10/100 Base-T network  
interface, Accessible via  
Internet or LAN, Fixed or  
Dynamic IP address, Auto e-mail warning or image  
FTP when alarm triggered, 15 fps, Built-in Auto  
Network Reconnection function, IE Browser display  
**(800)719-9605 sales@matco.com**

[www.matco.com](http://www.matco.com)

### 4 Channel Network DVR

IP Solution **DVR-2200-W**  
**\$499/ea**  
30 fps full size/120  
fps quad size; Up  
to 250 GB optional HDD; Dynamic or statistic IP;  
Internet accessible; Wavelet compression format;  
Alarm input/output; Video loss detection; Multiple  
quick search; POP/PIP; RS-232, RS-485 comm.  
**(800)719-9605 sales@matco.com**

[www.matco.com](http://www.matco.com)

### Real Time 4 Channel PC Based Digital Video Capture Card

**Internet Accessable**  
**Real Time DVRC-TD4**  
120/120 fps, 320 x 240,  
Local & Remote PTZ  
control, 4 BNC Video Input,  
Plug and Play  
**\$69/ea**  
**(800)719-9605 sales@matco.com**

[www.matco.com](http://www.matco.com)

### Pocket Digital Video Recorder

Wired Remote  
Control  
- Built-in HDD for 40hrs real-  
time recording in MP4  
- Wired button & IR Remote  
Control  
- A/V in/out, USB interface  
- 3.5" TFT LCD monitor  
- 5-1/8" x 3-3/8" x 13/8"  
- Weight 0.67 Lb.  
**\$499**  
**(800)719-9605 sales@matco.com**

## Amateur Radio

### ZAP CHECKER MODEL 270

#### WIRELESS INSTALLATION METER

for WIFI, WLANs  
& SURVEILLANCE

- Aims and Aligns Antennas
- Tests Transmitter/Antenna Output
- Measures Baseline RF and RFI
- Identifies HOT and COLD spots
- Finds Hacker Sites & Cable Leaks
- Optimizes Hub Placement

**\$329** w/ directional 1.8-4.5 GHz Ant.  
(+ \$7.50 CA Residents add 8.25% tax)

**ALAN BROADBAND CO.**  
93 ARCH ST., REDWOOD CITY, CA 94062  
TEL: (650) 369-9627 FAX: (650) 369-3788

[WWW.ZAPCHECKER.COM](http://WWW.ZAPCHECKER.COM)

### PROFESSIONAL EAVESDROPPING DETECTOR

2.4 GHz BUGS detected at 100 + feet

### ZAP CHECKER MODEL 270

with 2.4 GHz YAGI ANTENNA  
**\$549**

- DETERMINES DIRECTION
- SUPER FAR-FIELD DETECTION
- HOMES-IN & PINPOINTS LOCATION
- 10 MHz - 4.5 GHz BANDWIDTH - 70 dBm at 2.4 GHz

**ALAN BROADBAND CO.**  
(650) 369-9627 (888) 369-9627 FAX: (650) 369-3788

[WWW.ZAPCHECKER.COM](http://WWW.ZAPCHECKER.COM)

Radio Scanners  
Shortwave Radios  
CB & Amateur Radios  
Satellite Accessories  
Satellite Radios  
Satellite FTA Receivers  
Satellite C&Ku Bands Accessories  
Weather Radios  
Radar Detectors  
GPS  
Frequency Counters  
Power Supplies  
Handheld Radios  
Camcorders

Online Catalog Only  
[www.bjelectronics.com](http://www.bjelectronics.com)  
**914-665-3241**

Subscribe today!

[www.nutsvolts.com](http://www.nutsvolts.com)

## SCSI

I-U320 50Pin-68Pin-80Pin

1 to 8 Bay Case Enclosures  
Adapters Cables Terminators

Low Prices - Qty Discounts!  
(Also FireWire, USB, Video)

[www.mcpb.com](http://www.mcpb.com)

Mfg. Custom Data/Computer Cables

Network, Coaxial, Fiber Optics

Wholesale & Retail

**R & D Electronic Supply**

714-979-1834

3301 S. Harbor #108, Santa Ana, CA

Visit us at [www.rdelectronic.com](http://www.rdelectronic.com)

## Computer Hardware Wanted


### DEC EQUIPMENT WANTED!!!

Digital Equipment Corp.  
and compatibles.  
Buy - Sell - Trade

CALL KEYWAYS 937-847-2300  
or email [buyer@keyways.com](mailto:buyer@keyways.com)
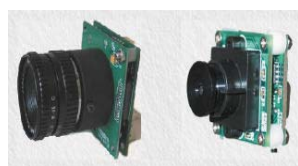
## CCD/Cameras/Video

USB 2.0 Camera module with SDK  
Mega pixel high-speed USB2.0 camera module.  
Capture size from 320x240 to 1280x1024 at real  
time speed. Complete SDK, highly customizable  
and flexible. On board hardware resources. Price  
from \$89 to \$169. Suitable for all kinds of  
computerized image capturing project.



For more information, visit our website

[www.fclab.com](http://www.fclab.com)

## Design/Engineering Services

OK, so now we have the world's smallest  
Microprocessor in SOT 23-6 pin, smallest



Op Amp in SOT 23-5 pin,  
smallest Power FET in  
SOT 23-4 pin. But, how

do you work with them  
without spending an

arm and a leg??? ONE PASSircuit™!

[www.onepasinc.com](http://www.onepasinc.com)

**Your Idea on a budget**

Product Development  
Electrical Design - Firmware  
Far East Manufacturing - Prototyping  
[www.elementinc.com](http://www.elementinc.com) 303-466-2750

\*Circuit board layouts

\*Prototype assemblies

[WWW.OSPREYELECTRONICS.COM](http://WWW.OSPREYELECTRONICS.COM)

Convert your sketch or print into a quality  
pcb for a reasonable price. Visit us on  
the web or call Osprey Electronics at  
(208) 665 1888 (USA)

## Military Surplus

### ELECTRONIC MILITARY SURPLUS



### FAIR RADIO SALES

WEBSITE: [fairradio.com](http://fairradio.com)

E-MAIL: [fairradio@fairradio.com](mailto:fairradio@fairradio.com)

PHONE: 419-227-6573

FAX: 419-227-1313

2395 St Johns RD - Box 1105

Lima, OH 45802

VISA, MASTERCARD, DISCOVER

Address Dept. NV

### 2000 WATT SOLA REGULATOR

Sola CVS 2000 Watt Constant Voltage  
Transformer provides a very well regu-  
lated sinusoidal waveform that is iso-  
lated from variations and disturbances  
in the input voltage. Also provides  
isolation and step-up/step-down to  
allow for various input/output voltages;  
Input 95-130V/175-235V/190-260V/380-520  
60Hz. Output 120/240VAC 60Hz  
2000VA. 17.8x11.4x9.6, 115 lbs sh. Unused, \$250 ea, 2/\$450

### WHEATSTONE BRIDGE

ZM-4 Wheatstone Bridge used to  
measure DC resistance.  
Resistance measurement  
range 1 ohm to 1,011 M ohms  
+/-0.15%. As a resistance sub-  
stitution box it is adjustable in  
1 ohm steps from 0-10110  
ohms. The current limit of the  
resistors is 15-500ma depend-  
ing on setting. Galvanometer indicates balance in test  
circuit. Requires three "D" batteries. Also 22.5 to 200  
VDC for more accurate readings above 1000 ohms.  
5.8x7.3x8.8, 12 lbs sh. Used Reparable, \$34.50  
Used Checked, \$49.50; Manual repro, \$12.00

Allow money for shipping on merchandise.

**SEND FOR OUR LATEST CATALOG !!**

Radios - Test Equipment - Tubes - Antennas

# CLASSIFIEDS

## Security

[www.matco.com](http://www.matco.com)  
**OEM Available**  
**Miniature CMOS Camera**  
**CML-100/CMP-101**  
 1/4" CMOS, 380 TVL,  
 3 Lux/f2.0, 3.6/5.5mm Lens  
 B/W: \$29/ea Color: \$39/ea  
**Color Mini Pinhole Camera**  
**BX-123LC/PC**  
 SONY 1/3" CCD,  
 380 TVL, 0.1 Lux/f2.0,  
 3.6 mm Lens \$69/ea  
 Size: 0.9" X 0.9" X 0.5" (with Audio)  
**Super Hi-Res Color Lens Box Camera**  
**BX-130LC-HR**  
 SONY 1/3" CCD,  
 470 TVL,  
 0.4 Lux/f2.0,  
 3.6 mm Lens  
 \$189/ea  
 (800)719-9605 sales@matco.com

**consumertronics.net**  
**Hi-Tech Survival Offers!**  
 Electronics, security, energy,  
 computers, Net, phones, medical,  
 legal, financial, weird. **Cat.\$1**

## Membrane Keyboards/Switches

**CUSTOM MEMBRANE  
KEYBOARDS / SWITCHES**



- 1 TO 2 WEEKS TURNAROUND
- VERY COMPETITIVE PRICING
- Ex.: (5) 4-switch keyboards for \$395.00
- Custom metal backplates, cases and assemblies
- Electronic assemblies/graphic overlays

**Picofab Inc.**  
 Tel: (418) 622-5298  
 Toll free: 1-888-408-4780  
 Email: sales@picofab.net

## Printer Supplies

**Hard-to-find  
Printer Supplies**

## Surveillance Equipment

**Buy Direct, Low Prices**  
**Spy Cameras, Underwater Cameras**  
**Vehicle Tracking, Telephone Recorders**  
**Phone Bug Detectors**  
**www.MJelectronics.com**  
**Tel: 914-699-2294**

[www.matco.com](http://www.matco.com)  
**18 Ch 12 VDC Power Distribution Box**  
 \$99/ea  
 12 VDC regulated. Total  
 current 6A. 18 outputs, 333  
 mA per terminal, 18 terminal  
 blocks, Fuse on each  
 channel, 18 female power  
 connectors on PCB board  
 for easy connect to camera  
 cable. 16"W X 9.5"H X 3.5"D  
**XF250DC-6A/18**  
 (800)719-9605 sales@matco.com

## Card-Access

**Magstripe**  
**Proximity**  
**Smart-Card**

- Low-cost access ctrl.
- Expandable system
- Door/gate relay control
- Windows host software
- USB & RS-485 comm.
- Controllers from \$69
- Systems under \$400
- Reseller discounts

[www.kadtronix.com](http://www.kadtronix.com)

## Batteries/ Battery Chargers

### Smart Battery Charger

FOR GEL-CELLS or  
LEAD ACID BATTERIES

**New &  
Improved**



Call us TODAY to start your  
subscription to **SERVO Magazine!**  
**800-783-4624**

## Plans/Kits/ Schematics

### Five Volt DC 100mA Kit

- Measures 1-3/4 x 1-5/8.
  - Kit contains bridge rectifier, all filter  
caps, and LM78L05 regulator.
  - \$9.95 ea. postpaid.
- G. JOSEPH FINN, JR.**  
 244 Mistwood Ln., N. Aurora, IL 60542  
 gjfdataRCDD@aol.com

## Computer Software

Need help with  
**ELECTRONICS?**  
**"FNC-ELCAD"**  
**Priced low, easy to use!**  
 Contact FNC Corp.  
**847.695.1210 or**  
**www.fncwired.com**

[www.nutsvolts.com](http://www.nutsvolts.com)

## Speakers

**PARTS**  
**EXPRESS**  
 YOUR ELECTRONICS CONNECTION  
**The Audiophile Source**

- Speakers
- Electronics
- Connectors
- A/V Accessories

Call for a Free Catalog  
**1-800-338-0537**  
 or visit us at  
**parts-express.com**  
 SOURCE CODE: NVM2

*Not too long ago, in a  
galaxy not so far away ...  
there was something that  
came along that would change  
the future of robotics forever ...*

**SERVO**  
 MAGAZINE

Subscribe TODAY and we won't send the Storm Troopers after you!  
 Call us at 800-783-4624 or go online at [www.servomagazine.com](http://www.servomagazine.com)



# VIDEO BASICS

BY KEITH JACK

*Although there are many variations and implementation techniques, video signals are just a way of transferring visual information from one point to another. The information may be from a VCR, DVD player, broadcast channel, cable television, satellite system, the Internet, or one of many other sources.*

**I**nvariably, video information must be transferred from one device to another. It could be from a satellite set-top box or DVD player to a television — or it could be from one chip to another inside the satellite set-top box or television. Although it seems simple, there are many different requirements and, therefore, many different ways of doing it.

Until a few years ago, most consumer video equipment supported only analog video. Digital video was confined to professional applications, such as video editing.

The average consumer now uses digital video every day, thanks to continually falling costs. This trend has

led to the development of DVD players and recorders, digital set-top boxes, digital television (DTV), portable video players, and the ability to use the Internet for streaming video data.

## **Video Data**

Initially, video contained only Y or grayscale (also called black-and-white) information.

While color broadcasts were being developed, attempts were made to transmit color video using analog RGB (Red, Green, Blue) data. However, this




that led to using Y, U, and V data to represent color information. A technique was then developed to transmit this Y, U, and V information using one signal — instead of three separate ones — in the same bandwidth as the original grayscale video signal. The general relationship between YUV and gamma-corrected RGB ( $R'G'B'$ ) is:

$$\begin{aligned} Y &= 0.299R' + 0.587G' + 0.114B' \\ U &= -0.147R' - 0.289G' + 0.436B' \\ &= 0.492(B' - Y) \\ V &= 0.615R' - 0.515G' - 0.100B' \\ &= 0.877(R' - Y) \end{aligned}$$

$$\begin{aligned} R' &= Y + 1.140V \\ G' &= Y - 0.395U - 0.581V \\ B' &= Y + 2.032U \end{aligned}$$

In order to transmit the color information so that black-and-white televisions would still display the grayscale image, the color information (U and V) is modulated onto a 3.58 MHz (NTSC) or 4.43 MHz (PAL) subcarrier and added to the grayscale video signal.

$$\text{composite color video} = Y + U \sin \omega t + V \cos \omega t + \text{timing}$$

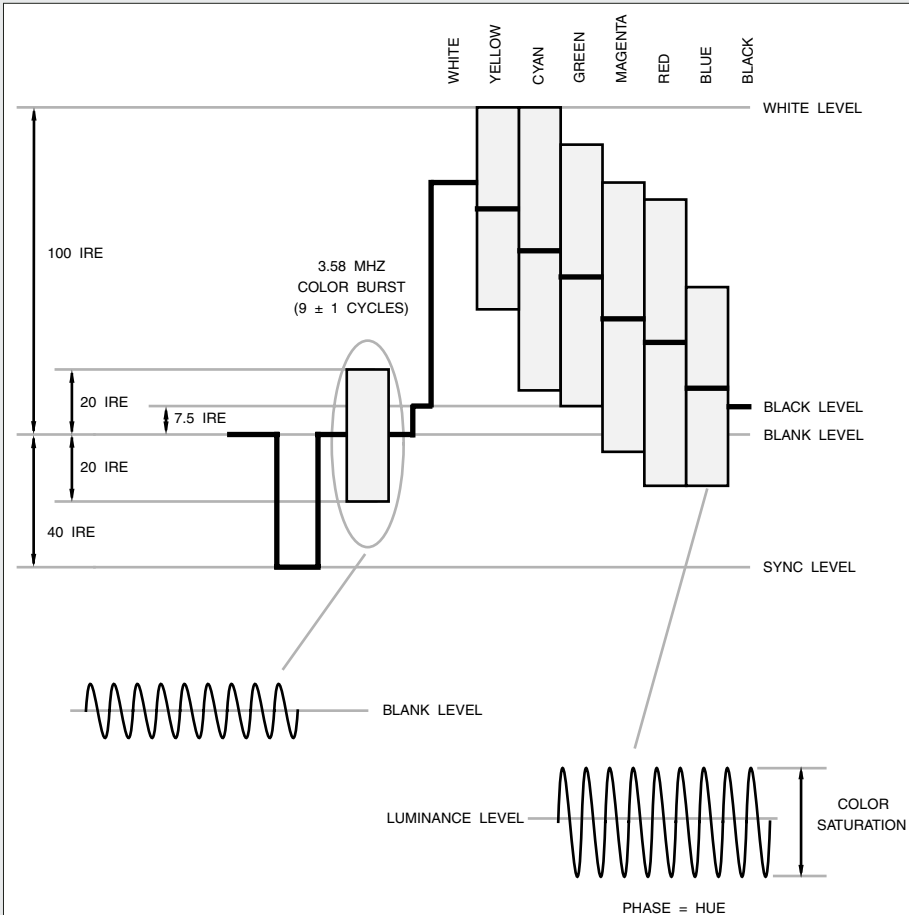


**FIGURE 1. NTSC COMPOSITE VIDEO SIGNAL FOR 75% COLOR BARS.**

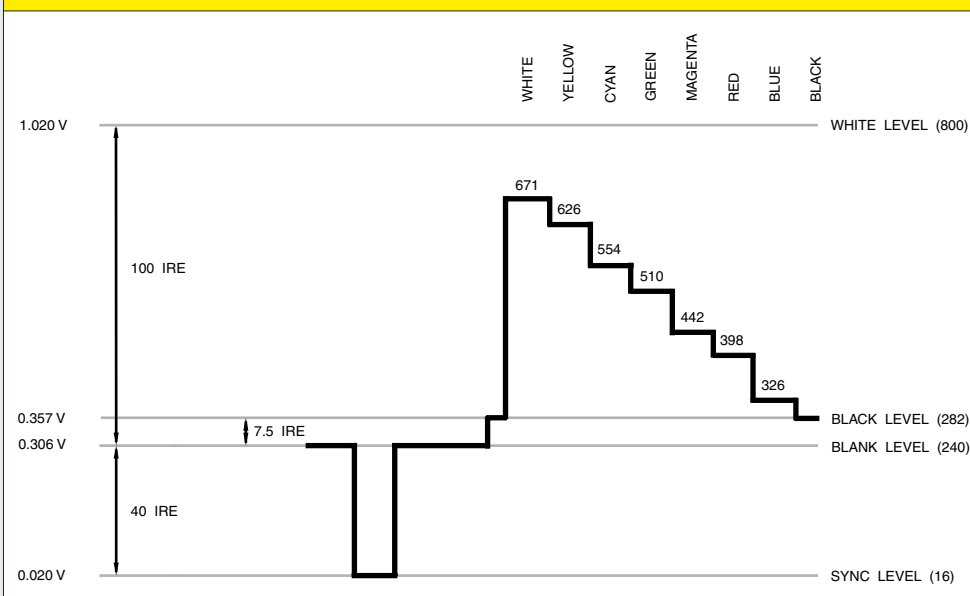technique occupied 3x more bandwidth than the current grayscale solution, so alternate methods were developed

$$\begin{aligned} w &= 2\pi F_{sc} \\ F_{sc} &= \sim 3.58 \text{ MHz for NTSC; } \sim 4.44 \text{ MHz for PAL} \end{aligned}$$

**FIGURE 2. NTSC LUMINANCE (Y) VIDEO SIGNAL FOR 75% COLOR BARS. INDICATED LUMINANCE LEVELS ARE 10-BIT VALUES.**



The resulting NTSC composite video signal (Figure 1) is what the NTSC, PAL, and SECAM video standards are still based on today.

S-video was later developed for connecting consumer equipment together (it is not used for broadcast purposes). It is a set of two analog signals — the grayscale (Y) signal (shown in Figure 2) and the chroma (C) signal that carries the U and V color information in a specific format (shown in Figure 3). Note that if Y and C are added together, the result is a composite video signal. Once available only for S-VHS, S-video is now supported

# VIDEO BASICS

on most consumer video products.

Although always used by the professional video market, analog RGB video data has made a temporary come-back for connecting high end consumer equipment together. Like S-video, it is not used for broadcast purposes.


A variation of the analog YUV video signals called YPbPr — illustrated in Figure 4 — is now commonly used for connecting consumer video products together. Its primary advantage is the ability to transfer high definition video between consumer products. Some manufacturers also label these YPbPr connectors as YUV, YCbCr, or Y(B-Y)(R-Y).

## Video Timing

Although it looks like video is in continuous motion, it is actually a series of still images, changing fast enough that it looks like continuous motion, as shown in Figure 5. This typically occurs 50 or 60 times per second for consumer video and 60–90 times per second for computer displays. Special timing information known as vertical sync is used to indicate when a new image is starting.


Each still image is also composed of scan lines — lines of data that occur sequentially, one after another, down the display, as shown in Figure 6. Additional timing information — horizontal sync — is used to indicate when a new scan line is starting. The vertical and horizontal sync information is usually transferred in one of three ways:

1. Separate horizontal and vertical sync signals
2. Separate composite sync signal
3. Composite sync signal embedded within the video signal

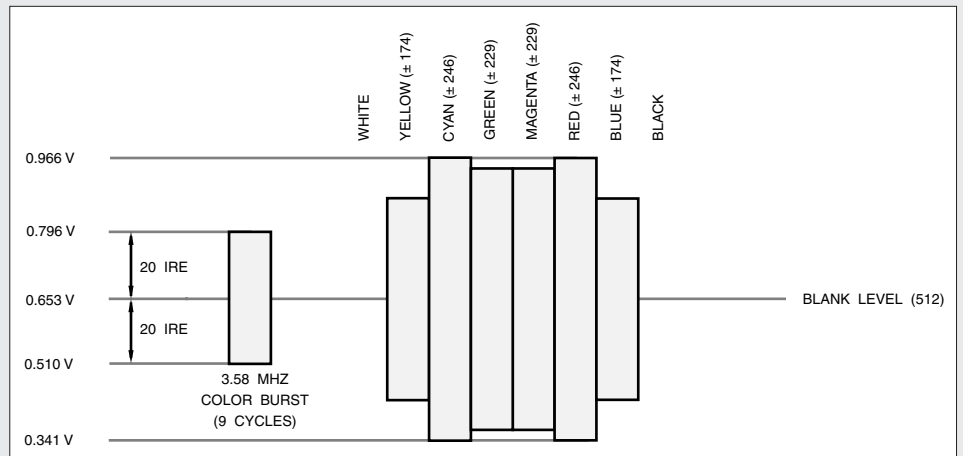


**FIGURE 3. (M) NTSC CHROMINANCE (C) VIDEO SIGNAL FOR 75% COLOR BARS. INDICATED VIDEO LEVELS ARE 10-BIT VALUES.**

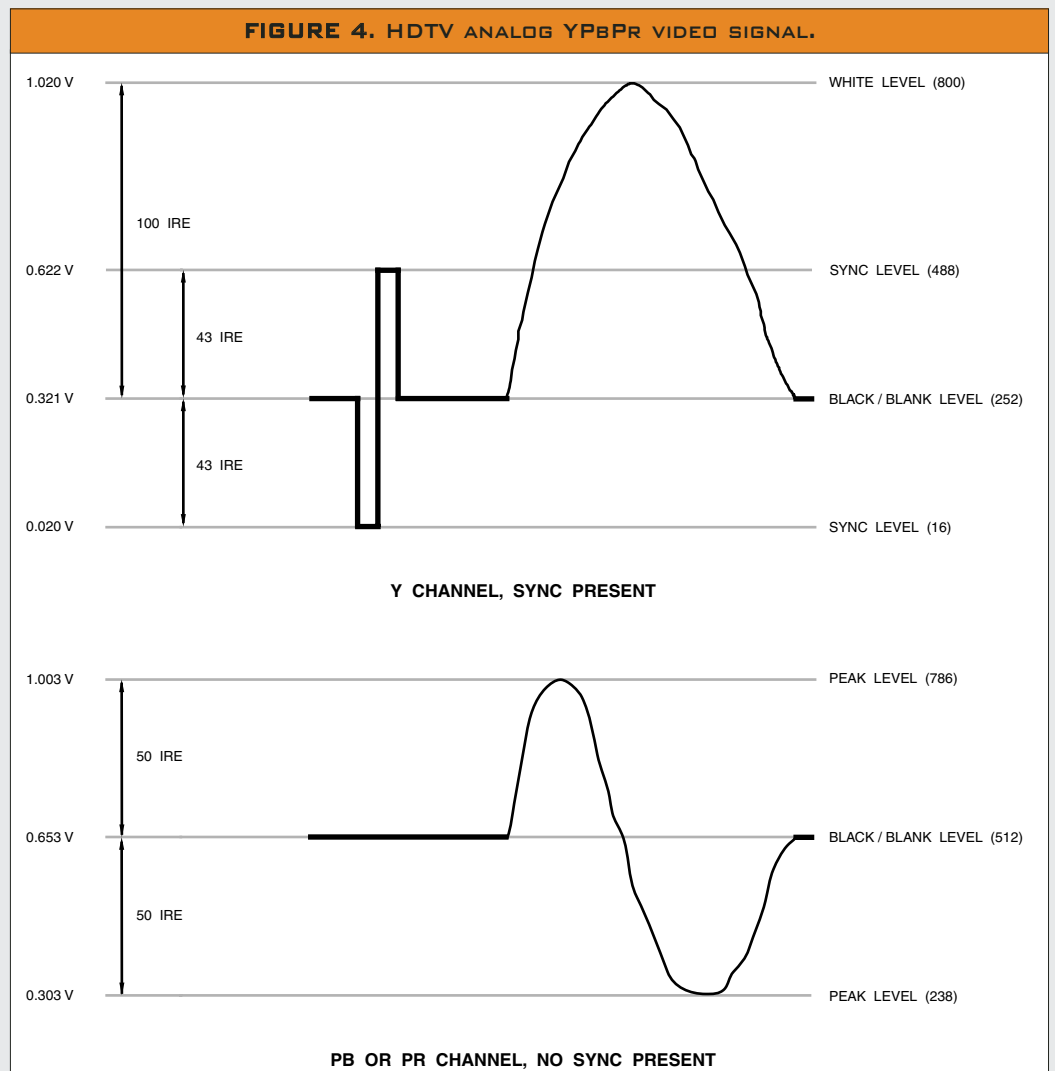The composite sync signal is a combination of both vertical and horizontal sync. Computer and consumer equipment that uses analog RGB video usually uses technique 1 or





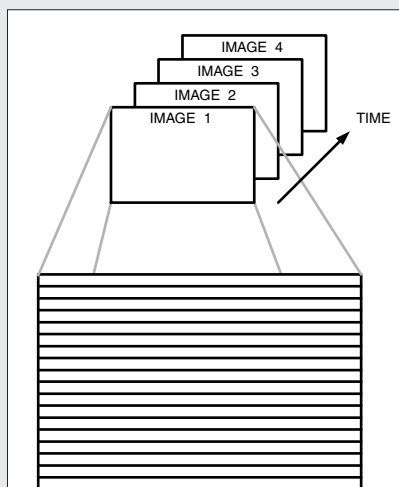


**FIGURE 5.** VIDEO IS COMPOSED OF A SERIES OF STILL IMAGES. EACH IMAGE IS COMPOSED OF INDIVIDUAL LINES OF DATA.

technique 3. For digital video, either technique 1 is commonly used or timing code words are embedded within the digital video stream.

## Interlaced vs. Progressive

Since video is a series of still images, it makes sense to simply display each full image consecutively, one after the another. This is the basic technique of progressive — or non-interlaced — displays. For progressive displays that “paint” an image on the screen (such as a CRT), each image is displayed starting at the top left corner of the display, moving to the right edge of the display. The scanning then moves down one line and repeats scanning left-to-right. This process is repeated until the entire screen is refreshed, as seen in Figure 6.

In the early days of television, a technique called “interlacing” was used to reduce the amount of information sent for each image. By transferring the odd-numbered

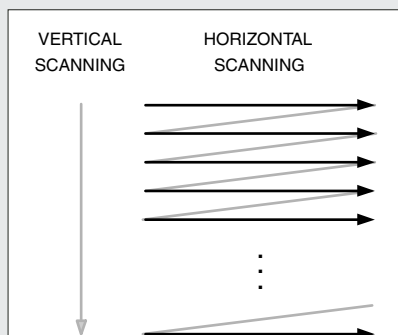

**FIGURE 6.** PROGRESSIVE DISPLAYS “PAINT” THE LINES OF AN IMAGE CONSECUTIVELY, ONE AFTER ANOTHER.

2. Consumer equipment that supports composite video or analog YPbPr video usually uses technique

lines followed by the even-numbered lines (as shown in Figure 7), the amount of information sent for each image was halved. Given this advantage of interlacing, why bother to use progressive?

With interlace, each scan line is refreshed half as often as it would be if it were a progressive display. Therefore, to avoid line flicker on sharp edges due to a too-low refresh rate, the line-to-line changes are limited, essentially by vertically lowpass-filtering the image. A progressive display has no limit on the line-to-line changes, so it is capable of providing a higher resolution image (vertically) without flicker.

Today, most broadcasts (including HDTV) are still transmitted as interlaced. Most CRT-based televisions are still interlaced, while LCD, plasma, and computer displays are progressive.

## Digital Video

The most common digital video signals used are RGB and YCbCr. RGB is simply the digitized version of the analog RGB video signals. YCbCr is basically the digitized version of the analog YPbPr video signals and is the format used by DVD and the various terrestrial, cable, and satellite digital television standards (ATSC, DVB, and ISDB).

Not too long ago, DVI was introduced to consumer products for transferring digital RGB video between components. In 2004, the trend has shifted to using HDMI, which has the advantage of a smaller connector, the ability to transfer digital audio, and the ability to support both the RGB and YCbCr digital video formats.


## Best Connection Method

There is always the question, “What is the best connection method for equipment?” For DVD players and digital cable/satellite/terrestrial set-top boxes, the typical order of decreasing video quality is:

1. HDMI (digital YCbCr)
2. HDMI/DVI (digital RGB)
3. Analog YPbPr
4. Analog RGB
5. Analog S-video
6. Analog Composite

Some may disagree about the order. However, most consumer products do digital video processing in the YCbCr color space. Therefore, using YCbCr as the interconnect for equipment reduces the number of color space conversions required. Color space conversion of digital signals is still preferable to D/A (digital-to-analog) conversion, followed by A/D (analog-to-digital) conversion, hence the positioning of DVI above analog YPbPr.

**FIGURE 7.** INTERLACED DISPLAYS FIRST “PAINT” ONE HALF OF THE IMAGE (ODD LINES), THEN THE OTHER HALF (EVEN LINES).

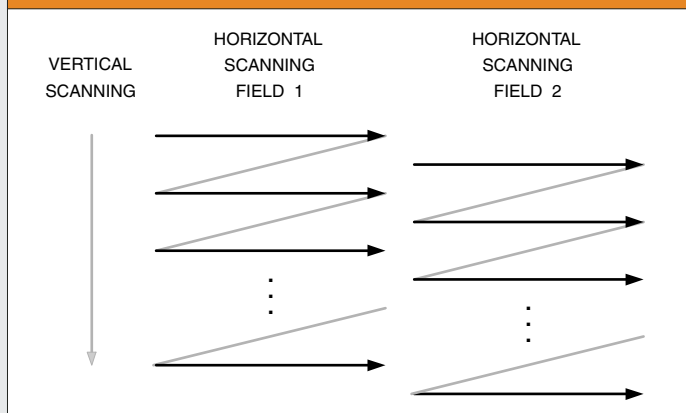

# VIDEO BASICS

## Video Resolution

Video resolution is one of those “fuzzy” things in life. It is common to see video resolutions of 720 x 480 or 1,920 x 1,080. However, those are just the number of horizontal samples and vertical scan lines and do not necessarily convey the amount of useful information.

For example, an analog video signal can be sampled at 13.5 MHz to generate 720 samples per line. Sampling the same signal at 27 MHz would generate 1,440 samples per line. However, only the number of samples per line has changed, not the resolution of the content.

Therefore, video is usually measured using “lines of resolution.” In essence, how many distinct black-and-white vertical lines can be seen across the display? This number is then normalized to a 1:1 display aspect ratio (dividing the number by 3/4 for a 4:3 display or by 9/16 for a 16:9 display). Of course, this results in a lower value for widescreen (16:9) displays, which goes against intuition.

### Standard Definition

Standard definition video is usually defined as having 480 or 576 interlaced active scan lines and is commonly called 480i or 576i, respectively.

For a fixed-pixel (non-CRT) consumer display with a 4:3 aspect ratio, this translates into an active resolution of 720 x 480i or 720 x 576i. For a 16:9 aspect ratio, this translates into an active resolution of 960 x 480i or 960 x 576i.

### Enhanced Definition

Enhanced definition video is usually defined as having 480 or 576 progressive active scan lines and is commonly called 480p or 576p, respectively.

For a fixed-pixel (non-CRT) consumer display with a 4:3 aspect ratio, this translates into an active resolution of 720 x 480p or 720 x 576p. For a 16:9 aspect ratio, this translates into an active resolution of 960 x 480p or 960 x 576p.

The difference between standard and enhanced definition is that standard definition is interlaced, while enhanced definition is progressive.

### High Definition

High definition video is usually defined as having 720 progressive (720p) or 1,080 interlaced (1,080i) active scan lines. For a fixed-pixel (non-CRT) consumer display with a 16:9 aspect ratio, this translates into an active resolution of 1,280 x 720p or 1,920 x 1,080i, respectively.

However, HDTV displays are technically defined as being capable of displaying a minimum of 720p or 1,080i active scan lines. They also must be capable of displaying 16:9 content using a minimum of 540 progressive (540p) or 810 interlaced (810i) active scan lines. This enables the manufacturing of CRT-based HDTVs with 4:3 aspect ratios and LCD/plasma 16:9 aspect ratio displays with resolutions of 1,024 x 1,024p, 1,280 x 768p, 1,024 x 768p, and so on, lowering costs.

JANUARY 2005

## Audio and Video Compression

The recent advances in consumer electronics — such as digital television, DVD players and recorders, digital video recorders, and so on — were made possible due to audio and video compression based largely on MPEG-2 video with Dolby® Digital, DTS®, or MPEG audio. New audio codecs (such as MPEG-4 HE-AAC and WMA Pro) and new video codecs (such as H.264 and SMPTE VC-1) offer much better compression than legacy codecs for the same quality. These advances are enabling new ways of distributing content (both to consumers and within the home), new consumer products (such as portable video players and mobile video/cell phones), and more cable/satellite channels. **NV**

## ABOUT THE AUTHOR

*Keith Jack is the author of Video Demystified and Director of Product Marketing at Sigma Designs, a leading supplier of Digital Media Processors that provides high quality processing of H.264, WMV9/VC-1, MPEG-4, MPEG-2, MPEG-1, and content. In his previous career in marketing and chip design, he was involved in bringing over 30 multimedia chips to the consumer market.*

## Complete Ethernet Development Kit

KIT PRICE  
**\$99**  
Reg. \$199



**Breathe new life into your embedded systems with the Ethernet Connection Development Kit.**

- RCM3720 RabbitCore™ with 512K Flash, 256K SRAM, 1MB Serial Flash, 33 digital I/O.
- Complete development software (not a trial version).
- Royalty-free TCP/IP stack and sample programs/libraries.
- Development board with prototyping area.
- AC adapter and complete documentation.



Learn More!  
[www.rabbitetherkit.com](http://www.rabbitetherkit.com)  
530.757.8400



Circle #84 on the Reader Service Card.





*For the  Gearheads who have it all ...*

Our special holiday offer lands  
**YOU AND A FRIEND** your very own  
one-year subscription to *Nuts & Volts*  
for just \$15.00 EACH!

**HURRY! Offer expires  
January 31, 2005!**

**Forget about fruitcake and soap-on-a-rope.  
What you and your friend need  
are BIGGER brains!**

Send yourself and a fellow gearhead a special gift this holiday season. Buy or renew your own subscription to *Nuts & Volts* for one year and get a second subscription for your friend or loved one. That's two (not one!) separate one-year subscriptions for a total of \$30.00 (US only).

***That's 40% off the regular subscription rate!***

More Friends? No problem! Additional subscriptions may be added at \$15.00 each.

Order by phone **(800) 783-4624**

Online **[www.nutsvolts.com](http://www.nutsvolts.com)**

Fax **(951) 371-3052**



# THE PID CONTROLLER

## Part 1

by Aaron Dahlen

*Welcome to the world of control systems. This is truly one of the most exciting and fascinating aspects of electronics.*

In this series of articles, we will explore how to implement both analog and digital control systems. We will be using a PID (Proportional Integral Derivative) controller. With a PID controller, we can control thermal, electrical, chemical, and mechanical processes. The PID controller is found at the heart of many industrial control systems.

In this first of three installments, we will answer the “why” questions. We will also lay a foundation to better understand what a PID controller is. In subsequent installments, we will explore how to tune the PID controller and how to implement a digital PID using the ZILOG Encore! microprocessor.

The goal of this series is to introduce you to the world of control electronics. Concepts will be explained in a simple, intuitive fashion and useful, practical examples will be presented. The math will be kept to an absolute minimum. This is not to say that the math is not important. Quite the opposite — control systems may be modeled and analyzed mathematically. The mathematics is nothing short of amazing and I would encourage you to peruse it. There are hundreds of books that explain the theory and mathematics of control systems. These books will introduce you to powerful tools, such as Laplace transforms, root locus, and Bode plots. Again, this series of articles hardly scratches the surface. There is much more to be learned.

### What Is PID Control?


The term PID is an acronym that stands for Proportional Integral Derivative. A PID controller is part of a feedback system.

A PID system uses Proportional, Integral, and Derivative drive elements to control a process. Some of you already know what P, I, and D stand for. Don't worry if you don't; we will soon cover these terms with easy-to-understand examples.

### Why Do I Need PID Control?

You need the PID because there are some things that are difficult to control using standard methods. Let me illustrate with an example. My first experience with control systems was a failure. My goal was to regulate the output of a power supply using a PIC microcontroller. The PIC read the output voltage with an AD converter and adjusted a PWM to regulate the output. The control strategy was very simple: If the voltage was below a set-point, turn on the PWM. If the measured voltage was above the set-point, then turn off the PWM. The PIC power supply almost worked. It did produce the DC output voltage that I wanted. Unfortunately, it also has a significant AC ripple riding on the DC signal.

The control strategy I just described is called on-off or bang-bang control. Many types of systems use this control strategy. Take the furnace in my house as an example. When the temperature is below the set-point, the furnace is on. When the temp is above the set-point, the furnace is off. Just like my power supply, the plot of temperature over time results in a sine wave.

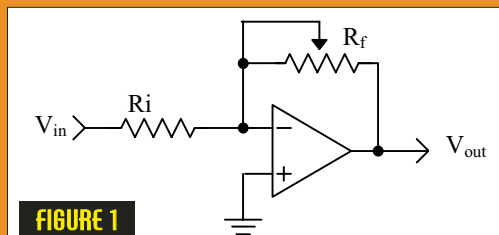

**FIGURE 1**

For some types of control, this is acceptable; for others, it is not. You wouldn't want this type of control for a servo motor — bad things would happen! Just imagine — the motor would be full power in one direction and, the next moment, full power in the other direction. You can see where the term bang-bang comes from. That servo won't last long!

The PID controller takes control systems to the next level. It can provide a controlled — almost intelligent — drive for systems. We will now examine the individual components of the PID system. This step is necessary to understand the entire PID system. Please don't skip this section; you must know how the individual components function to understand the whole system.


## What Is Proportional?

This one is easy. The proportional component is simply gain. We can use an inverting op-amp, as shown in Figure 1. In this op-amp circuit, the gain is set by the values of the resistors. We have the following mathematical relationship:

$$V_{out} = -V_{in} * R_f / R_i$$

## What Is Integral?

Integral is shorthand for integration. You can think of this as accumulation (adding) of a quantity over time. For example, you are now integrating this information into your store of knowledge. Your store of knowledge has

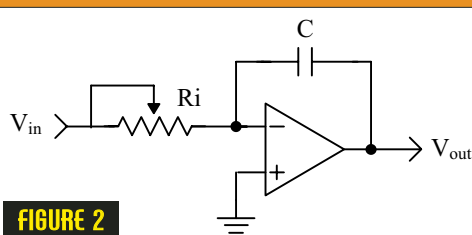

**FIGURE 2**


components of both time and knowledge. Obviously, we all started as babies with virtually no knowledge. Over time, we have integrated knowledge into our brains.

In our PID controller, we are integrating voltage as time progresses. A schematic of an integrator circuit is shown in Figure 2. The output voltage is described mathematically by the following equation:

$$V_{out} = -(1/RC) * (\text{area under curve}) + \text{initial charge on capacitor}$$

Area is a component of voltage and time. Let's examine the operation of an ideal integrator. We can simplify the math by making the  $1/RC$  term equal to 1 (i.e., let  $R=100\text{ K}\Omega$  and  $C=10\text{ }\mu\text{F}$ ). Figure 3 illustrates the input/output relationships of the integrator. From Time 0 to 2 seconds, have a 2 V square wave applied to the input of the integrator. The output of the integrator at the end of this time period is -4 V (remember the circuit is inverting). The integrator has accumulated a 2 V signal for 2 seconds. The area is equal to 4. From T2 to T4, there is no voltage applied to the integrator. The output is unchanged. In the remainder of this diagram, you can see that the integrator output changes polarity when the input signal changes polarity.

The previous discussion assumed an ideal integrator. Real capacitors will have some leakage and will tend to discharge themselves. Also, real op-amps may charge the capacitor with no input present. If the circuit is built as drawn, it will likely saturate after a few minutes of operation. To prevent this saturation, add a resistor in parallel to the capacitor. For our purposes, we are not concerned about the saturation. We will be using the integrator with other circuits to control the charge on the capacitor.

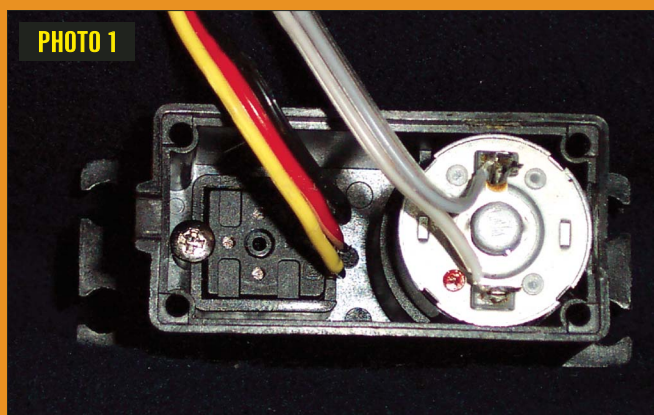

**PHOTO 1**




**PHOTO 2**



To better understand the integrator, let's look at a typical application. Integrators are often found in high end audio amplifiers. In this application, they are called DC servos. A typical application is shown in Figure 5. The purpose of this circuit is to remove the unwanted DC voltage from the output of the audio amplifier. Any DC voltage seen on the output of the amplifier will tend to charge the integrator's capacitor. The integrator then changes the bias of the audio amplifier to remove the DC component. The resistor and capacitor are selected so that the circuit will not respond to audio frequencies.

Also, recall that an AC waveform is symmetrical. The part above 0 tends to charge the capacitor, while the part below will discharge the capacitor. Therefore, when you integrate an AC waveform over a large amount of time, you get 0. Even a small DC voltage will charge the capacitor over a long period of time, thus rebiasing the amplifier.

FIGURE 3

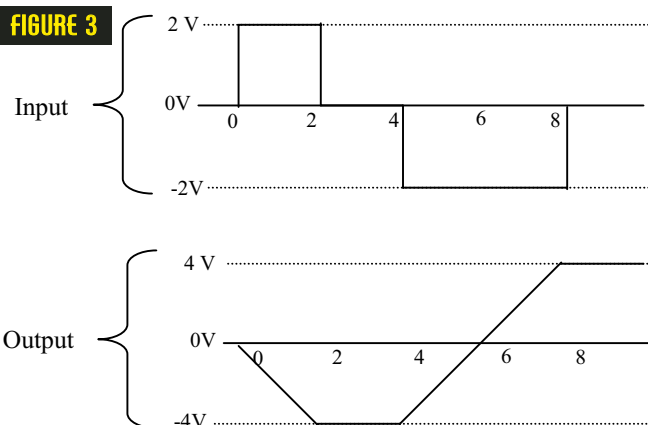

apply a ramp to the differentiator, we get a steady DC output voltage. Figure 6 illustrates the input/output relationship of

## What Is Derivative?

The derivative is a measurement of the rate of change. The ideal differentiator is shown in Figure 5. This circuit looks similar to the high pass filters you have seen in other schematics. Low frequencies are attenuated, while high frequencies are allowed to pass. The mathematics that describe the differentiator is:

$$V_{out} = -RC * (\text{rate of change})$$

Rate of change is equivalent to measuring the slope of a line. Slope is a measure of the change in voltage divided by the change in time. In mathematical terms, this is referred to as a delta voltage over delta time or simply  $dv/dt$ . If we

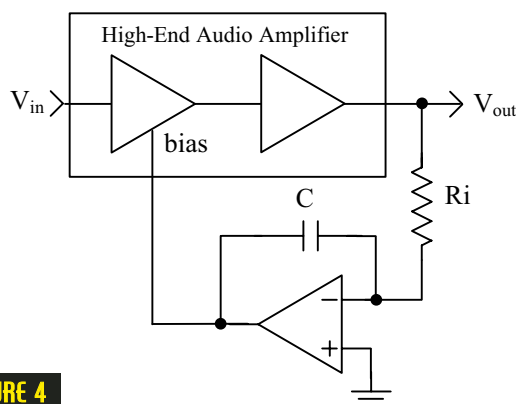


FIGURE 4

## Stepper Motor Book

### Easy Step'n

- For the experimenter.
- Determine surplus stepper motor specs using simple easy to build test equipment.
- Design and build microcontroller-based control systems (flow charts and code examples included).
- Design and build stepper motor driver circuits.
- Analyze the mechanical characteristics of stepper motor-driven devices.
- The book is full of experiments, circuits and code. \$34.95

Table Of Contents And Ordering Information On Web Site

<http://www.stepperstuff.com>

**SQUARE 1** ELECTRONICS

P.O. Box 1414, Hayden, ID 83835  
Voice (208) 664-4115 Fax (208) 772-8236

We have been selling on the Internet since 1996. We ship the day we receive your order or the next business day.

## PIC® Microcontroller Books



New Titles

Same Useful Books

Table Of Contents And Ordering Information On Web Site.

Not Distributed Via Book Sellers

We accept VISA, MC, AM, DS, MO, Check  
CA residents please add 7.25% CA sales tax  
See our web sites for s/h rates.

PIC, PICmicro and MPLAB are trademarks  
of Microchip Technology Inc.

Easy Microcontrol'n - Beginner \$29.95

- Programming Techniques
- Instruction set, addressing modes, bit manipulation, subroutines, loops, lookup tables, interrupts
- Using a text editor, using an assembler, using MPLAB
- Timing and counting (timer 0), interfacing, I/O conversion

Microcontrol'n Apps - Intermediate \$44.95

- Serial communication - PICmicro to peripheral chips
- Serial EEPROMS
- LCD interface and scanning keypads
- D/A and A/D conversion - several methods
- Math routines
- 8-pin PICmicros
- Talking to a PICmicro with a PC using a terminal program
- Test equipment and data logger experiments

Time'n and Count'n - Intermediate \$34.95



- 16-bit timing and counting applications
- Timer 1, timer 2 and the capture/compare/PWM (CCP) module

Serial Communications - Advanced \$49.95

- Synchronous - bit-bang, on-chip UART, RS-232
- Asynchronous - I2C (Philips Semiconductors)
- SPI (Motorola), Microwire (National Semiconductor)
- Dallas Semiconductor 1-Wire bus

<http://www.sq-1.com>

**FIGURE 6**

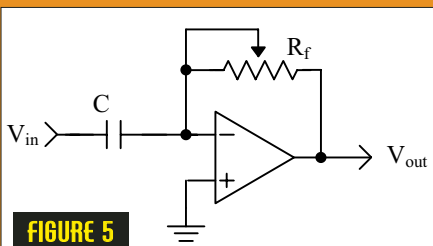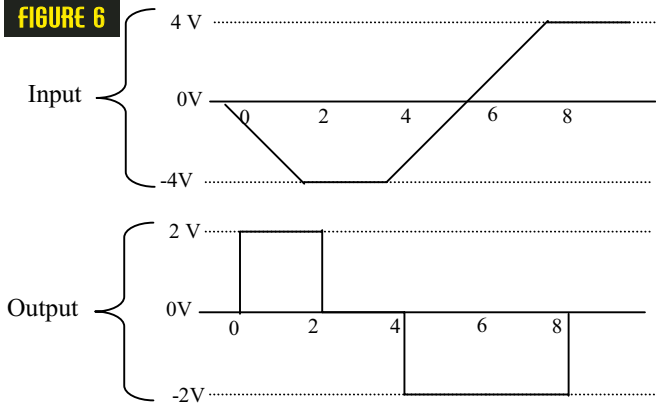

**FIGURE 5**

a differentiator. To simplify the math, we will let  $RC=1$ . From time 0 to 2, the voltage changes -4 volts, while the time changes 2

seconds. The slope of this line is, therefore, -2. The output of the differentiator will be equal to 2 — remember the stage is inverting.

## Servo Motor System

Now that we are familiar with the P, I, and D terms, let's examine how they are combined to form a complete system. We will be using the PID controller to control a DC servo motor. I used a Hitec brand servo motor typically found in R/C model cars and airplanes. This servo is inexpensive and readily available. You can also purchase replacement gears — more of that in the next installment!

The servo mechanism consists of several components, as shown in Photo 1. We have a DC motor, a set of gears, and a variable resistor. The resistor is attached to the last gear. This variable resistor is used to determine

the rotational position of the motor.

The servo was gutted. I only used the motor and the variable resistor, as shown in Photo 2.

## PID Block Diagram

A block diagram showing the functional relationships of the PID controller is shown in Figure 7. The first thing to notice is that this is a parallel process. The P, I, and D terms are calculated independently and then added at the summer  $\Sigma$ . The input to this loop is the set-point — in this application, it can range from -12 to +12 VDC. The output is motor position. Position is measured by the resistor and feedback as a voltage between -12 to 12 VDC. We will now examine each of the PID terms independently to see how they are related. For this discussion, assume that the set-point is 0 VDC.


On the far left of Figure 7, we see a summing junction. The difference between the set-point and feedback is the error of the system. If the measured motor position is positive of where it should be, the error will be negative (i.e., a negative correction is required). Likewise, if the measured motor position is -1, the error will be positive 1 (i.e., a positive correction is required — remember set-point is 0 VDC).

The error is multiplied by the gain of the proportional block. Notice that the block diagram shows this as a negative gain. This was done so that the block diagram and the schematic (presented later) will be consistent with each other. The proportional amplifier output is sent to the second summing junction, where the sign is again inverted. The amplifier boots the signal's current and drives the motor.

This chain gets to be quite long, so let's summarize proportional operation in a few simple sentences:

1. An error must be present!
2. The system will try to correct the error by turning the motor in a direction that opposes the error.
3. The intensity of the correction is determined by proportional gain. If there is no error, there is no proportional drive.

Moving on to integral — the integral is a device that charges a capacitor over a period of time. Recall the example of the audio amplifier. In that application, the integrator accumulated the DC output of the amplifier over time. It then rebased the amplifier to eliminate the DC

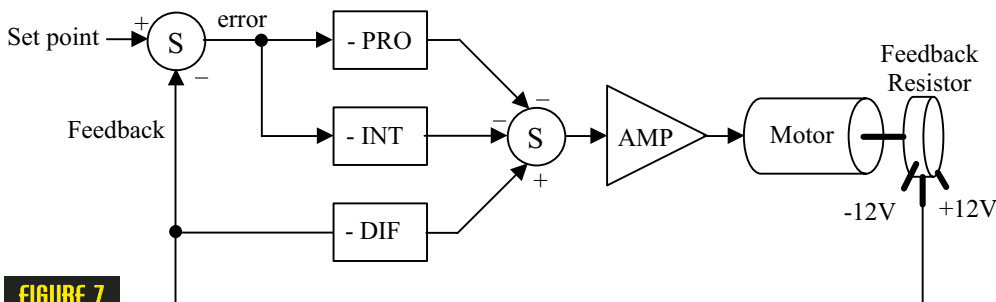

**FIGURE 7**

error. In the circuit in Figure 7, the integrator is performing the same task. It is integrating the error. It then provides a correction signal to the motor. We can summarize integral action in a few sentences:

1. An error must be present!
2. The integral section accumulates the error. A small error can become a large correction over a period of time.
3. As the error is accumulated, the motor is forced to correct the error.
4. Finally, the integrator will overshoot the set-point. It must produce an error opposite of the original in order to discharge the capacitor.

The final PID component is the derivative. Recall that the output of the differentiator was proportional to the slope of a wave. The same type of action is occurring in this circuit. When the motor starts to turn, the voltage measured by the resistor will be increasing or decreasing. If we have a voltage changing over a period of time, we have a ramp! The slope of this ramp changes with the speed of the motor. If the motor is going fast, the slope is high (i.e., voltage is changing fast for a given amount of time). Consequently, the output of the derivative stage will be high. The differentiator has the following attributes:

1. The motor must be moving!
2. The differentiator will have a high output voltage when the motor is moving fast and a low voltage when the motor is moving slow.
3. This signal is applied in such a way as to slow down the motor.
4. If the motor is not moving, the differentiator has 0 output voltage.

The connections for the differentiator are different than the proportional and integral sections. The differentiator receives its input directly from the resistor. It, therefore, measures only the speed at which the motor is moving. It does not care about the set-point. This is done to prevent large derivative drive signals when the set-point is changed. Again, the differentiator only responds to the speed of the motor.

## Schematic

Figure 8 contains a simplified schematic of a servo motor PID control system. This schematic is an adaptation of the PID controller presented by Professor Jacob in his book, *Industrial Control Electronics*. This type of system has the advantage of easy tuning. This circuit is also

## 16 bit analog development with a PIC 16F876 for precision instrumentation applications



RJL Systems has a 25 year history in medical devices and is proud to announce an analog development board for engineers and hobbyists who demand accurate signal processing for display and communications.

- Bipolar 16 bit ADC (+/- 1.5000 volts FS 100K SPS)
- Isolated 8 channel analog mux (single ended)
- Isolated power supplies (+/- 5.0V analog and 5.0V digital)
- Isolated 9 digital PIC I/O pins with buffered LED indicators
- Hard wired development area with access to all power
- Isolated RS-232C communications (115.2 Kbps max)
- 4 line X 20 character (blue) display with white LED
- In-circuit programming and debugging (RJ-12 connector)
- CCS PIC-C sample code and schematics provided (CD ROM)
- Operates from any battery or bench 6 to 12 VDC power supply
- Screw terminals for convenient wiring to external devices



RJL Systems, Inc.  
33955 Harper Ave.  
Clinton Twp, MI 48035  
**1-800-528-4513**  
[www.realanalog.com](http://www.realanalog.com)



# THE PID CONTROLLER — Part 1 ●●●●●

simple and easy to construct.

The schematic has the same physical layout as the block diagram. Op-amp U1 is used as the summing junction for the set-point and measured motor position. The individual P, I, and D functions are implemented by U2, U3, and U4, respectively. Finally, op-amp U5 sums the individual PID terms. The P and I terms are inverted,

while the D term is not. Darlington transistors have been added to U5 to boost the current to a level sufficient to drive the motor.

The individual P, I, and D components appear just as they were presented earlier in this article. Each of the terms has a variable resistor to adjust its gains. The adjustment (tuning) of this circuit is the topic for

the next installment.

Component selection for this circuit is not critical. The variable resistors should be multiturn for ease of adjustment. General-purpose op-amps may be used; however, U3 should be a FET input type. The FET design is better for the integrator, since it will not self-charge the integrator capacitor. I found a quad op-amp — such as the LF347N — to be ideal for this application. Large capacitors are required for the integrator and derivative circuits. The large values necessitate that electrolytic capacitors be used. The electrolytic capacitor may be operated as a non-polarized capacitor by placing two capacitors in series, as shown in the schematic.

A full schematic will appear in next month's installment. You may download the CAD files (in Eagle) from the *Nuts & Volts* website at [www.nutsvolts.com](http://www.nutsvolts.com)

## Testing

Before we can test the PID circuit, we need to know more about the mechanical system. We need to know how it responds to a command and how the individual P, I, and D terms interact. You will have to be patient and wait for next month's installment. In the meantime, go ahead and breadboard the circuit. You can use a function generator to verify the individual stages. See how the individual stages respond to sine, square, and triangle waveforms. Remember to use a low frequency — less than 10 Hz. This frequency is approximately the same as the servo motor system.

Stay tuned; next month, we will learn how to tune the PID controller. We will add additional circuitry to prevent a condition called integral wind-up. Also, keep a lookout for installment three, where we will implement the PID on a ZILOG Encore! microcontroller. **NV**

## REFERENCE

Jacob, Michael.  
*Industrial Control Electronics.*  
New Jersey: Prentice Hall, 1988.

8-16-bit EEPROM | Serial EEPROM | FLASH EPROM | GAL / PALCE | Most MCU's | Low Voltages to 1.3V. | DIL dev. w/o Adapter.

Conitec's last generation Galep-4 employs ASIC universal pin tech-



nology for each pin of 40 pin ZIF-socket. **6100+device library** / lifetime free updates. Programs 8/16 bit EPROM's, EEPROM's, 0-Pwr RAM, FLASH, Serial EEPROM's, GAL, PALCE,

**6100**  
DEVICES  
CONITEC

microcontrollers such as 87/89xxx, PIC, AVR, ST62, etc. Low voltage devices down to 1.3V. No adapter required for DIL devices. 8 Hrs. operation on battery (AC charger included). Runs **WIN 98,NT,ME, 2000,XP** with Hex/Fuse Editor.

Remote control from other apps, (e.g. VisualBasic). Substitutes high priced universal programmers e.g. ALL-11 (HILO) or LAB-TOOL-48 (ADVANTECH) Providing virtually matching performance at only 1/3-1/5 the price. Info, orders, softwre : **619-702-4420**

One Small Programmer handles 5,500 devices.  
Introducing the diminutive GALEP-4



**SMALL PACKAGE. BIG FEATURES.**  
DEVICE PROGRAMMERS SINCE 1985

SALES, SUPPORT, INFO / (EMAIL) [CONTACT@CONITEC.NET](mailto:CONTACT@CONITEC.NET) - (URL) [WWW.CONITEC.NET](http://WWW.CONITEC.NET). TEL: 619-702-4420. FAX: 619-702-4419

Circle #99 on the Reader Service Card.

## Get the Laser Edge.

*Our advanced technology delivers fast, accurate and affordable custom enclosures and front panels.*

- ★ **Quick**
- ★ **Affordable**
- ★ **Precise**
- ★ **No Minimums**



Integrated Ideas & Technologies, Inc.  
Precision Laser Cut Stencils

3896 N. Schreiber Way • Coeur d'Alene, ID 83815-8362 USA  
Ph (208) 665-2166 • Fax (208) 665-5906 • [www.integratedideas.com](http://www.integratedideas.com)

Circle #104 on the Reader Service Card.



# Impact of the Internet on the Printed Circuit Board Industry

by Robert Schnyder

**T**he Internet has transformed business in a very profound way. Similar to the impact of the Industrial Revolution, the Internet has generated tremendous opportunities for growth and expansion. It has created an entirely new way of thinking about the concept of business. Companies that have embraced the Internet and online e-commerce can efficiently target new customers and markets in a more proficient manner, which — in turn — creates a new paradigm for company strategy and focus.

The Internet has  
breathed

new life into traditional business models. For example, “I’ll call you,” has been replaced by, “I’ll Email you.” Traditional business calls and company visits have been replaced by Email correspondence or virtual conferencing. Company brochures have been transformed into corporate websites. These changes show the dramatic impact the Internet has made on business today.

One area that has been revolutionized lately is the printed circuit board industry. This article will examine the Internet’s impact on the circuit board industry, the transformation of the buying process, and what it means for the



future of circuit board production.

### Impact on the Circuit Board Industry

In the field of circuit boards, the Internet has created an explosive proliferation on the traditional concept of the quote and order process. Customization of board specifications has made it difficult to standardize this industry. The evolution of the ordering process demonstrates the Internet's impact based on consumer demand:

Face-to-face => Telephone => Faxing => Email (RFQ) => Online Quoting

All of the above remain important aspects, but online quoting (e-commerce) is the one that has become the most beneficial to consumers. The ability to generate quotes and evaluate parameters online has created a shift in control of the buying process from the supplier to the consumer. It is also important to note that this evolution has also granted consumers more control while reducing the level and time of interaction with suppliers.

E-commerce has forced companies to reinvent traditional business practices and adopt new, consumer-focused strategies to compete online. According to e-commerce research, the most successful online companies provide consumers with all of the following:

- Save the consumer money (or provide the best value).
- Save the consumer time and effort.
- Offer a unique product or service.
- Offer a unique buying experience.

Before the Internet, suppliers did not concentrate on these concepts. They relied heavily on their ability to provide a competitive advantage through a combination of a company's ability to effectively compete on quality, price, and delivery of goods. It was the consumer's responsibility to seek out and obtain quotes from several suppliers, evaluate services, and obtain the best value (which usually meant the best price). Since this was

usually a long and tedious process, most consumers remained loyal to a few suppliers to avoid repeating this hassle every time a quote was required.

The Internet has transformed this long-established method for ordering circuit boards — to the benefit of the consumer.

Nowadays, consumers can search the Internet and obtain several quotes from many circuit board manufacturers with minimal contact or interaction with those companies. The time and effort saved through online comparison has provided consumers with a greater flexibility in their choice of suppliers. As a result, companies are reinventing conventional ways to compete for consumer business. Suppliers are not only doing more and making their products more appealing, but are also making the method of ordering those products more convenient.

### The Transformation of the Circuit Board Buying Process

Due to the uniqueness and complexity of the circuit board industry, consumers have traditionally relied on interaction with suppliers during the buying process. Even simple circuit boards required that many specifications and factors be taken into consideration. The Internet has leveled the playing field between consumers and suppliers by making the buying process available online (e-commerce).

The buying process has undergone an enormous transformation that has provided both advantages and disadvantages to consumers and suppliers. As suppliers continue to incorporate Internet strategies into their business models, consumers will benefit in a variety of ways. For example, the ability for consumers to generate online, instant quotes provides the following advantages:

- Significant time reduction of the quote process.
- Ability to change requirements and evaluate their effects in real time.
- Eliminates back and forth hassle of traditional quoting.
- Time, involvement, and interaction is decided by customer.
- Levels the playing field for consumers.

Suppliers also benefit from developing an online presence. The Internet provides an entirely new business medium from which companies can develop larger and varied markets, as well as attract new and unrealized customers. It makes the company more accessible and provides a means to address focused messages to target consumers. The Internet provides accessibility 24 hours a day, seven days a week to consumers — both domestic and international. The potential for growth is limitless, which should be very appealing to smaller or specialized

### Online Custom PCB Vendors

EPic Design Company — [www.epicdesignco.com](http://www.epicdesignco.com)

ExpressPCB — [www.expresspcb.com](http://www.expresspcb.com)

Micromint — [www.micromint.com](http://www.micromint.com)

PCB123 — [www.pcb123.com](http://www.pcb123.com)

PCBexpress — [www.pcbexpress.com](http://www.pcbexpress.com)

Pulsar, Inc. — <http://home.flash.net/~yogii>

R4Systems — [www.labcenter-electronics.com](http://www.labcenter-electronics.com)

V & V Machinery and Equipment — [www.vandvmachy.com](http://www.vandvmachy.com)



suppliers. The following analogy puts these ideas into perspective:

*The Internet is like a new interstate highway, where traffic passes by on a continual basis. The goal for companies is to make that flowing traffic stop and buy. Websites and Internet strategies provide the roadside storefronts and exit ramps from which these goals can be achieved.*

## What Does This Mean for the Future of Circuit Board Production?

Circuit board suppliers will continually streamline processes to drive down costs. Suppliers should hone in on the manufacturing capabilities they do best and streamline those processes. This will continue to drive down prices, while maintaining quality levels.

The Internet provides a level playing field for smaller board shops to compete with larger ones. Smaller board shops will focus on more concentrated product offerings, based on limited manufacturing capabilities. As more circuit board suppliers — both large and small — adopt online strategies, distinct product offering and categories will begin to emerge.

Consumers will have a greater variety of choice and options. As a result, consumers may not remain loyal as comparison shopping becomes much easier. Consumers will be able to first sort through what services they need and then compare between suppliers who offer the specific services or specifications required.

Finally, will this online evolution bring about the elimination of traditional face-to-face customer service? Not at all, since there will always be consumers who prefer human interaction. Offline interaction will decrease, but it will evolve into more of a complimentary method for ordering when problems and questions arise that cannot be accommodated through the online buying process.

However, consumers will continue to increase their use of online purchasing as long as the buying experience remains beneficial, providing lower cost products and processes while remaining easier, faster, and hassle-free. **NV**


## About the Author

Robert Schnyder is the Marketing Manager for the Circuit Board Division of ECD, Inc. He can be reached at [robert.schnyder@ecd.com](mailto:robert.schnyder@ecd.com). For circuit board designs, the company offers three options to consumers: PCBexpress.com provides low cost, prototype pricing with set parameters and product features. PCBpro.com was created to provide more flexibility by allowing consumers to generate online quotes based on a variety of options and purchase boards online. PCB123.com is free design software that provides schematic and layout design functionality.

JANUARY 2005

# PROTEUS
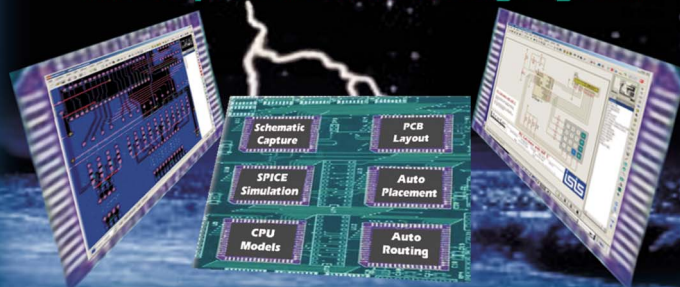
## The Complete Electronics Design System



## EASY TO USE CAD TOOLS

### Schematic and PCB Layout

- Powerful and flexible schematic capture.
- Auto-component placement.
- Rip/entry PCB routing.
- Polygonal gridless ground planes.
- Library of over 8000 schematic and 1000 PCB foot prints.
- Bill of materials, DRC reports and more.

### Mixed Mode SPICE Circuit Simulation

- Berkeley SPICE3F5 simulator with custom extensions for true mixed mode and interactive simulation.
- Six virtual instruments and 14 graph based analysis types.
- 6,000 models including TTL, CMOS and PLD digital parts.
- Fully compatible with manufacturers' SPICE models.

### Proteus VSM - Co-simulation & debugging for popular Micro-Controllers

- Supports PIC16 & PIC12, AVR, 8051, HC11 and ARM micro-controllers.
- Co-simulate target firmware with your hardware design.
- Includes interactive peripheral models for LED and LCD displays, switches, keypads, virtual terminal and much, much more.
- Provides source level debugging for popular compilers and assemblers from HiTech PICC, Crownhill, IAR, Keil and others.

### MicroChip PIC 18

- Supported models of the PIC 18 includes PIC18F242, PIC18F252, PIC18F442, PIC18F452, PIC18F248, PIC18F258, PIC18F448 and PIC18F458.

### Basic Stamp BS1 and BS2

- Proteus VSM for BASIC Stamp contains everything you need to develop and simulate designs based around the BASIC Stamp.
- See examples in downloadable Demo at [www.labcenter-electronics.com](http://www.labcenter-electronics.com)

"I finished my first design, schematic and PCB in one day."

"What a great tool! I love it."

DAN GILL

"For the cost of the software compared to the productivity gains, I consider Proteus to be pivotal in the commercial viability of my company and by far represents the best value for money of anything Tempus possesses."

ROB YOUNGS, Tempus Consulting

"PROTEUS stands out as the best all-round program in this review. Other programs reviewed have strengths in the pcb design process, Proteus maintains a constant high level of capability throughout. Whether a schematic, user-friendly interactive routing, configurable autoplacing, competent autorouting, or a combination of the above, PROTEUS handles everything very well." Electronic & Wireless World CAD Review Roundup

**Save Time. Save Money.**

**Proteus Starter Kit – \$199 • Full System – \$1899**

**"This is clearly superior in every respect."**

**R4** SYSTEMS INC.

**labcenter**  
Electronics

[www.labcenter-electronics.com](http://www.labcenter-electronics.com)

Tel: 905-898-0665 [info@r4systems.com](mailto:info@r4systems.com)

Circle #37 on the Reader Service Card.

## King's Bishop to RF



When life-long hobbyist Tom Van Baak's son displayed an interest in chess instead of circuitry, hacking, or programming, they found an interesting way to combine their interests. Tom — a software engineer by profession and an ultra-precise time hobbyist on the weekends — extended his building to a unique chess set.

Like all diligent hobbyists, he has an extensive collection of assorted finds from eBay and the *Nuts & Volts* Classifieds section. Over the years, his accumulation of RF

connections grew large enough that he was able to construct this complete set of chess pieces for his son. The pieces — which are gold and silver plated, respectively — are combinations of BNC, SMA, N, APC7, F, and UHF connectors and various elbows. The pawns are 50  $\Omega$  terminators. Tom's detail extended to the kings and queens, which are gender-accurate; male and female SMA connectors are mated with larger N connectors to make those pieces.

The set might be a bit removed from his interests in atomic clocks, WWVB, GPS, picoseconds, and the like, but Tom and his son have a beautiful piece of electronics-inspired art to use when they while away those father-son times!

Learn more about this project, along with Tom's elaborate atomic clock museum and home timing lab, at [www.LeanSecond.com](http://www.LeanSecond.com) or reach Tom via Email at [tvb@LeanSecond.com](mailto:tvb@LeanSecond.com)

## Da Vinci Decoding

A Dartmouth College team has developed a set of software tools that can determine the true artist of a painting, print, or drawing. As many pieces of art were done on a "class project" basis, the artist attributed to a work often only painted a portion of the image, with students filling in secondary forms, backgrounds, and details. Additionally, many famous works of art have had their creators questioned for decades or more.

The software analyzes various attributes of the artist's brush or pen stroke and statistically analyzes them and any inconsistencies in a work to validate or refute the authenticity of the piece. Although this may seem far-fetched, the practice is well-established in other fields, such as signature authentication.

"We've been able to mathematically capture certain subtle characteristics of an artist's work that are not necessarily visible to the human eye. We expect this technique — in collaboration with existing physical authentication — to play an important role in the field of art authentication.

"What's remarkable is not only that the mathematics confirms the expert opinion, but that — conversely — the true connoisseur is able to see similarities in detail in the body of an artist's works that is extracted by relatively sophisticated techniques," said Daniel Rockmore, Professor of Mathematics and Computer Science.

The software, which requires an enormous negative — 8" x 10", to be exact — that must be digitized at 16,852 x 18,204 pixels, has already supported the long-held belief that Perugino's "Madonna With Child," which resides in Dartmouth's own Hood Museum, is not entirely the artist's work, but includes the efforts of at least four other painters. In addition, of 13 Bruegel drawings from the Metropolitan Museum of Art in New York City, only eight were determined to be authentic.

**ATTENTION!**  
**ELECTRONICS**  
**TECHNICIANS**

**EARN YOUR**  
**B.S.E.E.**  
**DEGREE**  
**THROUGH HOME STUDY**



Our Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete the program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through our Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the engineering level. Advance rapidly! Many finish in 12 months or less! Students and graduates in all 50 states and throughout the world! Established Over 50 Years! Write or call for free Descriptive Literature. (601) 371-1351

**COOK'S INSTITUTE**  
**OF ELECTRONICS ENGINEERING**  
 4251 CYPRESS DRIVE, JACKSON, MISSISSIPPI 39212  
• FAX: (601) 371-2619

Visit us **TODAY** on the World Wide Web at <http://www.cooks.edu>



**CALL TOLL-FREE**

(800) 292-7711  
Orders Only

Se Habla Español

# C&S SALES

Secure On-line Ordering @ [cs-sales.com](http://cs-sales.com)

FREE GIFT with online purchase (use coupon code NV)

CALL OR WRITE  
FOR OUR  
**FREE**

64 PAGE CATALOG!  
(800) 445-3201

## Elenco Digital Multimeters

### Model M-1750



**\$24.95**

- 11 Functions:**
- Freq. to 20MHz
  - Cap. to 20µF
  - AC/DC Voltage
  - AC/DC Current
  - Beeper
  - Diode Test
  - Transistor Test
  - Meets UL-1244 safety specs.

### Model LCM-1950



**\$59.95**

- Large 1 3/4 Digit LCD
- Autorange Freq. to 4MHz
- Cap. to 400µF
- Inductance to 40H
- Res. to 4,000MΩ
- Logic Test
- Diode & Transistor Test
- Audible Continuity Test

### Model M-2795



**\$44.95**

- AC/DC voltage
- Current (10A max.)
- Beeper
- Frequency to 15MHz
- Capacitance to 200µF
- Transistor test
- Diode test
- Logic test
- Data hold
- Free holster

**Quantity Discounts Available**

## Test Equipment



### Elenco Handheld Frequency Counters

10Hz - 3GHz  
Models F-2800 & F-2850

- 10 digit display
- 16-segment RSSI bargraph
- Resolution to 0.1Hz (F-2850)
- Resolution to 1Hz (F-2800)
- Selectable gatetime (F-2850)

- Hi-speed (300MHz) direct count
- Includes NiCd charger and antenna

F-2800.....\$99

F-2850.....\$185

### Elenco Quad Power Supply Model XP-581

4 Fully Regulated Power Supplies in 1 Unit



**\$75**

4 DC Voltages: 3 fixed; +5V @ 3A, +12V @ 1A,  
1 variable: 2.5 - 20V @ 2A • Fully regulated & short  
protected • Voltage & current meters • All metal case

### Elenco Oscilloscopes

Free Dust Cover and x1, x2 Probes



2 year warranty

- S-1330 25MHz Delayed Sweep \$439
- S-1340 40MHz Dual Trace \$475
- S-1345 40MHz Delayed Sweep \$569
- S-1360 60MHz Delayed Sweep \$725
- S-1390 100MHz Delayed Sweep \$895

### Elenco RF Tracer 1MHz - 3GHz Model F-2700



**\$195**

- Pocket-size, easy-to-use
- Speaker/earphone/vibrate alerts
- 5-segment RSSI bargraph
- Low power consumption
- Includes NiCd, charger, and antenna
- Tells you if your room is bugged.

### Elenco 5MHz Sweep Function Generator w/ built-in 60MHz Frequency Counter Model GF-8056



**\$225**

Generates square, triangle, and sine waveforms, and TTL, CMOS pulse.

GF-8046 - 3MHz w/ counter \$199

GF-8025 - without counter \$99.95

### iBOTZ Hydrazoid Kit Model MR-1004



Walks and  
makes sounds

**\$29.95**

non-soldering

## Elenco Snap Circuits™

Elenco's new Snap Circuits™ make learning electronics fun and easy. Just follow the colorful pictures in our manual and build exciting projects, such as: FM radios, digital voice recorders, AM radios, burglar alarms, doorbells, and much more! You can even play electronic games with your friends. All parts are mounted on plastic modules and snap together with ease. Enjoy hours of educational fun while learning about electronics. No tools required. Uses "AA" batteries.

6 versions available.

Build up to **750** projects!

As low as **\$29.95**



Create  
Your Own  
Exciting Experiments



### Models Available

SC-750 - Extreme Version, contains over 80 parts to build over 750 experiments. Includes everything from SC-500 plus experiments in solar, electromagnetism, vibration switches, and 70 computer interfaced experiments.....\$119.95

SC-500 - Pro Version, contains over 75 parts including voice recording IC, FM radio module, analog meter, transformer, relay, and 7-segment LED display. Build over 500 experiments.....\$89.95

SC-300S - Deluxe Version, contains over 60 parts. Build over 300 experiments plus 20 bonus computer interfaced experiments.....\$74.95

SC-300 - Standard Version, same as SC-300S, but without bonus experiments.....\$59.95

SC-100 - Snap Circuits, Jr., contains over 30 parts. Build over 100 experiments.....\$29.95

## Elenco Educational Kits

### Model 21-880 Line Tracking Mouse Kit



**\$25.95**

Sound Activated Soldering Required

### Model AM-780K Two IC Radio Kit



**\$9.95**

### Model AK-700 Pulse/Tone Telephone Kit



**\$14.95**

### Model RCC-7K Radio Control Car Kit



**\$27.95**

7 Functions

Transmitter Inc. AK-870 (non-soldering) \$27.95

### Model M-1006K DMT Kit



**\$18.95**

18 Ranges

3 1/2 Digit LCD

Transistor Test

### Model K4001 7W Amplifier



**\$12.95**

K2837 - 2.5W Audio Amplifier - \$10.50

## Deluxe Soldering Irons

### Elenco 4-Functions-in-1 Instrument

**\$495**

Model MX-9300B

Ideal for labs, production lines, R&D and hobbyists!

### Sweep Function Generator

- 0.2Hz to 2MHz
- Sine, square, triangle, skewed sine, ramp, pulse, TTL level square
- VCF voltage 0 to 10VDC

### Digital Triple Power Supply

- Output #1: 0-30VDC, up to 2A
- Output #2: 5VDC, up to 2A
- Output #3: 15VDC, up to 1A



### Digital Multimeter

- 400mV - 400V AC/DC
- 20A max. AC/DC current
- Resistance to 40MΩ

### Frequency Counter

- 1Hz to 2.7GHz
- 7-digit display
- Selectable time base

### Weller® Low Cost

### Soldering Iron

Model WLC100



**\$34.95**

- Variable power control produces 5-40 watts.
- Ideal for hobbyists, DIYers and students.
- Complete with 40W iron.

## Electronic Science Lab

### Maxitronix 500-in-1 Electronic Project Lab

Model MX-909

Everything you need to build 500 exciting projects!

- Learn the basics of electronics. 500 different electronic experiments, special lighting effects, radio transmitter and receivers, sound effects, cool games and MORE!
- Includes built-in breadboard and an LCD.
- Explore amplifiers, analog and digital circuits plus how to read schematic diagrams.
- Includes 11 parts.
- Lab-style manual included.
- Requires 6 "AA" batteries.

MX-908 - 300-in-1 Lab \$69.95

MX-907 - 200-in-1 Lab \$49.95

MX-906 - 130-in-1 Lab \$39.95

EP-50 - 50-in-1 Lab \$18.95



**\$175**

## Guaranteed Lowest Prices

UPS SHIPPING: 48 STATES 7% (Minimum \$7.00)  
OTHERS CALL FOR DETAILS  
IL Residents add 8.5% Sales Tax

SEE US ON THE WEB

## C&S SALES, INC.

150 W. CARPENTER AVENUE  
WHEELING, IL 60090  
FAX: (847) 541-9904 (847) 541-0710  
<http://www.cs-sales.com>



15 DAY MONEY BACK GUARANTEE

2 YEAR FACTORY WARRANTY

PRICES SUBJECT TO CHANGE WITHOUT NOTICE



Putting the Spotlight on BASIC Stamp Projects, Hints, and Tips

# Stamp Applications

## Timing Is Everything

*The dreaded “I” word ... yes, everybody talks about it ... there’s lots of bloviating about it ... but what can we actually do with interrupts? Well, quite a lot, actually — if we’re patient and work carefully. Thankfully, SX/B makes interrupt programming more manageable than we thought it could be.*

It wasn’t very long after the BASIC Stamp and other BASIC language microcontrollers appeared that advanced users started asking about using interrupts. Well, neither the BASIC Stamp family nor — to my knowledge — any of the micros in the same class supports true interrupts; it’s just not practical in Basic and I’m about to explain why. Please, please, please ... don’t fill my Email basket with flame mail telling me that your favorite Basic language controller does do interrupts; let me qualify my statement.

Let’s back up a bit for those who may be a bit new. An interrupt is just that: an event or condition that suspends (interrupts) a program, forces the code into a special section (usually called an ISR, for Interrupt Service Routine), then goes back to what it was doing when the interrupt occurred. Sounds pretty simple and straightforward, right? Well, not quite.

Here’s why the BASIC Stamp and similar microcon-

trollers don’t support true interrupts (as I just described): What happens if we’re doing a bit-bang serial input (as most micros in the BASIC Stamp class do) and we get an interrupt? Well, if we process the interrupt, our serial timing is going to get trashed and we will corrupt the data — this could lead to a very big problem. The same problem holds true for any time-oriented function — things like **SERIN**, **SEROUT**, **PULSIN**, **PULSOUT**, **PAUSE**, **OWIN**, **OWOUT**, etc. You get the idea.

How is this handled, then? Well, the BS2p family has the ability to do what is called “pin polling.” When enabled, the BASIC Stamp 2p will check pin states in between high level instructions and act in accordance with the polling set up configuration (there are several options). This pseudo-interrupt process can be very useful. Now, I realize that some Basic language microcontrollers use hardware UARTs and timers and this does help alleviate the interrupt issue I just described. That said, the use of internal hardware occasionally limits design flexibility as specific I/O points on the micro are required. I’m not saying that any of this is bad ... it just is.


### Give Me an “I”

Okay, now that you know why the BASIC Stamp doesn’t support true interrupts, what about SX/B? For those of you who have checked it out, you’ve no doubt seen that there is indeed interrupt support. Yes, I’m going to show you how to use one type of interrupt this month — and to do two things with it: receive and buffer serial data (coming from a BASIC Stamp host) and to multiplex an eight-digit, seven-segment LED display.

The warnings I gave about interrupts above apply to SX/B — the difference is that SX/B allows interrupts any time you configure them. So, if you’re going to be using interrupts in an SX/B program, you should not be using any of the time oriented functions I mentioned earlier (note that SX/B does not have the one-wire commands of the BS2p).

As this is going to be a bit of a ride, let’s get right to it. I was in my favorite store the other day (yes, Tanner Electronics in Dallas, TX) and found a surplus eight-digit, seven-segment LED display that cost \$1.00; that’s

Figure 1. Serial data byte structure.

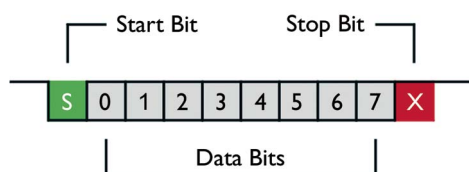

right, \$1.00. How could I not buy it? The question now was control. It's a common-cathode display, which means that the segment anodes for all eight digits are tied together. The only way to use such a display properly is with a multiplexing controller. Of course, I could use a MAX7219, but they're not cheap or easy to find anymore. Why not roll up my sleeves and create my own controller?

The idea was to create a serial LED controller that is AppMod protocol compatible — which means it could be controlled from one BASIC Stamp pin and can even share that pin with the line follower we created last month. While this seems to be a simple task on the surface, it does present a serious challenge.

To use the display properly, each active digit has to be refreshed at a regular rate. If we weren't doing anything else and the display was static, we could handle this in a program loop — especially in a compiled language like SX/B. The "problem" is that we want to be able to receive and buffer serial data at the same time. What this means for us, then, is that we will create an interrupt-driven program that multiplexes the display and handles the serial input.

## Bit-Bang Serial Interrupt Style

Take a look at Figure 1; this shows the structure of a serial byte in True (input idle state is high) mode. The stream begins with a start bit; this actually lets the receiver sync up and get ready for the incoming data bits, which will arrive LSB to MSB. At the end of the stream is a Stop bit period. Under non-interrupt conditions, the processor will simply loop until the serial line goes low to indicate a start bit. A timer is set for 1.5 bit periods so that the first bit is sampled in the middle of its period. After that, the timer is reloaded with the bit period and the rest of the sampling happens in a loop. If you want to see this for yourself, use **SERIN** in an SX/B program and look at the assembly code that gets generated.

In our project, however, we can't sit around waiting for the bit to come in, as we have to update the display periodically. What we have to do is sample the serial line at a rate that will let us accurately capture the incoming data. So, how fast do we sample? Well, I actually checked with programmers who are much better at this stuff than I am and the consensus was that — when doing interrupt-driven serial input — one should sample the serial line at least four times per bit period.

Okay, decision time. In order to know how fast to sample the serial line, we need to know what baud rate we want to support. For this project, I decided to go with 9600 baud, as this is somewhat standard for serial accessories and is supported by most micros. Also, if we can sample at 9600 baud, then lower baud rates will be no problem; they'll simply have longer bit timing periods.

At 9600 baud, the bit period is 104 microseconds

(1/9600). If we want to sample four times per bit period, we have to do that every 26 microseconds. So, that's our first hurdle: set the interrupt so that it activates every 26 microseconds.


To do this, we're going to program the SX to create a periodic interrupt based on an internal value called the RTCC (Real Time Clock/Counter). This eight-bit value can be incremented by a change of state on an external pin or by the oscillator that runs the SX. Since we can have a range of speeds to run the SX, we also have the ability to divide the oscillator frequency before sending it to the RTCC. This is called the prescaler and usually comes into play when we're running the SX at very high speeds (e.g., 50 MHz).

For this project, we'll run at 4 MHz, so the prescaler won't be required. What we'll have to do is set up the OPTION register in the SX to enable RTCC updates on the internal clock without being divided by the prescaler. Here's how:


```
OPTION = %10001000
```

This configuration allows RAM address \$00 to access the RTCC (bit 7=1) enable interrupt when the RTCC rolls over to zero (bit 6=0), increment RTCC on internal

# RF MODULES

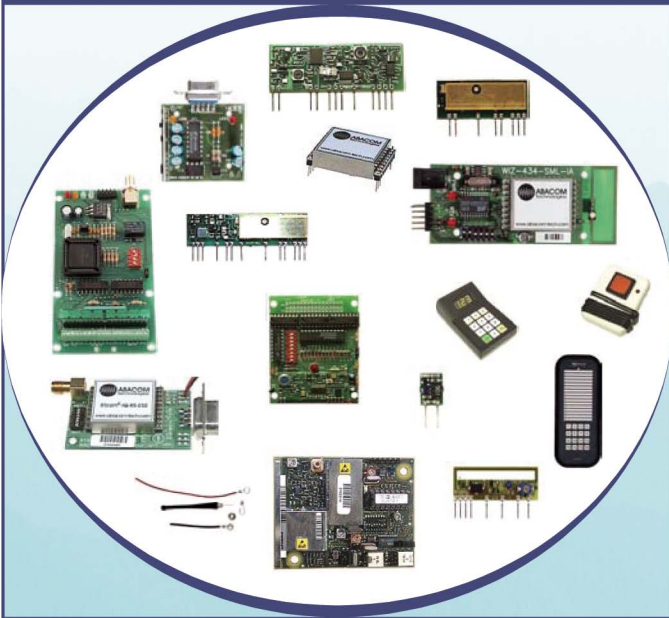

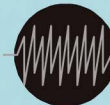[WWW.ABACOM-TECH.COM](http://WWW.ABACOM-TECH.COM)



**ABACOM**  
Technologies

Tel: +1(416)236 3858  
Fax: +1(416)236 8866  
[abacom@abacom-tech.com](mailto:abacom@abacom-tech.com)

instruction cycle (bit 5=0), and set the divide rate for the RTCC to 1:1 (bit 3=1). The SX28 documentation (download from Ubicom — [www.ubicom.com](http://www.ubicom.com)) goes into all the details of the OPTION register.

Okay, now that we've enabled interrupts, how do we make that happen at the desired interval of 26 microseconds? Here's what an empty ISR block looks like in SX/B:

```
INTERRUPT
    ' ISR code

RETURNINT 104
```

The key is actually at the end — the value following **RETURNINT**. This tells the SX how many cycles to run before generating an interrupt. How then, did we come up with 104? We start with the clock frequency of our project: 4 MHz.

At this rate, each instruction cycle takes 0.25 microseconds. Since we want our interrupt to trigger every 26 microseconds, we divide the instruction cycle speed into that. So, 26 divided by 0.25 is 104. This works because it is less than 255 (the maximum value of the RTCC). If you're ever doing a project where your interrupt cycles calculate to greater than 255, you either

have to reduce the oscillator speed or enable the RTCC prescaler.

At this point, our program will be interrupted every 26 microseconds — a rate that we've determined is fast enough to sample the serial input line enough to accurately capture data at 9600 baud. Okay, let's do it.

```
ISR_Start:
    ASM
    BANK $00
    MOVB C, Sin
    TEST rxCount
    JNZ RX_Bit
    MOV W, #9
    SC
    MOV rxCount, W
    MOV rxTimer, #BitTm15

RX_Bit:
    DJNZ rxTimer, Multiplex
    MOV rxTimer, #BitTm
    DEC rxCount
    SZ
    RR rxByte
    SZ
    JMP Multiplex

RX_Buffer:
    MOV FSR, #rxBuf
    ADD FSR, rxHead
    MOV IND, rxByte
    BANK $00
    INC rxHead
    CLRB rxHead.4
    ENDASM
```

Even though SX/B allows high level code in the ISR, we're not going to do that for the serial input. Why not? Well, there are two reasons: With assembly language, we can be a tiny bit more code-efficient and — even more importantly — the code was already written and working, so why not just use it?

Let me pause for a second and suggest that, if you're serious about programming the SX, you should consider the books that Parallax makes available: *Exploring the SX Microcontroller* by Al Williams (no, we're not related, but he lives in TX, too) and *Programming the SX Microcontroller* by Guenther Daubach. Both authors are great guys and very active in the Parallax support forums. You can get an SX starter kit that includes both books and — if you're on a budget — Al's book is available as a free PDF download.


Okay, back to the code. On entering the ISR, we want to make sure that we're pointing at the serial variables, so we issue a BANK \$00 statement to do that. Then, we sample the serial line by copying it into the SX Carry bit. When the serial line is idle, the Carry bit will now hold a value of 1. Let's continue to go through the code as if we're in the idle state. The TEST instruction will set the Zero bit if the register tested holds a value of zero. In our program, the variable rxCount is used to count down the

## Parts List Software for Engineers and Designers

- Easily create and manage multi-level parts lists for products in development...and after.
- Track sources for items with multiple price breaks.
- Calculate product costs at any quantity.
- Launch CAD, viewer or browser from any item.
- Automatically generate RFQs or POs.
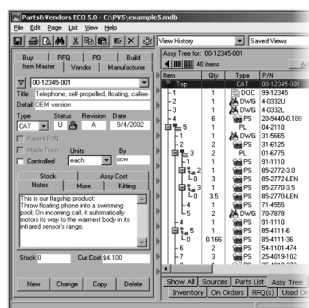
### New Version 5.0

- **New Report Layout Editor** customizes reports/labels.
- **New Connection to QuickBooks 2002/2003 Pro** simplifies accounting (us version only).
- **New Multi-currency** for foreign suppliers eases exchange rate calculations.



For Windows  
98/NT/Me/2K/XP  
3 Editions,  
starting at  
\$99 + s/h

**Parts & Vendors™**

Visit [www.trilogydesign.com](http://www.trilogydesign.com)  
and download our FREE DEMO.

**Trilogy  
DESIGN™**

Or, Call 800-280-5176  
530-273-1985 Fax 530-477-9106  
P.O. Box 2270, Grass Valley, CA 95945



bits as they're coming in; when rxCount is zero, we are not currently receiving a byte.

The next instruction, JNZ, will force the program to jump to RX\_Bit when the Z flag is not set — this happens when we are receiving (rxCount > 0). Since the Z flag is currently set, we will fall through the JNZ to where we load the value of 9 (start bit plus eight data bits) into the W register. After that, we will check the Carry bit; if it is 1 (and it currently is), we will skip the loading of rxCount and load the bit timer (rxTimer). With rxTimer loaded, we drop into RX\_Bit, where the timer is decremented and — if not 0 — the serial routine jumps to the label called Multiplex.

This process will repeat every interrupt cycle until a start bit is received. You may be wondering — as I did — why the rxTimer gets loaded when there is no start bit. Well, the reason there is no bail-out on a no start bit condition is that it actually adds more code than simply allowing the rxTimer to be loaded and the routine to exit.

Now, a start bit arrives; let's see what happens. This time, through, we will move 0 into the Carry bit. As rxCount is still 0, we will not jump to RX\_Bit, but we will end up moving 9 into rxCount (via W). Now, we load the rxTimer with 1.5 bit periods, decrement the timer for this interrupt cycle, and exit. On the next interrupt, we will have 9 in rxCount, so the code will jump right to RX\_Bit after sampling the serial line and then the rxTimer will be decremented again. This will continue until rxTimer is 0.

At this point, we're actually in the middle of the first data bit (the LSB). We will reload the rxTimer with the bit timing and then decrement the rxCount to account for the start bit. The program will drop through the SZ (skip, if zero) instruction, since rxCount is at eight and then move the data bit (currently sitting in Carry) into rxByte with the RR (rotate right) instruction.

Finally, the program will drop

through another SZ instruction and jump out of the serial routine to the Multiplexer.

This process will continue for eight bits. After the final bit arrives, rxCount will be 0 and the code will end up skipping the JMP Multiplex instruction and move to RX\_Buffer. This code will save the incoming byte to a 16-byte circular buffer. This will

let our foreground program handle important business while bytes are streaming in. That said, it's a circular buffer and — if we don't pull data from it before it fills — it can end up overwriting itself. That won't be a problem with our display.

The code at RX\_Buffer uses indirect addressing via the FSR (File Select Register) to update the circular

## It writes your USB code!

### NO Need to be a USB expert!

**HIDmaker (\$399)** – creates ready to compile PC & PIC programs that talk to each other over USB.

**Choose your favorite languages!**

**PIC:** Pic Basic Pro, CCS C, Hi-Tech C, MPASM. **PC:** VB6, Delphi, C++ Builder.

**Single chip solution:** PIC with built-in USB

**HIDmaker Test Suite (\$149)**

**USBWatch** – shows your device's USB traffic, even during 'enumeration', without expensive equipment.

**AnyHID** – Test any USB HID device. See what data it sends, even what the data is used for.




301-262-0300

WWW.TraceSystemsInc.com

## HOBBYENGINEERING

The technology builder's source for kits, components, supplies, tools, books and education.

### Robot Kits For All Skill Levels

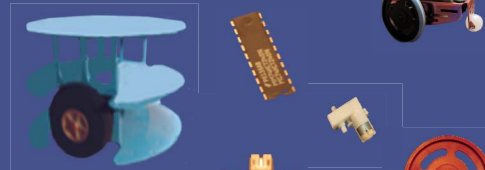

### Books and Educational Kits



### BEAM Kits and Components



### ICs, Transistors, Project Kits

### Motors, Frame Components and Scratch Builder Supplies.

Order by Internet, phone, fax or mail.

[www.HobbyEngineering.com](http://www.HobbyEngineering.com)

**1-866-ROBOT-50**

1-866-762-6850

1-650-552-9925

1-650-259-9590 (fax)

[sales@HobbyEngineering.com](mailto:sales@HobbyEngineering.com)

180 El Camino Real  
Millbrae, CA 94030

Visit our store near SFO!

Most orders ship the day received! World-wide shipping. Convenient payment options.

buffer. We start by moving the location of the first byte of the buffer into the FSR, then adding the head pointer (rxHead) to that. The MOV IND instruction takes the value of rxByte and puts it into the location being pointed to by the FSR. Then, we update the position of the head pointer and make sure that it stays within a 0 to 15 range by clearing bit 4. At the end of our serial section, we can terminate the assembly code block of our ISR with the **ENDASM** instruction.

Did you just take a big breath? I did! There will come a point when this all seems trivial, but — until you get to that point — you might want to review it a few times. It wouldn't hurt to map the position of the counters and bits on paper so that you make sure you understand it. By understanding how this works, you'll be able to modify it to suit your needs for a different application.

## Taking the Mystery Out of Multiplexing

Remember that our project has another important task: we have to multiplex the LED display, which means selecting the active column (cathode) and then

activating the appropriate segments (anodes) to create the desired pattern. We will handle this “in the background” via the ISR. This is actually much easier than the serial code though and can be done with SX/B instructions.


```
Multiplex:
    INC digPntr
    IF digPntr <= 7 THEN Next_Digit
    digPntr = 0

Next_Digit:
    Cathodes = NoDig
    IF digPntr > limit THEN ISR_Exit
    Anodes = anoBuf(digPntr)
    IF digBlank = 1 THEN ISR_Exit
    READ DigCtrl + digPntr, Cathodes

ISR_Exit:
    RETURNINT 104
```

The first step is to increment the variable called digPntr that points at the current active column. The next line will compare the value of digPntr to 7 (last legal column value) and, if digPntr is less than or equal to 7, then we will move on to Next\_Digit. Once digPntr hits 8,

Figure 2. SS8 schematic.

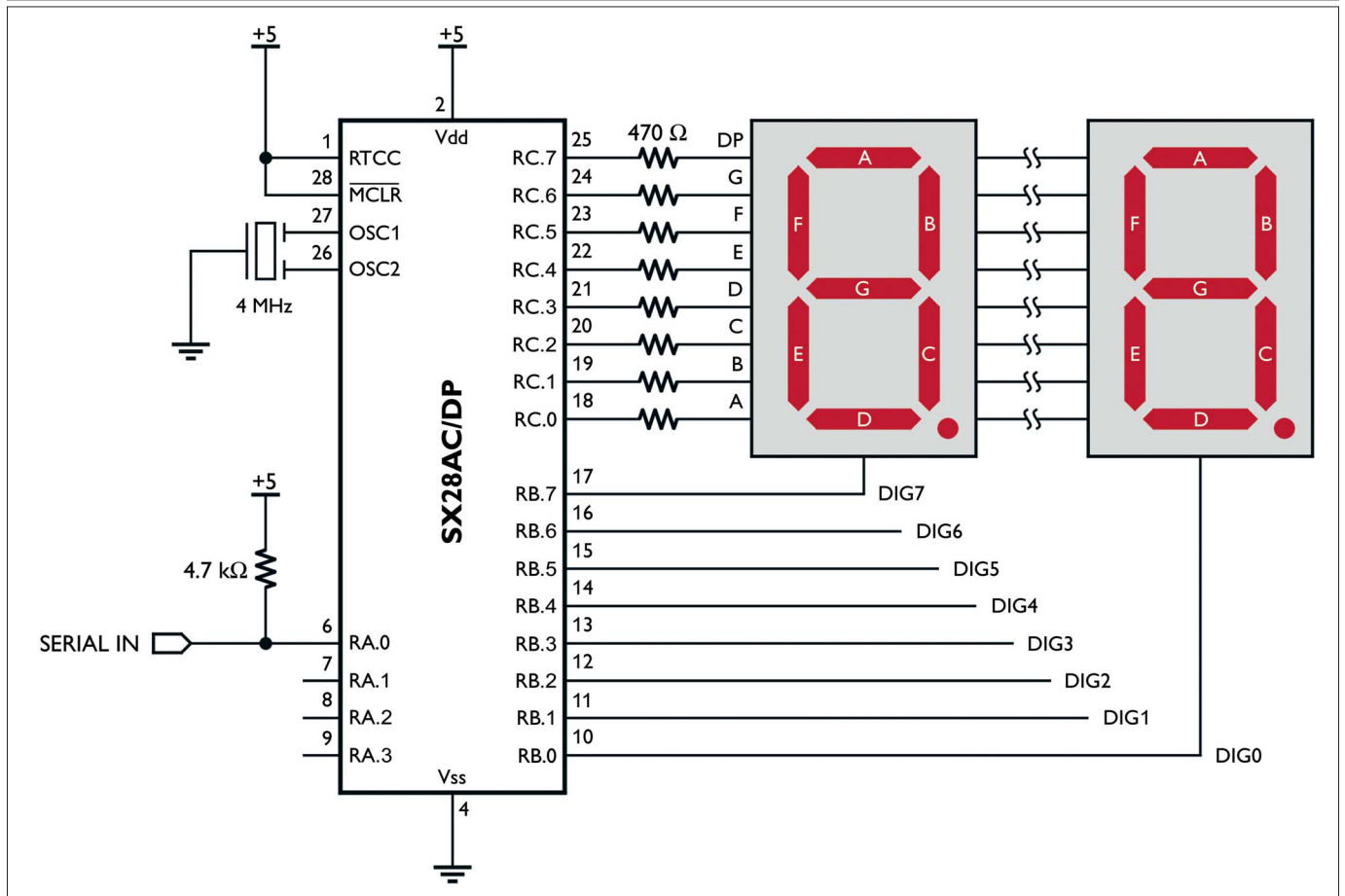

we will reset it before moving on. If you modify the program for a smaller display, be sure to update this section of code.

The code at `Next_Digit` actually updates the display. We start by turning it off — this will prevent ghosting when we change the anode (segments) values. Next, we're going to check a couple of values that can be set by the user via serial commands (more on that later). The first is the blanking bit, which turns the display off without affecting the contents of the display buffer. When blanking is enabled, we jump right out of the ISR before enabling the current column. The next value checked is the column limit. This lets us decide how many columns to activate (starting from the rightmost position). If the column pointer is beyond the column limit, we jump out of the ISR before activating the current column.

Finally, when blanking is off and the current column is active, we will move the contents of the anodes buffer for that column to the display. Then, we activate the column by setting its cathode control line to 0 and we're done.

Take another breath. The really cool thing about all this is that the multiplexing code was written in Basic — SX/B Basic. That's really neat. Now, before you get too excited, there is something very important to keep in mind: You must keep the longest path through the ISR to less than the number of cycles assigned to the ISR activation, minus three cycles (101, for this project). If we go over, what will happen is that an interrupt cycle may get ignored if it occurs while the current interrupt is still running (the SX disables interrupt while running the ISR) and this could be catastrophic for programs that require specific interrupt timing.

You can check the length of the ISR by looking at the assembly output — using Ctrl-L in the SX-Key editor is a quick way to do this. In this program, the final address of the ISR is \$0056 (86), so we're in good shape.

## Back to Easy Street

With the interrupt routine coded and working, the rest of the program is downright simple. Let's go through the important parts. In the beginning, we want to wait for the proper header string before processing any commands — this keeps us AppMod-compatible. The header for the LED controller is "ISS8" and will be followed by a command and one or more data bytes.

```
Main:
  GOSUB Get_Byte, @cmd
  IF cmd <> "!" THEN Main
  GOSUB Get_Byte, @cmd
  IF cmd <> "S" THEN Main
  GOSUB Get_Byte, @cmd
  IF cmd <> "S" THEN Main
  GOSUB Get_Byte, @cmd
  IF cmd <> "8" THEN Main
```

This code looks very similar to what we did in the line follower program. It simply goes through the input until the sequence "ISS8" is received. Remember that our serial input is being placed into a circular buffer by the ISR, so we need to write a routine to retrieve the first available byte.

```
_Get_Byte:
  IF rxTail = rxHead THEN _Get_Byte
  regAddr = __PARAM1
  temp1 = rxBuf(rxTail)
  INC rxTail
  rxTail = rxTail & $0F
  __RAM(regAddr) = temp1
  RETURN
```

Just as we did last time, we can pass the desired variable address by using the "@" preface. In the `Get_Byte` routine, this causes the address of that byte to be saved. Then the routine compares the value of the tail pointer (where we will get the byte) to the head pointer (where the next incoming byte will be saved). If these values are equal, the buffer is empty and we'll loop to the top of the routine until something arrives.

When the buffer isn't empty, we will move the byte currently sitting in the tail position to a temporary variable. As we did with the head pointer in the ISR, we have to update the position of the tail pointer and force it to stay within the 0 to 15 range of valid buffer addresses. Finally, we move the serial byte (sitting in `temp1`) to the variable specified by the caller by using the system `__RAM()` address. This is new in SX/B version 1.1 and makes it easy to modify or retrieve any SX RAM address.

Once we have the header, we will grab the command byte and then jump to a routine that takes care of any data or processing required by the command.

```
Get_Cmd:
  GOSUB Get_Byte, @cmd
  IF cmd = "R" THEN Do_Reset
  IF cmd = "C" THEN Do_Config
  IF cmd = "X" THEN Do_Blanking
  IF cmd = "W" THEN Do_Write
  IF cmd = "B" THEN Do_Block
  IF cmd = "<" THEN Do_ShiftL
  IF cmd = ">" THEN Do_ShiftR
  GOTO Main
```

To some, this structure may look a bit clunky, but keep in mind that SX/B is designed to be very close to assembly language. This lets the code compile very cleanly and, more importantly, it lets us learn from the compiled code. In many instances, you'll see that there is a one-to-one relationship between SX/B instructions and SX instructions. SX/B is built for speed.

Let's have a look at the valid instructions, starting with "R" for reset. The purpose of this command is to clear the serial buffer, clear the display buffer, and set the display mode for each column.



```

Do_Reset:
  GOSUB Get_Byte, @colMode
  rxHead = 0
  rxTail = 0
  limit = 0
  colEnable = %11111111
  FOR idx = 0 TO 7
    digBuf(idx) = 0
  NEXT
  GOSUB Update_Anodes
  GOTO Main

```

Note that the reset command allows us to specify the column mode bits. Since our display is eight digits wide, a single byte works perfectly. A “0” bit (default) indicates that the column is decoded — that is, the value in the data buffer will be translated to the appropriate patterns for the values 0 to F (15). A “1” bit in the mode byte will cause the raw bit’s value to be transferred to the display. This feature allows us to define other alpha characters and special patterns that may be used in animations (the BS2 demo program shows off this feature).

The rest of the reset code clears the serial input buffer, sets the display limit to one column, enables all columns (up to the column limit), and clears the display buffer (digBuf). After these changes are made, we have to call the Update\_Anodes subroutine as the anodes buffer is what gets transferred to the display in the ISR.

```

_Update_Anodes:
  FOR temp1 = 0 TO 7
    temp2 = 0
    temp3 = colEnable >> temp1
    IF temp3.0 = 0 THEN _Put_Dig
    temp2 = digBuf(temp1)
    temp3 = colMode >> temp1
    IF temp3.0 = 1 THEN _Put_Dig
  NEXT temp1
_Decode_Dig:
  temp2 = temp2 & $0F
  READ SegMaps + temp2, temp2
_Put_Dig:
  anoBuf(temp1) = temp2
NEXT
RETURN

```

This subroutine probably looks a bit more complicated than it is. The code loops through eight columns, first checking to see if a column is enabled. If it isn’t, the anodes buffer for that column is cleared. If the column is enabled, then we need to check the mode for that column. When the mode bit is “0,” we will take the low nibble of the column value and use it as an index into the patterns table that make up the shapes for the numbers 0 through F. If the mode bit for a column is “1,” the raw value is transferred to the anodes buffer. After the display is reset, we may want to change the configuration. Let’s say that we wanted to enable the rightmost three columns in decoded mode. Here’s how we could do that using a BASIC Stamp:

```
SEROUT Sout, Baud, [!"SS8C", 2, 0, $FF]
```

The first byte in the stream limits us to the third column (column 2). The next byte specifies that all columns are decoded (all bits are 0) and that all visible columns are enabled. Let’s look at the code that processes the “C” (configuration) command:

```

Do_Config:
  GOSUB Get_Byte, @limit
  GOSUB Get_Byte, @colMode
  GOSUB Get_Byte, @colEnable
  limit = limit MAX 7
  GOSUB Update_Anodes
  GOTO Main

```

As you can see, there is no magic here — we simply grab the bytes coming in and move them to their respective variables. The only byte of concern is the column limit, which has a maximum value of 7. The **MAX** operator handles this for us. Since the configuration command can change column display modes and enable bits, we need to call Update\_Anodes again to refresh the anodes buffer.

Before we run out of space, let’s actually put a value into the display, shall we? We’re going to use the “W” (write) command that will let us specify a column and a value to write to it.

```

Do_Write:
  GOSUB Get_Byte, @idx
  GOSUB Get_Byte, @cmd
  IF idx > 7 THEN Main
  digBuf(idx) = cmd
  GOSUB Update_Anodes
  GOTO Main

```

After retrieving the column and data values, we just need to make sure that a column value beyond our display has not been specified. If this happens, we exit to Main and leave the raw digits buffer alone. If the column index is good, then we update the digits buffer and — as we did before — we update the anodes buffer, as well. This updates the display. Before we go, let’s look at a bit of PBasic code that can run the project — it will make sense of some of the main features.

```

idx2 = 0
FOR cntr = 1 TO 100
  FOR idx = 0 TO 2
    SEROUT Sout, Baud, [!"SS8W", idx, cntr DIG idx]
  NEXT
  SEROUT Sout, Baud, [!"SS8W", 7, 1 << idx2]
  idx2 = idx2 + 1 // 6
  LOOKDOWN cntr, <[10, 100, 1000], last
  LOOKUP last, [$FE, $FC, $F8], cMode
  LOOKUP last, [$C1, $C3, $C7], cEnable
  SEROUT Sout, Baud, [!"SS8C", 7, cMode, cEnable]
  PAUSE 100
NEXT

```

The purpose of this code is to display a three-digit counter in the display, as well as run a little animated "bug" on the left. The main loop handles the counter. At the top of the main loop is a smaller inner loop that uses the Write command to send the counter digits to the display.

Notice how convenient the **DIG** operator is for us in this application. The next section animates the outside segments of the leftmost display. It's a very simple attention getter.

Now that we have data in the SS8 buffer, we need to configure the display so that digits are shown on the right and the animated "bug" on the left.

With **LOOKDOWN**, we can determine how many columns the current count value occupies and, with that value, **LOOKUP** will give us the proper column mode and enable bytes. This lets us blank leading zeros and create a more professional looking display.

One of the things that you probably noticed is that the column mode and column enable bytes can — in some cases — be used to accomplish the same thing.

If I'm being honest, the column enable feature was a late addition to the project and this came after a lot of display experimenting. One technique that I experimented with while I was developing the code was prewriting to the display, and then revealing the display column by column by updating the column enable byte.

Well, it's up to you now. I will admit that programming the SX — even with SX/B — can be challenging, however the rewards are really worthwhile.

If you use this display project as a guide, you can build any number of serial accessories that require buffered input. But be sure to download the SX documentation for the Ubicom, and please do check out the books I told you about; they will really make your journey into SX mastery far easier.

By the way, please feel free to contact me at the email address provided. I look forward to hearing from *Nuts & Volts* readers!

Have a Happy New Year! And until next time ... Happy Stamping. **NV**


**Jon Williams**  
jwilliams@parallax.com  
**Parallax, Inc.**  
www.parallax.com

## WIRELESS MADE SIMPLE™

BRING YOUR WIRELESS PRODUCT QUICKLY AND LEGALLY TO MARKET
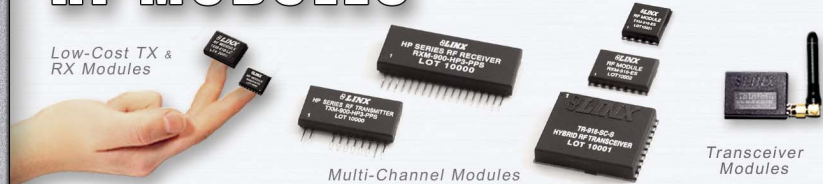
### RF MODULES

Add **INSTANT** wireless analog / digital capability to your product.



### OEM PRODUCTS

FCC PRECERTIFIED & ready to customize for your application.



### ANTENNAS

From ceramic chips to gain yagis, keyless entry to WIFI.



**LNKX**  
TECHNOLOGIES  
WIRELESS MADE SIMPLE  
www.linxtechnologies.com


**Digi-Key**  
www.digikey.com  
1-800-DIGI-KEY

Proudly Distributed by:  
**RF DIGITAL**  
WIRELESS  
www.rfdigital.com  
1-818-541-7622

# TechKnowledge 2005

## Events, Advances, and News From the Electronics World
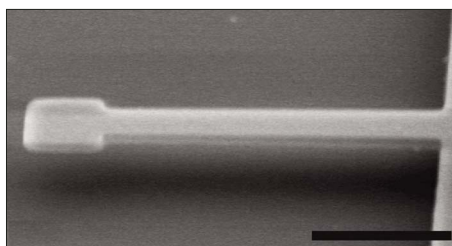
### Advanced Technologies Oscillator Senses Viruses



Scanning electron micrograph of a cantilever oscillator 6  $\mu\text{m}$  long, 0.5  $\mu\text{m}$  wide, and 150 nm thick, with a 1  $\mu\text{m}$  square paddle. The scale bar corresponds to 2  $\mu\text{m}$ . Courtesy of Craighead Group, Copyright Cornell University.

**S**uppose you want to measure an extremely small entity, such as a bacterium, a virus, or the amount of weight you have lost by taking Cortislim®. A standard scale just won't do the job; you'll need an exotic device that is capable of detecting extremely low mass. No problem there, though, if you have access to a cantilever oscillator developed at Cornell University ([www.cornell.edu](http://www.cornell.edu)).

The principle is pretty simple. Think of a kitchen knife that you just tossed across the room, sticking it into the front door. It will quiver on its own for a short time, using energy left over from the throw. After that, if you make the door vibrate at the knife's resonant frequency, the knife will respond with the same lateral oscillation.

The knife's resonant frequency depends partially on the mass of the handle, so — if you stick a piece of gum on it — the resonant frequency will change. Obviously, it would be possible to compute the

mass of the gum if you have a basic knowledge of how a change in mass affects the resonant frequency.

To enable such measurements on a nanoscale level, Cornell researchers simply substituted a silicon paddle for the knife and reduced its length to 6 to 10  $\mu\text{m}$ . If you mount the paddle on a piezoelectric crystal instead of your front door, it can be made to vibrate at frequencies of 5 to 10 MHz. By adding a few virus particles to a paddle, you can change its resonant frequency by about 10 kHz, which is easy to detect.

In the reported experiment, researchers were able to sense as few as half a dozen viruses and they believe the device to be inherently sensitive enough (down to about 0.41 attograms) to sense just one. The type of viruses used in the experiment (*Autographa californica* nuclear polyhedrosis, in case you care) weigh about 1.5 femtograms. One complication is that air has a tendency to damp the paddle's vibration, so measurements must be made in a vacuum, but it is otherwise pretty straightforward.

With development, the technique could provide a practical way to look for other viruses, DNA, proteins, and toxic organic chemicals. In addition, by using arrays of paddles, one could build a simple field detector that tests for a range of pathogens in a single pass.

### Speed of Light = 670 MPH

**I**f you want to communicate over long distances using optical

fibers, it's usually a good thing that light travels at roughly 186,000 MPS. However, light occasionally needs to be slowed down so signals can be routed, converted, or synchronized. A common way to do that is to feed it into a loop, but it currently takes 300 km of fiber to delay an optical signal for a thousandth of a second, so it would be really helpful if you could slow it down.

It now appears that physicists at the National Institute of Standards and Technology (NIST, [www.nist.gov](http://www.nist.gov)) have figured out a way to do that. The key is the optical soliton — a solitary, intense light pulse that can travel long distances without changing its shape or spreading out. The NIST people have shown that it is possible to use a very stable pulsed laser to create a soliton that travels slowly through a cryogenic gas of rubidium atoms for more than 5 cm without noticeable distortion.

Using this principle, the soliton could travel at one millionth of the usual speed of light and the 300 km of optical fiber could be reduced to a few centimeters. The next step for NIST scientists is to translate the theory into practical experiments. The long term goal is to help simplify and reduce the cost of high speed optical communications.

### Computers and Networking "Fastest Computer" Title Changes Hands Again

**L**ast September, IBM's Blue Gene supercomputer became the big





NEC's SX-8 is rated at up to 65 TFLOPS when configured with 512 nodes. Courtesy of NEC Corp.

dog on the block by achieving 36.01 TFLOPS performance, based on the Linpack benchmark.

However, NEC Corporation ([www.nec.com](http://www.nec.com)) has announced the worldwide launch of its model SX-8, claiming that it can deliver 65 TFLOPS.

Using the same vector architecture as NEC's Earth Simulator, the new product combines enhanced CPUs with improved memory and I/O processing performance.

An enhanced, single-chip vector processor — also used by the SX-6 — contributes to the improved price performance and space savings offered by the SX-8. The machine is intended for use in fields that require large scale and ultra high speed computing of massive data, such as meteorological forecasting, environmental simulations, and automotive crash analysis.

The single-node model (which can include up to eight CPUs) will give you only 128 GFLOPS, so you'll need to order a multiple-node to achieve peak performance. Monthly rental charges are reported to start at about \$11,000.00.

Keep in mind, however, that the "fastest supercomputer" crown is still being passed around and IBM plans to get it back by delivering a 360 TFLOP machine to the Lawrence Livermore Laboratory later this year.

## New Portable USB Hard Drives




Western Digital's Passport drives are compact and require no separate power supply. Courtesy of Western Digital Corporation.

Late in 2004, Western Digital Corporation ([www.western-digital.com](http://www.western-digital.com)) unveiled the Passport line of portable USB hard drives offering a choice of 40 or 80 GB capacities and (in most cases) no need for a separate power supply. The drives are based on the 2.5 inch Scorpio mechanism, include the company's Data Lifeguard data protection, and are packaged in a rugged case.

According to the vendor, WD

Passport Portable Drives are able to withstand the rigors of mobile professionals and other users who need to carry substantial amounts of data with them. A detailed product spec sheet and photos of the drives are available on the company's website. The list price is \$199.00 for the 40 GB version and \$249.00 for the 80 GB one.

## Playing With Disaster

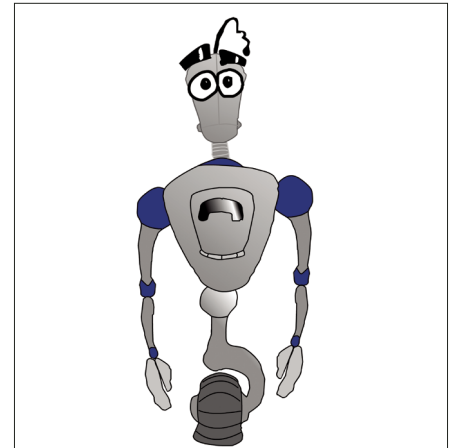

Disaster Dave helps kids learn disaster readiness skills in "Disaster Dave's Misadventures," a new educational computer game developed by Purdue Extension and the Federal Emergency Management Agency.

For those who want to teach children in the community about

## The Standard for checking Capacitors in-circuit



Good enough to be the choice of Panasonic, Pioneer, NBC, ABC, Ford, JVC, NASA and thousands of independent service technicians.

Inexpensive enough to pay for itself in just one day's repairs. At \$199, it's affordable.

And with a 60 day trial period, satisfaction guaranteed or money-back policy, the only thing you can lose is all the time you're currently spending on trying to repair all those dogs you've given up on.

### CapAnalyzer 88A

Available at your distributor, or call 561-487-6103

**Electronic Design Specialists**

## Locate shorted or leaky components or conditions to the exact spot *in-circuit*

Still cutting up the pcb, and unsoldering every part trying to guess at where the short is?

\$199 

Your DVM shows the same shorted reading all along the pcb trace. LeakSeeker 82B has the resolution to find the defective component. Touch pads along the trace, and LeakSeeker beeps highest in pitch at the defect's pad. Now you can locate a shorted part only a quarter of an inch away from a good part. Short can be from 0 to 150 ohms

### LeakSeeker 82B

[www.eds-inc.com](http://www.eds-inc.com)

## Amazing Devices

[www.amazing1.com](http://www.amazing1.com)

### Anti Gravity Projects

All new mini 35 kv 1.5 ma adjustable output power supply with instructions on making a simple craft.



**GRA1K Kit** ..... \$69.95  
**GRA10 Assembled** ..... \$119.95


### Green Lasers Pointers with Colimator

10,000 feet plus - Full 5 mw. A real beauty!!

**LAPNGR5 Ready to use**...\$129.95
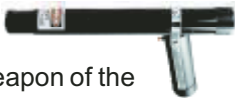
### Ion Ray Guns

Potential concept for the ultimate weapon of the future. Produces force fields, induces shocks and other weird effects.



**IOGHP1 Plans** ..... \$10.00  
**IOGHP1K Kit** ..... \$149.95  
**IOGHP10 Assembled** ..... \$249.95

### Laser Window Bounce

Receiver and laser illuminator modules for building a listening device.



**LWB9 Plans complete system**...\$20.00  
**Infra Red Laser Module**  
**CWL1K Kit** ..... \$199.95  
**CWL10 Assembled** ..... \$299.95  
**Optical Receiver with Voice Filter**  
**LLR4K Kit** ..... \$149.95  
**LLR40 Assembled** ..... \$199.95

### Electrokinetic Guns

Fires an actual projectile using a magnetic pulse. Advanced project must be used with caution. Battery powered.



**EML3 Plans** ..... \$10.00  
**EML3K Kit** ..... \$69.95

### Information Unlimited

Box 716, Amherst, NH 03031 USA  
 Orders: 1-800-221-1705  
 Fax: 1-603-672-5406  
 Email: [riannini@metro2000.net](mailto:riannini@metro2000.net)  
 Catalog \$2.00

## TechKnowledgey 2005

disaster readiness (and perhaps scare the bejeebies out of them at the same time), "Disaster Dave's Misadventures" — an educational computer activity — has been developed by Purdue University Extension with funding from the Federal Emergency Management Agency (FEMA).


Now available to the public, its focus is to teach disaster readiness skills in a fun and entertaining fashion with the assistance of "Disaster Dave," whom students help navigate through a variety of natural and other disasters. Faced with blizzards, tornadoes, hazardous materials spills, and national security emergencies, Disaster Dave's fictional community is either destroyed or spared, depending on the skills and knowledge of the player.

In one activity, for example, Disaster Dave faces a snow emergency. He has to decide how and when to take shelter and what items to pack in disaster supply kits. If Dave makes the right choices, the city and its residents make it through the storm.

However, if he makes poor choices, the simulated story worsens and the city is trashed (pretty much like Washington, DC, every time it snows). Single copies are available for \$10.00 and organizations can buy a set of 25 for \$150.00. Details are available at [www2.ces.purdue.edu/eden](http://www2.ces.purdue.edu/eden)

with part numbers P/N 9364U, P/N 7832D, or P/N 4983D. For more information, visit [www.delladapterprogram.com](http://www.delladapterprogram.com)
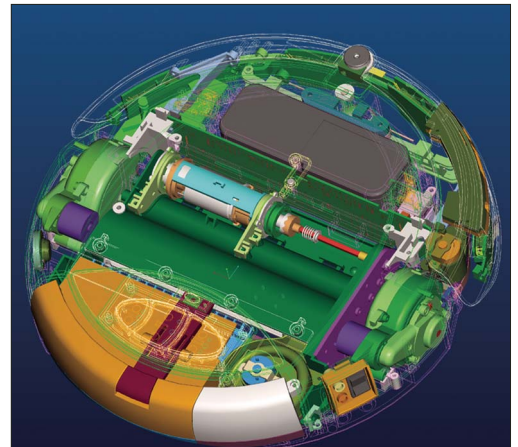
### Circuits and Devices Robot Passes 1 Million Sales Level



This CAD rendering of the Roomba shows that there is much more to this robot than meets the eye. Intricate sensors are required for everything from drop offs, walls, pets, and floor coverings.

Two decades ago, we imagined a future in which intelligent robots would free humanity from dull, dangerous, and repetitious labor, dutifully generating previously unimagined prosperity and freeing us for a pursuit of happiness unencumbered by material needs.

We have fallen a little short of

### Power Supplies Recalled

If you own a Dell Latitude, Precision, or Inspiron notebook computer and bought it between September 1998 and February 2002, you'll want to take a look at the power supply. About 990,000 of them — manufactured by Delta Electronics — are being recalled because of a risk of fire or electrical shock. The afflicted adapters are marked



iRobot wizard Joe Jones discusses the engineering behind the steering and drive mechanisms of the Roomba.

that, but at least many of us have stopped vacuuming our floors. Yes, as of late 2004, more than a million people had purchased the \$200.00 Roomba robotic floor vacuum from iRobot ([www.irobot.com](http://www.irobot.com)).

Well, maybe having an oversized hockey puck wandering around your house isn't all that romantic, but owners generally report that it actually works. The Roomba has infrared sensors that allow it to follow walls and avoid falling down stairs, wheel-drop sensors that stop the unit when it is lifted, and a bump sensor that keeps it from interfering with furniture and other objects on the floor.

It also employs a flapper-and-brush system to pick up large particulates and a high velocity nozzle that sucks up small particles, such as dust. The latest Discovery and Roomba Red models add a system called Dirt Detect that senses particularly dirty areas and tells the robot to concentrate on them until they are clean.

One reviewer noted that his Roomba (affectionately named "Monica") doesn't do stairs or baseboards, requires frequent emptying, and can leave dirt when moving from tile to carpet.

However, he noted that it provides a cleaner house, with very little effort and at an affordable price. Now, if they can only get it to feed and walk the dog, we would all be set!

## Humidity Sensor/Controller Introduced

If your latest design employs sensitivity to moisture or temperature, you may be interested in the HS-2000C humidity sensor/controller from Precon, Inc. ([www.preconusa.com](http://www.preconusa.com)), which combines analog moisture and temperature sensing with dual channel on/off control capability.

Based on user requirements, high and low limits are embedded in the device at the factory and it can be configured for either direct or reverse action. The two outputs will equal either zero or the supply voltage, which can range from 2 to 5 V. Proportional control, LCD display, and various packaging options are also available. The dime-sized HS-2000C is a little pricey at \$35.00, but it is available in small quantities with no programming charge. Accuracy is rated to  $\pm 2$  percent, with good stability from -30 to +100°C.

## Industry and the Profession Things Sneaking Under Your Hood

For many years, "black boxes" have been used in commercial aircraft to gather and retain crash data. You may not be aware of it, but similar devices are now appearing in noncommercial Earth-bound vehicles, including passenger cars and trucks. In fact, the devices were installed in all 2004 General Motors cars and several Ford models.

In its usual standardization role, the Institute of Electrical and Electronics Engineers (IEEE, [www.ieee.org](http://www.ieee.org)) recently published IEEE Standard 1616 for motor vehicle event and data recorders (MVEDRs), which is the term for equipment that collects, records, stores, and provides readout data about your vehicle's operation.

The information includes vehicle speed and changes in velocity, how many occupants are in the car, seat belt use or lack thereof, braking and steering data, geographic location, direction of travel, and other items, all linked to dates and times.

Proponents of MVEDRs argue that the digital data can complement accident information collected from victims and witnesses, improve vehicle design, reduce fraudulent insurance claims, and provide other useful benefits. However, many privacy advocates doubt the desirability of giving insurance companies and law enforcement agencies the ability to download a history of everything your car has experienced from the very moment you took it home and to use this information against you in unfortunate situations.

If you have any misgivings, it is now time to make them known to the auto companies and your elected officials. **NV**

## PC KEYBOARD EMULATION

*Interface Keyboards, Switches, and RS-232 to your PC Keyboard Input*

### Model KE24

**ONLY \$99.95**

- PS/2 Keyboard Emulation
- Up to 12 x 12 matrix
- Programmable
- RS-232 Port



The KE24 is the ultimate in flexibility. Inputs from keypads, switches, or serial data can emulate any of the 104 keys from a standard keyboard.

### Model KE18

**ONLY \$44.95**

- 9 x 9 matrix or 18 Individual inputs
- 2.5" x 3.0" size
- PS/2 Keyboard Port



The KE18 provides a quick and easy interface to the PS/2 port from your switches and keypads.

**HAGSTROM ELECTRONICS, INC.**

11 Fiddlers Green, Lansing, NY 14882



**Toll Free: 888-690-9080**

**Phone: (607) 533-4441**

**Fax: (607) 533-4443**

**[www.hagstromelectronics.com](http://www.hagstromelectronics.com)**



The Business of Electronics Through Practical Design and Lessons Learned

# In The Trenches

## Analog to Digital Conversion Considerations

Using an Analog to Digital Converter (A/D) is really a fairly easy task for most non-critical applications. Unfortunately, there seems to be a lot of confusion about the steps that are necessary for a good conversion to take place.

This month, we'll examine the error sources and problems that occur when the necessary attention to detail is ignored.

### The Sample and Hold

We'll limit this discussion to the common successive-approximation class of A/D converters. Perhaps because the manufacturers have made them so "easy" to use, hobbyists and engineers don't always stop to think about what actually happens when they press the "convert" switch. Without a doubt, carelessness is

the major cause of improper A/D function.

There was a time when you had to buy a separate sample/hold (or track/hold) IC and attach it to your A/D.

Nowadays, everything is integrated into one chip and, in many cases — as with microcontrollers ( $\mu$ Cs) — the A/D is only another feature. Just because you don't see the sample/hold doesn't mean that it isn't important or that it can be ignored. It is a critical piece of the conversion process. Understanding how it operates is important in understanding the limitations of the A/D.

Fundamentally, the sample/hold is just a means of stopping the input signal from changing during A/D conversion. The successive approximation procedure requires that the input signal be fixed; otherwise, the conversion can be corrupted. This is because there are  $N$  sequential comparisons for an  $N$ -bit converter. An eight-bit A/D needs eight comparison steps and a 16-bit A/D needs 16 steps, etc.

Obviously, these steps take time. If the input signal changes halfway through the sequence, the second half will represent the changed value. You can see that even a small input change can result in a really fouled-up binary number.

A practical example will show the importance of the sample/hold. Let's say that you have a 12-bit A/D — *without* a sample/hold — that takes  $1\ \mu\text{s}$  for each of the 12 steps for a conversion speed of  $12\ \mu\text{s}$ . What is the fastest sine wave it can



1010 Jorie Blvd. #332  
Oak Brook, IL 60523  
1-800-985-8463  
www.atomictime.com

|  |  |  |
|--|--|--|
|  <p><b>H15U</b></p>  | <p><b>Office School Clock #1</b><br/>WT-3121A \$39.95&gt;</p> <p>This wall clock is great for an office, school, or home. It has a professional look, along with professional reliability. Features a manual set option, daylight saving time disable option, and a safe plastic lens and case.</p>                  |  <p><b>WT-3121A</b></p>   |
|  <p><b>56G24-4</b></p>   | <p><b>Arcron Atomic Watch</b><br/>&lt;56G24-4 \$249.99</p> <p>This elegant watch features a shock-resistant titanium case with hardened mineral lens. Silver dial with arabic numerals, and high quality replaceable leather band. Watch can change to any world time zone. Case diameter 40mm. Made in Germany.</p> |  <p><b>WS-8007U-C</b></p> |
| <p><b>1-800-985-8463</b><br/>www.atomictime.com</p> <p>Tell time by the U.S. Atomic Clock - The official U.S. time that governs ship movements, radio stations, space flights, and warplanes. With small radio receivers hidden inside our timepieces, they automatically synchronize to the U.S. Atomic Clock (which measures each second of time as 9,192,631,770 vibrations of a cesium 133 atom in a vacuum) and give time which is accurate to approx. 1 second every million years. Our timepieces even account automatically for daylight saving time, leap years, and leap seconds. \$7.95 Shipping &amp; Handling via UPS. (Rush available at additional cost) Call M-F 9-5 CST for our free catalog.</p> |  |  |

sample without error? Re-stating this in different terms: what is the fastest sine wave that doesn't change by one Least Significant Bit (LSB) in 12  $\mu\text{S}$  (given a full-scale sine wave)?

One LSB is 1/4,096 or 0.000244 of full-scale. This is also 0.0140 degrees of a sine wave. So, the signal can't vary 0.0140 degrees in 12  $\mu\text{S}$ . There are 25,714 of these 0.0140 steps in a full 360 degree sine wave. Each step requires 12  $\mu\text{S}$ . So 25,714 steps at 12  $\mu\text{S}$  each give a period of 0.3086 seconds or a 3.24 Hz frequency. That's right. Without a sample/hold, the 12-bit A/D is frequency limited to about 3.34 Hz, even though the conversion takes only 12  $\mu\text{S}$ . Now, it is clear why the sample-hold is needed.

A sample-hold is simply a capacitor that can be disconnected from the input signal. When this is done, it maintains its charge — for a while, anyway. No capacitor is perfect. There is leakage through the capacitor insulation. This is called "droop." Obviously, you don't want the droop to be more than one LSB over the conversion interval. This means that you want a large value capacitor.

Unfortunately, a large value capacitor requires a large charging time, as well as large charging current, so there is a trade-off. Most manufacturers make the hold capacitor as small as possible for maximum speed. If the conversion speed is fast enough, a small capacitor will work well.

There is also the series resistance of the IC to the capacitor. No switch conductor is perfect. This means that there is a resistor-capacitor (RC) network made from the hold capacitor and the input resistance. This causes a delay or phase error. We'll discuss phase error in more detail later.

How big are the RC values? Let's look at the popular Microchip PIC  $\mu\text{C}$ . The basic eight-bit A/D is detailed in the section titled "A/D Sampling Requirements," as well as in Sections 21 and 22 of the 1997 PIC Micro Mid-Range MCU Family Reference Manual. Here, you find that the hold capacitor is about 51 pF and the series resistance (due to the electronic switch) is about 7,000  $\Omega$ .

It should be noted that this resistance varies considerably with supply voltage. They provide lots of detail on the A/D hardware. (Some other companies don't.) Since the Microchip people are very considerate, they have tables that specify the proper A/D clock rates for various system clock speeds. You don't have to actually figure them out for yourself. It is very important to follow their advice; otherwise, your A/D may lie to you.

## Nyquist Nonsense

It is true that, if you sample more than twice the highest frequency of interest (Nyquist limit), you can recover the complete signal, but it is only true if you process those samples with a Fast Fourier Transform (FFT) or other

sophisticated digital signal processing procedure. For virtually all applications using a small  $\mu\text{C}$ , this is not practical.

This means that Nyquist is not really useful to apply. The idea that you won't have any errors if you sample at the Nyquist limit is simply wrong. Trying to apply Nyquist-like concepts to a system without digital signal processing invariably causes problems. Let's look at some examples (in systems without digital signal processing).

## Filtering

I've seen people work very hard to eliminate all higher frequency components from their signal before applying it to their A/D because they remember that aliasing can occur. Aliasing is caused when sample clock and signal frequency mix or "beat." This beat frequency cannot be distinguished from a real signal of that frequency after sampling. (There are special exceptions to this rule.) After all, this is what they were taught and this is what they're going to do! Unfortunately, blind faith is a poor virtue in engineering.

Here's an example: A robot had photo-interrupters on two wheels that were used to determine rotation rate and

# USB DAQ

## LabJack U12

Available now for only ...

**\$119** qty 1  
**(\$99** qty 10+)



USB Data Acquisition  
& Control

- \* Built-in screw terminals
- \* Easy-to-use USB
- \* Everything included
- \* Use with C, VB, LabVIEW, etc.
- \* Windows 98SE/ME/2000/XP
- \* 12-bit analog inputs (8)
- \* 10-bit analog outputs (2)
- \* 20 digital I/O
- \* 32-bit counter



Made in Colorado, USA, by LabJack Corp.  
info@labjack.com, (303) 942-0228

**www.labjack.com**

wheel position. These signals peaked at 3 volts and were roughly rectangular in shape, so an A/D was used (rather than a digital method). We all know that square or rectangular wave shapes have loads of higher-order harmonics, so a filter was needed. Right?

Unfortunately, in this case, filtering simply made things very bad. The filters actually worked very well. The resultant wave looked very much like a sine wave. All the higher frequency components were removed, but what really happened was that the system was changed from measuring time relationships to voltage relationships. A little dirt on the sensor changed the voltage levels, which the software saw as a changed wheel position. Performance was poor. Removing the filter made things much better. Why?

It goes back to the sample-hold we talked about before. First, there was the RC network that acts like a low-pass filter, but — much more importantly — the sample-hold was disconnected from the signal during conversion. All those higher order harmonics were not present in the "held" sample.

Fundamentally, the analog signal

was changed to a stepped-DC signal, which significantly reduced the high frequency components automatically. (This is not true for some special very high speed A/Ds.)

I don't think I've ever used an anti-aliasing filter on a  $\mu$ C product. I've filtered to reduce noise, to eliminate strong RF (which can really create problems), and to clean up signals. You will need a filter if you are going to recreate the input signal with digital signal processing or, perhaps, if you are sampling a signal close to the Nyquist limit. If you know what your input signal is and how your A/D works, you really should be able to anticipate most near-Nyquist problems.

## Amplitude Errors

No A/D will ever provide you with the precise maximum or minimum value for a sine wave. It may be close. It may be so close that it doesn't matter, but it won't be exact. If you think about it, it becomes clear. The sample-hold capacitor is connected to the signal for a finite time. During that time, it effectively averages the signal. Therefore, the single peak value will be diluted with

lower than peak values (and vice versa for the minimum value), but this isn't the major cause of amplitude errors. The biggest source of amplitude errors comes from the sampling rate.

Let's look at an example. You have a 1,000 Hz sine wave that you sample at 100,000 Hz. It seems like 100 samples per cycle should be adequate, right? If you use 100 conversions per sine wave, you will have one conversion every 3.6 degrees. So, you can have up to a 3.6 degree error in amplitude. At the zero crossing point, this corresponds to a 6.3% amplitude error. You may have thought that your eight-bit A/D converter would provide 0.4% error. In reality, you will have only 6.7% error ( $6.3\% + 0.4\%$ ).

How many samples per cycle are needed for one LSB error? With eight bits, there are 256 amplitude levels, with the worst case/largest level being 0.224 degrees (inverse sine of  $1/256$ ). There are about 1,607 of these increments per 360 degrees ( $360/0.224$ ). This means that you have to sample at 1,607 samples per cycle or 1.607 MHz for a maximum 0.4% amplitude error. Don't forget to add in the basic A/D error of 0.4% for a total error of 0.8%. Faster sampling will reduce the error, but you will always have a minimum A/D error of 0.4%.


## Frequency/Period Errors

Generally, you don't directly measure the frequency of a signal with an A/D. Rather, you measure the period of a single cycle and invert it to get the frequency. Naturally, there are errors that show up here, as well.

Let's look at our 1,000 Hz signal, sampled at 100,000 Hz. As we noted above, each sample is 3.6 degrees and, therefore, the basic error can be 3.6 degrees. This means that, instead of 360 degrees per period, it could be 356.4 degrees. This is an error of 1% (obviously, because we are sampling
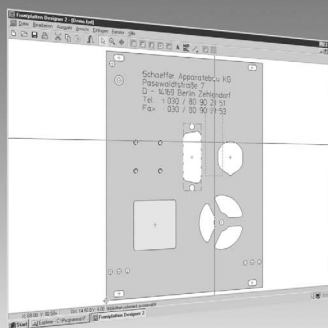
## Front Panels?

Download the free »Front Panel Designer« to design your front panels in minutes



Order your front panels online and receive them just in time

[www.frontpanelexpress.com](http://www.frontpanelexpress.com)

Unrivaled in price and quality for small orders



at 100 samples per cycle). If we measure from zero crossing to zero crossing point (the proper method), the basic A/D error is 0.224 degrees (see above). So, our total error can be a maximum of 3.82 degrees or 1.06%. The 1,000 Hz signal might be measured as 1,060 Hz. Again, this is well in excess of the basic 0.4% eight-bit A/D error.

You can improve things by sampling faster. You will need to sample every 1.44 degrees (0.4% of 360) or 250 samples per cycle to match the A/D error of 0.4%. For our 1,000 Hz signal, this comes to a 250,000 Hz sample rate.

Another way to increase the accuracy of your measurements is to measure multiple cycles. This is usually easy to do. Count 10 cycles instead of one for a 10-fold increase in accuracy. This spreads the error over 10 cycles and reduces the per-cycle error by 10. (Many hardware frequency counters do this. Some count 1,000s of cycles for very high accuracy.)

## Phase Errors

The last basic error is phase. (Amplitude, frequency, and phase define any signal.) Basically, this is a delay error from the sampling and conversion process. This is probably the most obvious error of the three. Generally, it is usually the least significant. However, there are times when phase error can be really nasty.

First, how much error is there? With 100 samples per cycle, the error is 1% or 3.6 degrees. However, this is only due to the sampling error. There is also the acquisition error. This depends on how long the sampling process takes. Usually, this is much less than the sampling error, but it is important to verify that. (We will ignore that factor because it is A/D dependent.)

The worst case phase error from the A/D comes at the peak and trough of the sine wave where the amplitude changes take a

relatively long time. This is the opposite of the frequency error above. The amplitude error can be 1/256 of full-scale. This corresponds to 0.996 instead of 1.000 (full-scale equals 1.000). The inverse sine of 0.996 is about 85 degrees. This is a difference of 5 degrees from the proper value of 90. Add this 5 degree error to the sampling error of 3.6 degrees and there is a whopping 8.6 degree potential phase error (or 9.5%) at 90 degrees. This is nearly 25 times worse than the basic A/D error of 0.4%.

How fast do we need to sample to get the phase error down to our basic 0.4% A/D amplitude error? Quite simply, you can't get there from here. We just saw that there was an inherent 5 degree error due to the step-size of our eight-bit A/D. An eight-bit A/D is just not good enough to resolve 1.44 degrees (0.4% of 360

degrees). We will need a step-size of 0.03%, which corresponds to about 3,000 steps — which means a 12-bit A/D converter.

Here's how those values were determined. Our desired resolution is 1.44 degrees. The worst case point is at 90 degrees. So, we have to be able to resolve the difference in amplitude between 90 degrees and 88.56 degrees (90-1.44). The sine of 90 degrees is 1.000 and the sine of 88.56 degrees is 0.99968. They differ by 0.00032. This defines the minimum step-size necessary (with a full-scale of 1.000). There are 3,125 steps of 0.00032 in a full-scale value of 1.000 (or 1/3125). A 12-bit A/D has 4,096 steps.

We still have to sample faster, too. We saw that 100 samples per cycle yielded a 3.6 degree error. It's easy to calculate our sampling speed for 1.44 degrees per sample. It's just 360/1.44 or 250 samples per cycle.



**DeoxIT<sup>®</sup> TIP**  
of the month

**INCREASE DATA SPEEDS**  
and eliminate  
intermittents

Apply DeoxIT to edge connectors and cable connections to increase performance and reliability!



Available in spray, pen & other forms

**Improves the Performance of ALL Electrical Devices & Equipment GUARANTEED!**

*Cleans, Enhances, Rejuvenates, Protects...Electrical Connections*



- Audio/Radio
- Computer
- Automotive
- Communications
- Marine
- Electrical
- Video
- Photography
- Medical
- Security
- Avionics

Available at:




Since 1956



LABORATORIES, INC.

[electronicspirin.com](http://electronicspirin.com)

**Used by those who demand the best:**

- Bose
- Ford
- General Electric
- Hewlett Packard
- Honeywell
- Intel
- Monster Cable
- Motorola
- Texas Instruments
- Toshiba
- Xerox
- and Many More!

With our 1,000 Hz signal, our new sampling speed is 250,000 Hz (with a 12-bit A/D).

## Think

The purpose of these exercises is to show how carelessness can create significant problems. It's important to stop and think about

what actually happens during an A/D conversion. It's important to be able to determine these fundamental sources of error.

Also, of course, it's critical to understand how these errors can affect your design.

Most of the time, you should have a good idea of what signal you expect your A/D to see. You should

always know what is to be done with the A/D data, even if that is not your job. It makes no sense to design eight-bit hardware when the software requires 12 bits of resolution. Many times, the A/D is only measuring a slowly varying signal, which is essentially DC (like room temperature).

In such cases, the error considerations are simple, but don't think all situations are like that. It can't be over-emphasized that you need to know which signal parameters are important (amplitude, frequency, phase) and how to determine the error budget for your application.

## Error Is in the Eye of the Tester

You may have noticed that there are a number of ways to calculate the above errors.

For example, you might argue that the worst case frequency error should be measured from peak to peak rather than from zero crossing to zero crossing. The zero crossing procedure gives a smaller error. Conversely, the phase error could be reduced by measuring zero crossings rather than peaks.

"Standard engineering practice" dictates how these errors are measured. However, I am not aware of any reference that details what "standard engineering practice" actually is. There are books on "standard methods," but these are chemical analytical techniques. I'm also sure that there are probably references in various text books and manuals that provide occasional examples, but I haven't found anything like a collection of standard engineering practices. (If you know of such a collection, let me know.) These techniques are usually learned from experience.

First, all errors should be defined as worst case errors. "Average" errors or "typical" errors should never be used without first stating — very clearly — what the worst case error actually is. Proper engineering must always

## HAMBOREE® 2005

*Southeast's Top Choice for  
Communications • Electronics • Computers*

**February 5-6, 2005**

**Fair Expo Center, Miami, Florida**

**Manufacturers, Dealers, Tailgate,  
License Exams, Fox Hunts, Awards**

**[www.hamboree.org](http://www.hamboree.org)**

**[wd4sfg@bellsouth.net](mailto:wd4sfg@bellsouth.net) or [w4wyr@arrrl.net](mailto:w4wyr@arrrl.net)**

**TEL: 305-226-5346 or 305-642-4139**

Details via mail: Evelyn Gauzens, W4WYR, 2780 N.W. 3rd St, Miami, FL 33125

**SO. FLORIDA SECTION CONVENTION**

## The Power to Design...

**PICs AVR KITS PC I/O  
CPLDs**

### Development Tools & Kits


Kits for most micros, CPLDs, and more starting at \$15...

- Universal CPU Board
- PIC and AVR Kits
- Programmable Logic Kits
- SeaBass Basic Compiler (as low as \$10!)
- TTL RS232 Adapters
- PC I/O for Basic, C, Java, Linux, and More
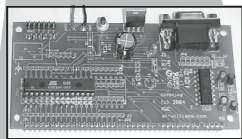
### PAK Coprocessors

Add powerful features to any microcontroller project. Perfect for use with Basic Stamps! Starting at **under \$10...**

- Floating Point & A/D
- PWM & Pulse Output
- Servo Control
- Pulse Input
- PS/2 Keyboard or Mouse




C Programmable AVR Kit  
\$39.95




RS232 Adapter  
Sale: \$13.95



Serial PWM  
\$24.95

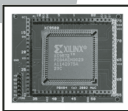

Xilinx CPLD Kit  
Starts at \$49.95

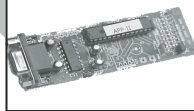

PIC Programming Kit  
Starts at \$29.95

**Visit us for free tools, tutorials and projects**

**[www.awce.com/nv](http://www.awce.com/nv)**

account for the worst case scenario. Otherwise, failures will occur. Some failures are trivial. Others can be catastrophic. No good engineer tolerates a failure based on faulty error estimates or wishful thinking.

So, why is the above frequency error not the absolutely worst error possible? It's because the accepted practice is to measure the frequency of a signal with the zero crossing points. There are two basic reasons for this. The first is that it's pretty easy to determine the zero crossing points. The second is that the steepest slope of the sine wave is there, which makes the measurement the most precise. The error calculated above is the worst case using standard engineering practice.

The phase error is not measured that way because proper phasing implies that there are two systems working together. (Any phase measurement must relate to another phase measurement.)

Typically, phase measurements are used in motors or positioning systems. In such applications, phase comparisons are required over the whole 360 degree range. Therefore, the worst case error must be defined for a full 360 degrees. This is very different from the frequency measurement that only required two points on that 360 degree interval.

## Reducing the Errors

There are two common ways to reduce basic errors at the A/D. As noted above, you can increase the sampling speed or increase the resolution. You can also use software. Probably the easiest method is to use multiple measures. I've discussed this previously in my "Statistics" columns (May and June 2004). Very briefly, you can increase the precision of a system by taking repeated measurements of the same signal and averaging them. The noise in the measurements will tend to cancel, while the true signal will tend to reinforce itself.

In theory, you can generally

expect a decrease in error that is equal to the square root of the number of measures. (Four measures reduces the error by a factor of two; 100 measures reduces it by a factor of 10.) There are other, more complicated methods, as well. No error reduction system is suitable for every application. Be sure the method you choose is appropriate.

## Conclusion

Using a basic low speed A/D is not always as simple as it first appears. Amplitude, frequency, and phase errors may be much larger than expected. Knowing how to anticipate and calculate these errors is an important part of data acquisition. **NV**

# Embedded Solutions.

*Dozens of Embedded Controllers with Countless Configurations to fit ANY Industry.*

**ATMEL AVR®**  
Based Controller


**Micro64**  
AVR® Based Controller

■ Pin 1 [www.micromint.com](http://www.micromint.com)

- Small size - 1.5" x 2.1" x 0.52
- Dual powered - operates on +5V or 6.5-20V at 55 mA (typical)
- Program and Data Memories
  - 64k or 128k Bytes of In-System Reprogrammable Flash with 10,000 Write/Erase Cycles
  - 2 or 4 K Bytes EEPROM with 100,000 Write/Erase Cycles
  - 36K Bytes SRAM
  - Programming lock for Software Security
- Peripheral Features

Starting at \$119 - Single Qty

- Optional 2-channel 12-bit ADC
- 8-channel 10-bit ADC
- 8 Single-ended Channels
- 7 Differential Channels
- 2 Differential Channels with Programmable Gain (1x, 10x, 200x)
- Byte-oriented Two-wire Serial Interface (I2C)
- Dual Programmable Serial USARTs
- 1 TTL
- 1 RS-232A, RS-422, or RS485
- Master/Slave SPI Serial Interface
- Two 8-bit Timer/Counters with Separate Prescalers and Compare Modes
- Two Expanded 16-bit Timer/Counter with Separate Prescaler, Compare Mode, and Capture Mode
- Two 8-bit PWM Channels
- 6 PWM Channels with Programmable Resolution from 1 to 16 Bits
- Programmable Watchdog Timer with On-chip Oscillator
- 29 Digital I/O that can sink or source 20 mA

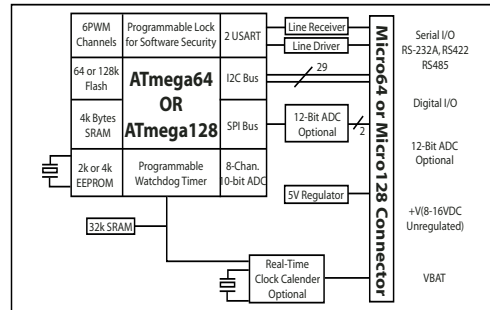

Data sheets, Online Ordering and a Complete Catalog of Products at...

[www.micromint.com](http://www.micromint.com)

## Reduce Your Time to Market.

Minimize your time from conception to production by utilizing one of Micromint's market-proven controllers. Whether your concerns are digital or analog, inputs or outputs, Micromint has a product to fit your needs. Order quantities of one to thousands. Custom design and configurations are available.

With over 500,000 controllers in the marketplace, Micromint has been providing innovative, turn-key solutions to the OEM market for 24 years—from design through production, as well as packaging and shipping the final product. Our broad line of embedded controllers and turn-key solutions can turn your imagination into reality.

Visit our website @ [www.micromint.com](http://www.micromint.com) to see our complete line of OEM Solutions.

**Micromint**

115 Timberlachen Circle | Lake Mary, FL 32746 | 800-635-3355 | 407-262-0066 | Fax 407-262-0069

Circle #35 on the Reader Service Card.



# Tech Forum

## QUESTIONS

I have an RV and I installed a homemade electronic rear-view mirror. I already had a 5" monitor and connected it to a \$39.00 CMOS black-and-white camera with 0.1 lux light sensitivity. It works fine, but the image is opposite from a mirror view when viewed on the monitor. I solved the problem by pointing the camera vertically into a mirror positioned at 45 degrees to the rear.

There are cameras with mirror switching capabilities, but I've been unable to locate one with 0.1 lux or better sensitivity. I would like to know about modifying an existing unit or if reversing the function is built into an LSI chip where I can't get to it? A

functional diagram or schematic of a camera would be helpful.

#1051

Anonymous  
via Internet

I am looking for a simple on/off switch that can be triggered by electrodes placed on the skin. It needs to have a sensitivity adjustment. I would also like to have it opto-isolated for safety. Any suggestions or places I can look?

#1052

Chris Tauscher  
via Internet

I have acquired an HP 7580b plotter that is mechanically sound. When I turn it on, E02 is displayed after a self-test. The operator manual says it's a microprocessor error/ROM

checksum error. When I plot a drawing, it plots to one side and only half of the drawing is on the page. HP does not support this plotter any more and I am having trouble acquiring information on how to troubleshoot. Where should I start?

#1053

Alex Malachowski  
via Internet

Anyone know of an after-market lens to convert a common PC board camera into a microscope with a magnification between 60 and 150X?

#1054

Joe R.  
via Internet

I recently purchased a communications test set for aligning my ham radio related equipment. The output generator's frequency is set using thumbwheel switches. Although I have had no trouble aligning receivers with this piece of test equipment, I got quite a surprise when I attached three frequency counters to the output. The readings go wild, but — when I connect them to older signal generators — the responses are as expected. After hooking the test set to my oscilloscope, I saw the reason. The signal generator is synthesized, not a pure sign wave, and is chock full of harmonics.

How, if at all, can I filter the output sufficiently so a frequency counter can be properly used? A series of low pass filters lined up to be switched in and out up to 1 GHz seems a little far fetched.

#1055

John Ciperano K4EBC  
via Internet

I'd like to use X10 cameras and receivers — such as those sold by **www.x10.com** — to beef up the security of my home, inside and out.

The problem is that the units do not secure their transmissions, which leaves me vulnerable to outsiders seeing inside my home, knowing where things are, and whether or not someone is at home. I've contacted the resellers and they confirmed they have no security.

This is a READER-TO-READER Column. All questions AND answers will be provided by *Nuts & Volts* readers and are intended to promote the exchange of ideas and provide assistance for solving problems of a technical nature. All questions submitted are subject to editing and will be published on a space available basis if deemed suitable to the publisher. All answers are submitted by readers and **NO GUARANTEES WHATSOEVER** are made by the publisher. The implementation of any answer printed in this column may require varying degrees of technical experience and should only be attempted by qualified individuals. Always use common sense and good judgement!

Send all material to *Nuts & Volts Magazine*, 430 Princeland Court, Corona, CA 92879, OR fax to (951) 371-3052, OR email to [forum@nutsvolts.com](mailto:forum@nutsvolts.com)

## ANSWER INFO

- Include the question number that appears directly below the question you are responding to.
- Payment of \$25.00 will be sent if your answer is printed. Be sure to include your mailing address if responding by email or we can not send payment.
- Your name, city, and state, will be printed in the magazine, unless you notify us otherwise. If you want your email address printed also,

indicate to that effect.

- Comments regarding answers printed in this column may be printed in the Reader Feedback section if space allows.

## QUESTION INFO

### To be considered

All questions should relate to one or more of the following:

- 1) Circuit Design
- 2) Electronic Theory
- 3) Problem Solving
- 4) Other Similar Topics

### Information/Restrictions

- No questions will be accepted that offer equipment for sale or equipment wanted to buy.
- Selected questions will be printed one time on a space available basis.
- Questions may be subject to editing.

### Helpful Hints

- Be brief but include all pertinent information. If no one knows what you're asking, you won't get any response (and we probably won't print it either).
- Write legibly (or type). If we can't read it, we'll throw it away.
- Include your Name, Address, Phone Number, and Email. Only your name, city, and state will be published with the question, but we may need to contact you.

Can anyone suggest a means to securely transmit data from the X10 cameras to the receivers? External methods are okay, but I suspect tapping inside connections would work best.

**#1056** **Errol White**  
via Internet

Regarding reading an ADC output from an aperture opening, then advancing film or paper to be cut, I understand the ADC and the electronics. I know little about programming; could this be done with a PIC?

**#1057** **Arthur Williams**  
Ashland City, TN

I'm using an LM3909 in a circuit to control a flashing red and green light on a model railroad. Is there a pin-for-pin replacement for it? If not, is there one that isn't pin-for-pin?

**#1058** **R. Thompson**  
Richmond, MO

## ANSWERS

### [20410 - February 2004]

*I have a surplus VFD display module, but no specs. It looks like one of those large cash register displays that's mounted on a pole. Inside is a pair of Futaba M202LD01DA vacuum fluorescent displays. The interface cable has eight pins where 20 VDC power is applied and an RS-485 serial interface is used to talk to the modules.*

I, too, have one of these displays. I talked to the engineers at Futaba, who said that this display unit is a customer-proprietary product and no information is available.

They did allude to the fact that the ROM uses a completely unorthodox pattern for addressing the display. I've searched the Internet without success and even pulled a few strings at Futaba with the same results. Sorry.

**Ed Edmondson, Jr., Ph.D.**  
Alamosa, CO

### [3046 - March 2004]

*Does anyone have a simple circuit that uses an IR sensor to trigger a camera? I'd like to snap pictures of the nocturnal visitors in the backyard of my country home.*

**#1** A simple solution — though perhaps expensive — is to buy a Stealth Cam. Sportsman's Guide ([www.Sportsmansguide.com](http://www.Sportsmansguide.com) or 800-882-2962) has two models on their website. These units are self-contained, weatherproof 35 mm cameras. They use standard 35 mm film slides — print or black-and-white. They sense motion and take pictures with flash. They have options for how many pictures at a time and how long to delay between pictures. The cheapest is part number WX2-73967 at \$79.97.

**Jim Schmidt**  
Deer Lodge, MT

**#2** Buy an IR floodlight (motion-sensing flood light) unit at Home Depot. Remove the floodlight lamp sockets and wire a relay with a 120 VAC coil in place of one of the sockets. Control the camera with the relay contacts. The cost is about \$10.00 for the sensor and \$5.00 for the relay.

**Anonymous**  
via Internet

### [50410 - May 2004]

*I have an old keyboard (from a Wyse 2108 computer, vintage 1988 or so). It has a fantastic touch that I have been unable to find in modern keyboards. I've tried all 24 possible combinations of the four signals in an adapter cable, but none of them works. I'm guessing that there is some other incompatibility preventing this old keyboard from working on a more modern computer.*

The Wyse 2108 is not a computer, but a terminal. What you can do is use it as such by installing Linux on your PC and connecting the Wyse to a serial port that is

configured as a terminal line. Unfortunately, you can only use shell commands on your terminal and not all the fancy graphics environments and applications that are available for Linux nowadays.

Therefore, a better solution for your question is to get an old PS/2 or USB keyboard for free somewhere in the garbage or at a flea market. Each keyboard has a controller that converts keys connected in a matrix to the PS/2, USB, or other bus protocol. (The first IBM-PC keyboards back in the 1980s were equipped with the 8048 microcontroller.) Your task now is to connect the Wyse terminal keys to the matrix of the controller which was obtained from the "garbage" keyboard.

**Gerrit Polder**  
The Netherlands

### [9042- September 2004]

*I am trying to find info on a kit that was offered back in Radio Electronics Magazine called the HyperClock. It was offered by an outfit named SkiTronix around 1991. I built one back in high school and it has just now failed. I cannot locate the schematics or magazine issue that featured it. Searching the web has not yielded anything.*

This was answered by many N&V readers, but William Richter was the first to supply a photocopy of the actual article to Rich White. Thanks, William! — Editor Dan

### [10046- October 2004]

*I just installed new AT & T 2.4 GHz phones: a base and three handsets. Now — if all the phones are in their charging cradles — I get big, double horizontal bars on TV channels 4 and 5 and buzz on my portable FM radio. If the phones are out of their cradles, everything is okay.*

They are no doubt using pulse width modulation to regulate battery charging and the shielding is poor.

Try purchasing a choke core (RadioShack 273-104) and wind the power cord through it per the directions. Put the choke as close to the base unit as possible. If that is not sufficient, try wrapping the base units in aluminum foil. If that works, I would return them and demand my money back.

**Russ Kincaid**  
Milford, NH

## [10047- October 2004]

*I've just picked up a couple of 6" neon light tubes that I want to put into my PC. The tubes were sold for automotive use and have power converters — 12 VDC/150 mA in, 1,000 V/15 mA out. I could buy a module that will "blink" the lights to music, but I want a different effect.*

*I want the lights to appear to "breathe" — slowly dimming to some adjustable level (maybe 30-40%) and then going back to full brightness again without pause.*

In short, you cannot slowly dim a neon tube. You can flash the tube on/off, but not partially dim it. Any neon gas discharge tube has a distinct voltage value where it will begin conducting current. Any voltage below the turn-on point will do nothing to the tube because the tube has a very high resistance between its terminals (so no current can flow and no glow is emitted). Once the turn-on voltage is reached, the resistance across the terminals drops very low and the neon gas conducts current emitting the glow you see.

The voltage — say 1,000 volts — must be current limited to only a few tens of milliamps, typically. This can be done with a series resistor or electronically in the design of the power supply. An increase in the specified operating voltage or current may make the tube slightly brighter, but at a great reduction to its life. Lowering the voltage will make almost no change in brilliance and then, suddenly — when the cut-

off voltage is reached — the tube will stop conducting.

Input is given at 12 volts DC. You cannot decrease this voltage, as the power supply will not work properly and increasing significantly above 12 volts may result in damage to the tube or power supply.

**Erik von Seggern**  
via Internet

## [11041- November 2004]

*Does anyone know of a source or replacement for a 95H0359 180 MHz triple or/nor gate IC? It was used in a Heathkit IB-1103 frequency counter, part number 443-79.*

I would consider buying a complete unit (eBay) as spare parts.

I see IB-1103s selling in the \$10.00-\$20.00 range. This way, you will have a complete set of replacement parts — including the nixie tubes — should other parts fail.

If you know the internal logic of the device (sometimes this will be shown on the schematic), it may be possible to replace the device with a programmable logic device. Just make sure that the supply voltage is correct because some of Heathkit's digital logic ran in the 3 V range, not 5 V. Have a look at the PALCE16V8 (AMD), GAL16V8 (Lattice), and XC7500 (Xilinx) series of devices.

I'd try Motorola and National Semiconductor Databooks. The part may have been given an OEM part number for sale to Heathkit, but most likely it was also sold as a standard device under a more well-known part number. If it is a 5 V device, try looking in the 7400/74LS/74ALS/74F series for a device with the same functionality and pinout.

**Phillip Stevens**  
Pocasset, MA

## [11044- November 2004]

*I need a variable speed PWM controller that can drive a brushed DC motor at 48 volts (or higher) and at about 200 or 300 amps.*

*Is there, perhaps, a kit? It's for an electric bike.*

While I do not know of any kits with those ratings, you should check with your local forklift dealer about a "General Electric 'EV-1'" controller. They are used in a lot of forklifts and have the ratings that you require. They seem to work forever without much — if any — maintenance.

**Ron Baxter**  
Hayward, CA

## [11047- November 2004]

*I am trying to find articles on building a DC accumulating ammeter, similar to an AC watt/hour meter. It will be used to monitor the charge/discharge of an "off the grid" home power source.*

The exact solution to this question was published in the November 1994 issue of *Popular Electronics Magazine* as a construction article starting on page 50. It is an easily constructed battery ampere-hour meter that is powered by a 9 V battery. It works in both directions and will accumulate the number of Ah delivered to a load or to a battery under charge.

The load current is passed through a 0.1  $\Omega$  resistor connected to a linear current-to-voltage converter that provides 1 V per ampere output. A Teledyne voltage-to-frequency converter chip — TC9402CPD — is used to convert the detected voltage to a frequency. The output frequency of the Teledyne chip is adjusted to 582.5 Hz when the detected current is 0.1 ampere.

A CD4045 binary divider chip is used to divide the 582.5 Hz down to a frequency of 0.000278 Hz, which is 1 pulse per hour for each 0.1 ampere of current. This is followed by a set of two CD4029 counter chips driving a pair of LCD display modules, which provide a two-digit display of the ampere-hour count in increments of 0.1 Ah.

**Anthony J Caristi**  
Waldwick NJ



|                                     |       |                                     |    |  |    |                                      |            |                                      |    |
|-------------------------------------|-------|-------------------------------------|----|--|----|--------------------------------------|------------|--------------------------------------|----|
| Abacom Technologies .....           | 77    | Cunard Associates .....             | 53 | Integrated Ideas & Technologies, Inc. .... | 70 | Net Media .....                      | 2          | Smartronix .....                     | 39 |
| ActiveWire, Inc. ....               | 53    | Earth Computer Technologies .....   | 30 | Intronics, Inc. ....                       | 53 | Parallax, Inc. ....                  | Back Cover | Square 1 Electronics .....           | 67 |
| All Electronics Corp. ....          | 41    | eBay .....                          | 11 | Jameco .....                               | 27 | PCB123/PCBexpress .....              | 5          | Supercircuits .....                  | 35 |
| APEC 2005 .....                     | 20    | Electronic Design Specialists ..... | 85 | Jaycar Electronics .....                   | 7  | Pico Technology Ltd. UK .....        | 10         | Surplus Sales of Nebraska .....      | 24 |
| Atlantic Int'l Institute, Inc. .... | 25    | Electronix Express .....            | 29 | LabJack .....                              | 89 | PULSAR .....                         | 30         | Technological Arts .....             | 23 |
| Atomic Time .....                   | 88    | EMAC, Inc. ....                     | 20 | Lemos International Co., Inc. ....         | 25 | Pulsar, Inc. ....                    | 53         | Trace Systems, Inc. ....             | 79 |
| AWC .....                           | 92    | ExpressPCB .....                    | 9  | Linx Technologies .....                    | 83 | QKITS .....                          | 53         | Trilogy Design .....                 | 78 |
| Bellin Dynamic Systems, Inc. ....   | 53    | Front Panel Express LLC .....       | 90 | Lynxmotion, Inc. ....                      | 49 | R4Systems, Inc. ....                 | 73         | Tropical Hamboree 2005 .....         | 92 |
| C & S Sales, Inc. ....              | 75    | Hagstrom Electronics, Inc. ....     | 87 | Matco, Inc. ....                           | 53 | RABBIT .....                         | 63         | V&V Machinery & Equipment, Inc. .... | 53 |
| CAIG Laboratories, Inc. ....        | 91    | Halted Specialties Co. ....         | 3  | Maxstream .....                            | 46 | Ramsey Electronics, Inc. ....        | 12-13      | Windsor Distributors .....           | 21 |
| Circuit Specialists, Inc. ....      | 98-99 | Hobby Engineering .....             | 79 | microEngineering Labs .....                | 52 | RJL Systems, Inc. ....               | 69         | www.bsio.us .....                    | 53 |
| Command Productions .....           | 47    | Imagine Tools .....                 | 33 | Micromint .....                            | 93 | Rogue Robotics .....                 | 53         | XGameStation .....                   | 53 |
| Conitec DataSystems .....           | 70    | Information Unlimited .....         | 86 | Multilabs .....                            | 37 | Saelig Company .....                 | 31, 40     | Zagros Robotics .....                | 53 |
| Cook's Institute .....              | 74    |                                     |    |  |    | Scott Edwards Electronics, Inc. .... | 46         |                                      |    |

## AMATEUR RADIO & TV

|                                 |       |
|---------------------------------|-------|
| Atomic Time .....               | 88    |
| Ramsey Electronics, Inc. ....   | 12-13 |
| Supercircuits .....             | 35    |
| Surplus Sales of Nebraska ..... | 24    |
| Windsor Distributors .....      | 21    |

## BATTERIES/CHARGERS

|                         |    |
|-------------------------|----|
| Cunard Associates ..... | 53 |
|-------------------------|----|

## BUYING ELECTRONIC SURPLUS

|                                   |    |
|-----------------------------------|----|
| Earth Computer Technologies ..... | 30 |
| Jaycar Electronics .....          | 7  |

## CCD CAMERAS/VIDEO

|                                |       |
|--------------------------------|-------|
| Circuit Specialists, Inc. .... | 98-99 |
| Matco, Inc. ....               | 53    |
| Ramsey Electronics, Inc. ....  | 12-13 |
| Supercircuits .....            | 35    |

## CIRCUIT BOARDS

|                                      |        |
|--------------------------------------|--------|
| Cunard Associates .....              | 53     |
| ExpressPCB .....                     | 9      |
| Maxstream .....                      | 46     |
| Micromint .....                      | 93     |
| PCB123/PCBexpress .....              | 5      |
| Pulsar, Inc. ....                    | 53     |
| R4Systems, Inc. ....                 | 73     |
| Saelig Company .....                 | 31, 40 |
| V&V Machinery & Equipment, Inc. .... | 53     |

## COMPONENTS

|                                    |    |
|------------------------------------|----|
| Bellin Dynamic Systems, Inc. ....  | 53 |
| Electronix Express .....           | 29 |
| Front Panel Express LLC .....      | 90 |
| Jameco .....                       | 27 |
| Lemos International Co., Inc. .... | 25 |
| Linx Technologies .....            | 83 |
| Maxstream .....                    | 46 |
| Micromint .....                    | 93 |
| PCB123/PCBexpress .....            | 5  |
| Pulsar, Inc. ....                  | 53 |
| Windsor Distributors .....         | 21 |

## COMPUTER

|                                   |    |
|-----------------------------------|----|
| <b>Hardware</b>                   |    |
| ActiveWire, Inc. ....             | 53 |
| Earth Computer Technologies ..... | 30 |
| Hagstrom Electronics, Inc. ....   | 87 |
| Halted Specialties Co. ....       | 3  |
| Imagine Tools .....               | 33 |
| Smartronix .....                  | 39 |
| Surplus Sales of Nebraska .....   | 24 |

|                                      |            |
|--------------------------------------|------------|
| <b>Microcontrollers / I/O Boards</b> |            |
| Abacom Technologies .....            | 77         |
| AWC .....                            | 92         |
| Conitec DataSystems .....            | 70         |
| EMAC, Inc. ....                      | 20         |
| microEngineering Labs .....          | 52         |
| Micromint .....                      | 93         |
| Multilabs .....                      | 37         |
| Net Media .....                      | 2          |
| Parallax, Inc. ....                  | Back Cover |
| R4Systems, Inc. ....                 | 73         |

|                                      |    |
|--------------------------------------|----|
| Scott Edwards Electronics, Inc. .... | 46 |
| Square 1 Electronics .....           | 67 |
| Technological Arts .....             | 23 |
| Trace Systems, Inc. ....             | 79 |
| www.bsio.us .....                    | 53 |
| XGameStation .....                   | 53 |

|                      |    |
|----------------------|----|
| <b>Software</b>      |    |
| PULSAR .....         | 30 |
| Trilogy Design ..... | 78 |

## DESIGN/ENGINEERING/REPAIR SERVICES

|                                      |    |
|--------------------------------------|----|
| ExpressPCB .....                     | 9  |
| Front Panel Express LLC .....        | 90 |
| Pulsar, Inc. ....                    | 53 |
| R4Systems, Inc. ....                 | 73 |
| RJL Systems, Inc. ....               | 69 |
| Trace Systems, Inc. ....             | 79 |
| V&V Machinery & Equipment, Inc. .... | 53 |
| www.bsio.us .....                    | 53 |

## EDUCATION

|                                     |    |
|-------------------------------------|----|
| Atlantic Int'l Institute, Inc. .... | 25 |
| Command Productions .....           | 47 |
| Cook's Institute .....              | 74 |
| EMAC, Inc. ....                     | 20 |
| Hobby Engineering .....             | 79 |
| RJL Systems, Inc. ....              | 69 |
| XGameStation .....                  | 53 |

## ENCLOSURES

|  |    |
|--|----|
| Integrated Ideas & Technologies, Inc. .... | 70 |
|--|----|

## EVENTS

|                              |    |
|------------------------------|----|
| APEC 2005 .....              | 20 |
| Tropical Hamboree 2005 ..... | 92 |

## KITS

|                                      |       |
|--------------------------------------|-------|
| C & S Sales, Inc. ....               | 75    |
| Earth Computer Technologies .....    | 30    |
| EMAC, Inc. ....                      | 20    |
| Hobby Engineering .....              | 79    |
| Imagine Tools .....                  | 33    |
| Information Unlimited .....          | 86    |
| Jaycar Electronics .....             | 7     |
| QKITS .....                          | 53    |
| RABBIT .....                         | 63    |
| Ramsey Electronics, Inc. ....        | 12-13 |
| Scott Edwards Electronics, Inc. .... | 46    |
| XGameStation .....                   | 53    |

## LASERS

|                             |    |
|-----------------------------|----|
| Information Unlimited ..... | 86 |
|-----------------------------|----|

## MISC./SURPLUS

|                                 |    |
|---------------------------------|----|
| All Electronics Corp. ....      | 41 |
| Front Panel Express LLC .....   | 90 |
| Halted Specialties Co. ....     | 3  |
| Surplus Sales of Nebraska ..... | 24 |
| Windsor Distributors .....      | 21 |

## PROGRAMMERS

|                           |    |
|---------------------------|----|
| Conitec DataSystems ..... | 70 |
| Intronics, Inc. ....      | 53 |

|                             |    |
|-----------------------------|----|
| microEngineering Labs ..... | 52 |
|-----------------------------|----|

## PUBLICATIONS

|                            |    |
|----------------------------|----|
| Square 1 Electronics ..... | 67 |
|----------------------------|----|

## RF TRANSMITTERS/RECEIVERS

|                           |    |
|---------------------------|----|
| Abacom Technologies ..... | 77 |
| Linx Technologies .....   | 83 |
| Matco, Inc. ....          | 53 |

## ROBOTICS

|                                    |    |
|------------------------------------|----|
| Hobby Engineering .....            | 79 |
| Imagine Tools .....                | 33 |
| LabJack .....                      | 89 |
| Lemos International Co., Inc. .... | 25 |
| Lynxmotion, Inc. ....              | 49 |
| Net Media .....                    | 2  |
| Rogue Robotics .....               | 53 |
| Zagros Robotics .....              | 53 |

## SATELLITE

|                                    |    |
|------------------------------------|----|
| Lemos International Co., Inc. .... | 25 |
|------------------------------------|----|

## SECURITY

|                             |    |
|-----------------------------|----|
| Information Unlimited ..... | 86 |
| Linx Technologies .....     | 83 |
| Matco, Inc. ....            | 53 |
| Supercircuits .....         | 35 |

## STEPPER MOTORS

|              |    |
|--------------|----|
| Jameco ..... | 27 |
|--------------|----|

## TEST EQUIPMENT

|                                     |        |
|-------------------------------------|--------|
| Bellin Dynamic Systems, Inc. ....   | 53     |
| C & S Sales, Inc. ....              | 75     |
| Circuit Specialists, Inc. ....      | 98-99  |
| Conitec DataSystems .....           | 70     |
| eBay .....                          | 11     |
| Electronic Design Specialists ..... | 85     |
| Intronics, Inc. ....                | 53     |
| Jaycar Electronics .....            | 7      |
| LabJack .....                       | 89     |
| Pico Technology Ltd. UK .....       | 10     |
| Saelig Company .....                | 31, 40 |
| Smartronix .....                    | 39     |
| Trace Systems, Inc. ....            | 79     |

## TOOLS

|                              |    |
|------------------------------|----|
| C & S Sales, Inc. ....       | 75 |
| CAIG Laboratories, Inc. .... | 91 |

## VIDEO

|                 |    |
|-----------------|----|
| Multilabs ..... | 37 |
|-----------------|----|

## WIRE/CABLE & CONNECTORS

|                  |    |
|------------------|----|
| Jameco .....     | 27 |
| Smartronix ..... | 39 |

**Digital Storage Oscilloscope Module**

PC based Digital Storage Oscilloscope, 200MHz 5GS/s equiv. sampling USB interface

Details & Software Download at Web Site

> Test Equipment > Oscilloscopes/Outstanding Prices

Item# **200DSO** Only **\$859.00**

Convert any PC with USB interface to a high performance Digital Storage Oscilloscope. This is a sophisticated PC based scope adaptor providing performance compatible to mid/high level stand alone products costing much more! Comes with two probes.

**ESD Safe Thru-Hole Soldering/Desoldering Repairing System**

Item# **CSI701**



Only **\$199.00!**

High precision thermostatically controlled station w/ 35W Iron & desolder gun. Built-in double cylinder vacuum pump.

Details at Web Site

> Soldering Equipment & Supplies > Rework Stations

**Digital Laser Tachometer**

- 5 digit, 6" LCD Display
- 2.5-99,999 RPM test range
- Auto-Ranging
- 2" to 80" test range
- memory function

Details at Web Site

> Test Equipment > Specialty Test Equipment

**\$49.00!**

Item# **DT-6234C**

**Triple Output Bench Power Supply**

**CSI3003X3/\$179.00**  
(qty 5+/\$169.00)

with Large LCD Displays  
Output: 0-30VDC x 2 @ 3 AMPS  
& 1ea. fixed output @ 5VDC@3A  
Source Effect:  $5 \times 10^{-4} = 2mV$   
Load Effect:  $5 \times 10^{-4} = 2mV$   
Ripple Coefficient:  $< 250uV$   
Stepped Current: 30mA +/- 1mA  
Input Voltage: 110VAC

Details at Web Site

> Test Equipment > Power Supplies

**www.CircuitSpecialists.com**

**Circuit Specialists Soldering Station w/Ceramic Element & Seperate Solder Stand**

**\$34.95!**

- Ceramic heating element for more accurate temp control
- Temp control knob in F(392° to 896°) & C(200° to 489°)
- 3-prong grounded power cord/static safe tip
- Seperate heavy duty iron stand
- Replaceable iron/easy disconnect
- Extra tips etc. shown at web site

Item#

**CSI-STATION1** Rapid Heat Up!

**Also Available w/Digital Display & MicroProcessor Controller**

A black soldering station with a digital display and a microprocessor controller.

Item# **CSI-STATION2**

**\$49.95**

Details at Web Site

> Soldering Equipment & Supplies > Soldering Stations

**SMD Hot Tweezer Adaptor Fits CSI Stations 1 & 2, and also CSI906**

**\$29.00**

Item#

**CSITWZ-STATION**

A black tweezer-like tool with a digital display and a microprocessor controller.

**In Business**

A diamond-shaped logo with the text 'Circuit Specialists Inc.' inside.

Since 1971

Logos for MasterCard, Visa, Discover, and American Express.

**With Certificate of Calibration!**

**Item# CSI825A++ MicroProcessor Controlled!**

Includes 4 Nozzles!

**FANTASTIC VALUE!!**

Only **\$199.00!**

**SMD RE-WORK SYSTEM w/Vacuum Pick-up tool**

Details at Web Site

> Soldering Equipment & Supplies > Rework Stations

A black device with a vacuum pick-up tool and a soldering iron.

**SMD RE-WORK SYSTEM w/Solder Iron**

Item# **CSI906**

A black device with a soldering iron and a vacuum pick-up tool.

**Incredible Deal.. only \$169.00!**

Includes 4 Nozzles!

Details at Web Site

> Soldering Equipment & Supplies > Rework Stations

**High Basic Accuracy/True RMS Digital Multimeter**

This True RMS meter provides the user with a low cost alternative when a high basic accuracy is required, especially if the application requires a **certificate of calibration**. If your facility is ISO certified and needs to maintain calibration certificates, we supply this product at a fraction of the cost you would expect to pay. Each unit is calibrated by the manufacturer implementing a state of the art Fluke calibrator, meeting NIST standards.

Details at Web Site > Digital Multimeters/World Beater Prices

Only **\$89.00!**

- Auto Ranging High Voltage test up to 1000VDC and 750VAC
- 6000 count Jumbo LCD display
- High Accuracy (basic accuracy 0.3%)
- Exclusive Patented MCU controlled ATLLI technology

A digital multimeter with a large LCD display showing '8888'.

**1500W Heat Shrink Gun**

Item# **ZD509**

With a temperature range of 392°F to 932°F & two power settings, 800W and 1500W, it will shrink tubing effortlessly. A thermo-control rotating knob on the rear of the unit will adjust the temperature electronically for precise control, while the three-way trigger switch adjusts the speeds. Comes complete with a concentrator air nozzle and a retractable stand.

Details at Web Site **Only \$18.95**

> Heat Shrink Tubing SoftTube Our Own Brand

A yellow heat shrink gun with a concentrator air nozzle.

**Protek 100MHz Realtime Scope**

**Super Blowout Price!**

- 2 Ch Dual Trace
- 6" Internal Grid
- ALTMAG
- ALTRIG
- TV Sync
- 5 Vertical Modes

A black oscilloscope with a large screen showing a waveform.

Item# **6510**

Brand New Not Refurbished! Includes 2 scope probes

**A \$975.00 Value!**

**100MHz only \$499.00**

While Supplies Last!

Details at Web Site > Test Equipment > Oscilloscopes/Outstanding Prices

**Hot Air Gun w/Digital Display for SMD's**

Now, precise temperature and airflow control is at your finger tips with this digitally controlled Hot Air Gun. Quickly solder and de-solder DIP, BGA and SMT electronic components. Plus, be able to shrink, "Heat shrink tubing".

Details at Web Site Item# **CSIHOTGUN-2**

A black hot air gun with a digital display and a control knob.

**\$89.00**

> Soldering Equipment & Supplies > Soldering Irons

**Dual Output DC Bench Power Supplies**

High stability digital read-out bench power supplies featuring constant voltage and current outputs. Short-circuit and current limiting protection is provided. SMT PC boards and a built-in cooling fan help ensure reliable performance and long life.

**NEW!**

- Source Effect:  $5 \times 10^{-4} = 2mV$
- Load Effect:  $5 \times 10^{-4} = 2mV$
- Ripple Coefficient:  $< 250uV$
- Stepped Current: 30mA +/- 1mA

**HOT ITEM!**

\*Both Models have a 1A/5VDC Fixed Output on the rear panel\*

**CSI3003X-5: 0-30v/0-3amp/1-4..\$97.00/5+..\$93.00**

**CSI5003X-5: 0-50v/0-3amp/1-4..\$107.00/5+..\$103.00**

Details at Web Site > Test Equipment > Power Supplies

**As Low As \$93.00!**

A white bench power supply with a digital display and control knobs.

**Circuit Specialists, Inc.** 220 S. Country Club Dr., Mesa, AZ 85210

800-528-1417 / 480-464-2485 / FAX: 480-464-5824

Circle #105 on the Reader Service Card.



**3M™ DataCom Cable Tester****UNBEATABLE PRICE**

This unit allows for mapping, testing and troubleshooting of various lines, including installed data communications, phone wiring and coaxial cable runs. Performs multiple test on the following cable types, up to 1000 feet in length: Unshielded telephone cables with RJ-11 and RJ-45 connectors; Ethernet 10 (100) Base-T; Token Ring; EIA/TIA-568 A/B; AT&T 258a; USOC; 50 or 75 ohm Coax with F or BNC connectors.

**Only \$49.00****Item# DT-2000**

Details at Web Site

Includes: Holster, Case, 7 Remotes &amp; Telecom Alligator Clips

&gt; Test Equipment &gt; Specialty Test Equipment

**RF Field Strength Analyzer****Compare at Over \$2000!**

The **3201** is a high quality hand-held RF Field Strength Analyzer with wide band reception ranging from 100kHz to 2060MHz. The 3201 is a compact & lightweight portable analyzer & is a must for RF Technicians. Ideal for testing, installing & maintenance of Mobile Telephone Comm systems, Cellular Phones, Cordless phones, paging systems, cable & Satellite TV as well as antenna installations. May also be used to locate hidden cameras using RF transmissions

**Item# 3201**

Details at Web Site

&gt; Test Equipment &gt; RF Test Equipment

**New Fantastic Low Price: \$1299.00!**

- WFM/NFM/AM/SSB modulated signals may be measured.
- Signal Levels up to 160Channels can be displayed simultaneously on the LCD
- PLL tuning system for precise frequency measurement and tuning
- Built-in Frequency Counter
- LED Backlight LCD (192x192 dots)
- All functions are menu selected.
- RS232C with software for PC & printer interface
- Built-in speaker

**(Includes Antenna)****Limited Time Offer****BAG of LEDs DEAL**

Normal brightness LEDs now available in **RED**, **GREEN** or **YELLOW** in 3mm or 5mm sizes. Your choice. **Each bag** contains 100 of the **same** LEDs.



**BAG-RED3MM.....\$1.50 BAG-RED5MM.....\$1.50**  
**BAG-GREEN3MM.....\$1.50 BAG-GREEN5MM.....\$1.50**  
**BAG-YELLOW3MM.....\$2.00 BAG-YELLOW5MM.....\$2.00**

**Super Bright LEDs Deal:**

|                               |                     |    |        |      |        |       |        |
|-------------------------------|---------------------|----|--------|------|--------|-------|--------|
| 53B3SCS08...5mm <b>Blue</b>   | SB LED(1500max MCD) | 1+ | \$0.70 | /10+ | \$0.65 | /100+ | \$0.60 |
| 5G3UTB-2... 5mm <b>Green</b>  | SB LED(1100max MCD) | 1+ | \$0.45 | /10+ | \$0.35 | /100+ | \$0.30 |
| 5R3UT-2/R...5mm <b>Red</b>    | SB LED(3500max MCD) | 1+ | \$0.25 | /10+ | \$0.20 | /100+ | \$0.15 |
| 53BW3SCC08...5mm <b>White</b> | SB LED(3500max MCD) | 1+ | \$1.69 | /10+ | \$1.49 | /100+ | \$1.18 |
| 5Y3STC-2...5mm <b>Yellow</b>  | SB LED(3500max MCD) | 1+ | \$0.25 | /10+ | \$0.20 | /100+ | \$0.15 |

Details at Web Site &gt; Semiconductor Devices &gt; LEDs, Displays &amp; Lamps

**FC5001 2 Way FM Radio Tester/ FC6002 Radio Frequency Tracer**

The **FC5001** 2-way FM radio tester has the ability to lock automatically and almost instantly on to any FM signal within its frequency range. The **FC6002** radio frequency tracer is useful in locating stuck transmitters or bugging devices in a room or automobile. It excels at silent detecting RF signals for RF security and counter-surveillance applications.

**FC5001: \$99.00 < RF Security > FC6002: \$149.00**

Details at Web Site &gt; Test Equipment &gt; RF Test Equipment

**SONY Super HAD CCD Color Weatherproof IR Camera**

- Day & Night Auto Switch
- Signal System: NTSC
- Image Sensor: 1/4" SONY Super HAD CCD
- Effective Pixels: 510 x 492
- Horizontal Resolution: 420TV lines
- Built-in Lens: 4.3mm
- S/N Ratio: > 48dB (AGC OFF)
- Min. Illumination: 0Lux

**1-4:\$89.00 5+:\$79.00**

Details at Web Site

&gt; Miniature Cameras(Board,Bullet,Mini's, B/W, Color)

**Item# VC-819D****SONY Super HAD CCD™ equipped camera's feature dramatically improved light sensitivity****SONY Super HAD CCD Color Camera****Item# VC-805 1-4:\$69.00 5+:\$65.00**

- Weather Proof
- Signal System: NTSC
- Image Sensor: 1/4" SONY Super HAD CCD
- Effective Pixels: 510 x 492
- Horizontal Resolution: 420TV lines
- Lens: 3.6mm
- S/N Ratio: > 48dB
- Min. Illumination: 1Lux/F1.2

**Unbelievable Price!**

Details at Web Site

&gt; Miniature Cameras(Board,Bullet,Mini's)

**SONY Super HAD CCD Mini B/W Board Camera****Item# VC-103**

- Signal System: EIA
- Image Sensor: 1/3" SONY Super HAD CCD
- Effective Pixels: 510 x 492
- Horizontal Resolution: 420TV Lines
- Lens: 3.6mm/92° Angle of View
- Min. Illumination: .05Lux/F1.2

**1-4:\$33.00 5+:\$29.00**

Details at Web Site

&gt; Miniature Cameras

**SONY Super HAD CCD Color Weatherproof IR Cameras**

- Day & Night Auto Switch
- Signal System: NTSC
- Image Sensor: 1/3" SONY Super HAD CCD
- Effective Pixels: 510 x 492
- Horizontal Resolution: 480TV lines
- Built-in Lens: 6mm/F1.5
- S/N Ratio: > 48dB
- Min. Illumination: 0Lux

**480 TV Lines Resolution****Item# VC-827D**

Details at Web Site

**1-4:\$149.00 5+:\$139.00**

&gt; Miniature Cameras(Board,Bullet,Mini's, B/W, Color)

**SONY Super HAD CCD B/W Weatherproof IR Camera**

- Day & Night Auto Switch
- Signal System: EIA
- Image Sensor: 1/3" SONY Super HAD CCD
- Effective Pixels: 510 x 492
- Horizontal Resolution: 420TV lines
- Built-in Lens: 6mm/F1.5
- S/N Ratio: > 48dB
- Min. Illumination: 0Lux

**1-4:\$69.00 5+:\$65.00 Item# VC-317D**

Details at Web Site

&gt; Miniature Cameras(Board,Bullet,Mini's)

**SONY Super HAD CCD Mini Color Pinhole Camera**

- Signal System: NTSC
- Image Sensor: 1/3" SONY Super HAD CCD
- Effective Pixels: 510 x 492
- Horizontal Resolution: 420TV lines
- Lens: 3.8mm/F2.0 Pinhole/90° Angle of View
- Min. Illumination: 0.8Lux/F1.2
- S/N Ratio: > 48dB

**Now:\$48.95****CLOSEOUT! Limited to Stock on hand****Item# VC-8063CP 1-4:\$79.95 5+:\$74.95**

Details at Web Site &gt; Miniature Cameras(Board,Bullet,Mini's)

**SONY Super HAD CCD Mini Color Camera**

- Signal System: NTSC
- Image Sensor: 1/4" SONY Super HAD CCD
- Effective Pixels: 510 x 492
- Horizontal Resolution: 420TV lines
- Lens: 3.6mm/92° Angle of View
- S/N Ratio: > 48dB
- Min. Illumination: 1.0Lux/F1.2
- White Balance: Auto tracking

**1-4:\$77.00 5+:\$73.00****Now:\$44.95****CLOSEOUT! Limited to Stock on hand**

Details at Web Site &gt; Miniature Cameras(Board,Bullet,Mini's, B/W, Color)

Visit our website for a complete listing of our offers. We have over 8,000 electronic items on line @ [www.CircuitSpecialists.com](http://www.CircuitSpecialists.com). PC based data acquisition, industrial computers, loads of test equipment, optics, I.C's, transistors, diodes, resistors, potentiometers, motion control products, capacitors, miniature observation cameras, panel meters, chemicals for electronics, do it yourself printed circuit supplies for PCB fabrication, educational D.I.Y. kits, cooling fans, heat shrink, cable ties & other wire handling items, hand tools for electronics, breadboards, trainers, programmers & much much more! **Some Deals you won't believe!**




# Apply Yourself!

## We just keep on providing you with more applications!

The Nuts & Volts of BASIC Stamps books are a favorite Parallax technical pick and are a tremendous informational resource for all PBASIC programming projects.

The latest in the series - Volume 5, contains the entire collection of Nuts & Volts "Stamp Applications" columns for 2004. Including popular columns that highlight topics such as IR distance measuring for Halloween props, remote control with Bluetooth, a drum sequencer, using the Javelin Stamp as the brain for a PLC, and more.

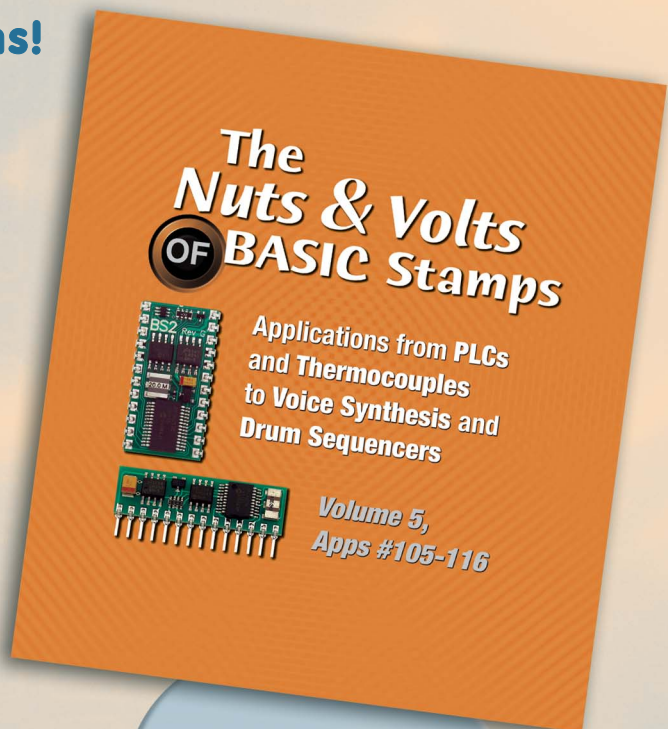**Nuts & Volts of BASIC Stamps Volume #5; #70015; \$14.95** Note: Nuts & Volts of BASIC Stamps Volumes 1, 2 & 3 are only available as free downloads from our website or from the Parallax CD. Volume 4 currently has a limited quantity available for purchase, and is also available as a free download from our website or the Parallax CD.



#70015  
\$14.95

Order online at [www.parallax.com](http://www.parallax.com)  
or call the Sales Department  
toll-free at 888-512-1024  
(Monday - Friday, 7 am - 5 pm, PT).

BASIC Stamp is a registered trademark of Parallax Inc.  
Javelin Stamp, Parallax, and the Parallax logo are trademarks  
of Parallax, Inc. ©2005 by Parallax, Inc. All Rights Reserved.

[www.parallax.com](http://www.parallax.com)  
PARALLAX